

## MODULE –5a

## Unbalanced Three Phase Systems

## Content:

## Unbalanced Three Phase Systems:


1. Analysis of three phase systems ( 3-wire and 4 wire systems )
2. Calculation of real and reactive Powers.

## 5.1 Introduction


- Industrial and residential consumers use equipment that can be single phase and / or three phase.
- In general, the distribution networks offer the two types of voltage, and the single phase is obtained from the three-phase using only the neutral and one of the phases.
- As the load on the three phases changes constantly, a four-wire (neutral + 3 phase) system is used to maintain stable voltage and provide a return path for the neutral current due to load unbalance.
- This system is used by energy distribution companies electrical, when in low voltage, for homes, commercial rooms and small industries.

## 5.1.1 For a three-phase system to be considered unbalanced if:

- The voltages of the source are not equal in modulus and / or differ in phase (different angles);
- The load impedances are unequal (at least one of them). This is the most likely situation to happen.

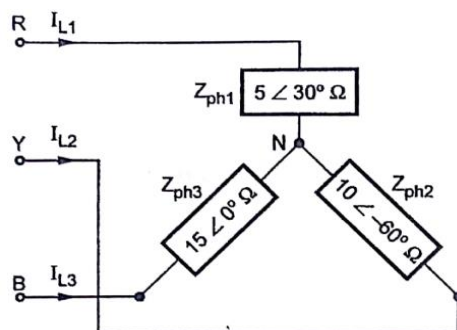**Example:**

(a) Star connected unbalanced load

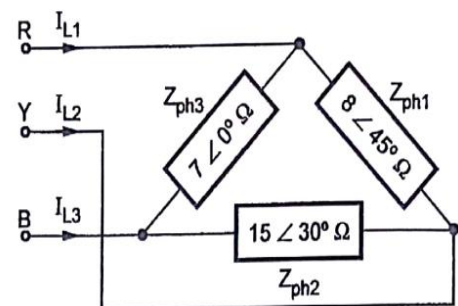

(b) Delta connected unbalanced load

## 5.2 Types of Unbalanced Loads

- The unbalanced load is the load in which the load impedances are not same but having different values.

- The values of voltages and currents are also different in each phase.
- The unbalanced loads may also be connected either in star or in delta.
- With unbalanced loads, the power in each phase has to be calculated separately.

Consider three phase star connected four wire unbalanced load system as shown in Fig.

$I_R, I_Y, I_B$  -line currents which are same as the phase currents.

$V_{RY}, V_{YB}$  and  $V_{BR}$  -line voltages.

$$I_N = I_R + I_Y + I_B$$

The phase voltage is lagging by  $30^\circ$  from the line voltage.

Let  $V_{RN}$  - reference phase voltage

Phase voltages are given by,

$$V_{RN} = V_{ph} \angle 0^\circ \text{ volts}$$

$$V_{YN} = V_{ph} \angle -120^\circ \text{ volts}$$



$$V_{BN} = V_{ph} \angle 120^\circ \text{ volts}$$

If  $Z_1, Z_2$  and  $Z_3$  are load impedances then the currents are given by,

$$I_R = \frac{V_{ph}}{Z_1} = \frac{V_{ph} \angle 0^\circ}{Z_1 \angle \phi_1} = \frac{V_{ph}}{Z_1} \angle -\phi_1 \text{ Amp.}$$

$$I_Y = \frac{V_{YN}}{Z_2} = \frac{V_{ph} \angle -120^\circ}{Z_2 \angle \phi_2} = \frac{V_{ph}}{Z_2} \angle -120^\circ - \phi_2 \text{ Amp.}$$
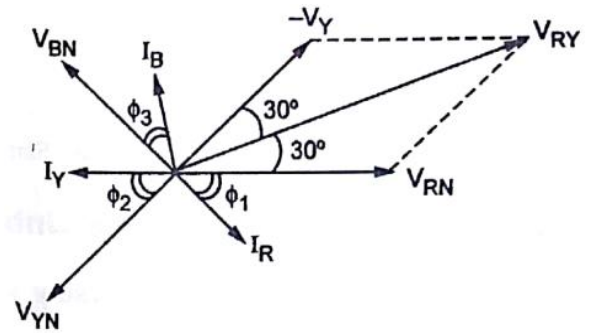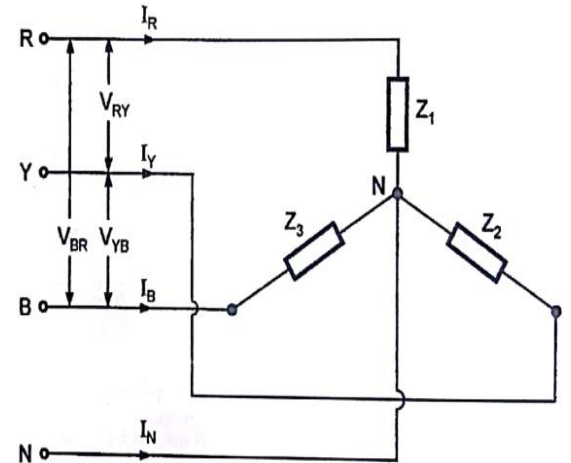
$$I_B = \frac{V_{BN}}{Z_3} = \frac{V_{ph} \angle 120^\circ}{Z_3 \angle \phi_3} = \frac{V_{ph}}{Z_3} \angle +120^\circ - \phi_3 \text{ Amp.}$$



**Thus in general following types of unbalanced loads are possible in practice**

- Unbalanced three wire star connected load.
- Unbalanced four wire star connected load.
- Unbalanced delta connected load.

### 5.3 Analysis of Three Phase Unbalanced Loads

#### a. Unbalanced Four Wire Star Connected Load

In such loads a fourth wire is used to connect the neutral of the load to the neutral of supply system. There are two cases in such a load.


##### 1. Neutral wire with zero impedance

If neutral wire has negligible impedance, it is assumed to have zero impedance. The star point of load and generator supply system get directly connected and are at the same potential. Thus in this case if line voltages are balanced & then each phase voltage is a forced voltage such that the phase voltages are balanced. The voltage across the three load impedances are equalized. Here neutral current is given by,

$$\bar{I}_N = \bar{I}_R + \bar{I}_Y + \bar{I}_B$$
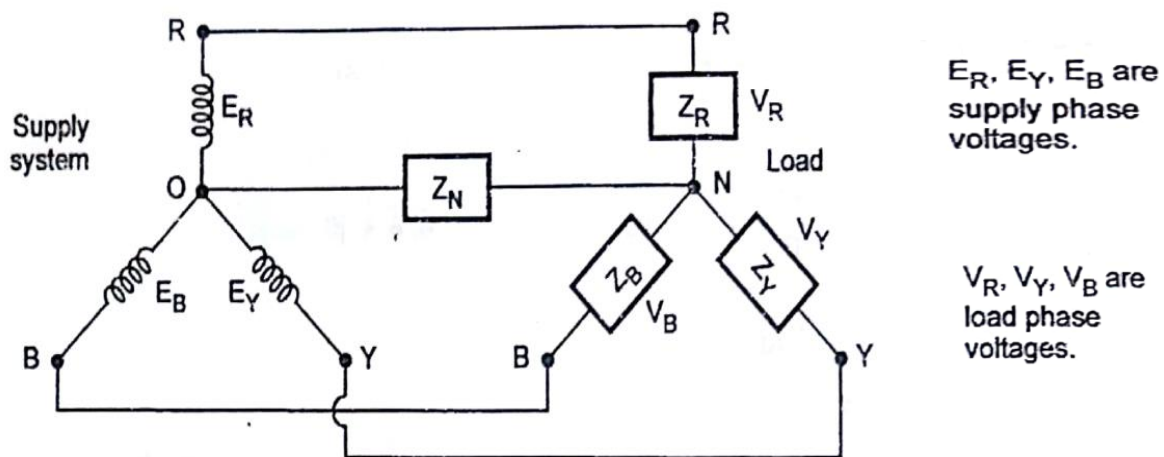
##### 2. Neutral wire with Impedance $Z_N$

In some case a neutral of load is connected to neutral of the supply through an impedance  $Z_N$ . This is shown in the Fig.



In this method, the voltage  $\bar{V}_{NO}$  is given by,

$$V_{NO} = \frac{E_R Y_R + E_Y Y_Y + E_B Y_B}{Y_R + Y_Y + Y_B + Y_N}$$

Where  $Y_R$ ,  $Y_Y$  and  $Y_B$  are the load phase admittances. Due to  $V_{NO}$ , the load phase voltages are not equal to one another.

$$\bar{V}_R = \bar{E}_R - \bar{V}_{NO}$$

$$\bar{V}_Y = \bar{E}_Y - \bar{V}_{NO}$$

$$\bar{V}_B = \bar{E}_B - \bar{V}_{NO}$$

#### b. Unbalanced Delta Connected Load

In unbalanced delta connected load, the phase voltages are same as the line voltages hence the phase currents can be obtained by dividing the phase voltages by the respective phase impedances. From the phase the line currents can be obtained.

#### 5.4 Power Factor of Unbalanced Load

- The power factor is defined as the ratio of active power to the apparent power.  
But
- in unbalanced system, each phase has different power factor hence overall factor can not
- be precisely defined.
- Still the ratio of total active power  $\sqrt{3} \cdot V_L \cdot I_L \cdot \cos \phi$  to the total apparent power  $\sqrt{3} \cdot V_L \cdot I_L$  gives approximate power factor of the unbalanced load.
- In unbalanced loads a vector power factor is defined which is defined as,

$$\text{Power factor} = \frac{\sum V I \cos \phi}{\sum V I}$$

The numerator is the algebraic sum of all the active powers of all individual phases.

$$\therefore \sum V I \cos \phi = V_{ph1} I_{ph1} \cos \phi_1 + V_{ph2} I_{ph2} \cos \phi_2 + V_{ph3} I_{ph3} \cos \phi_3$$

$$\text{While, } \sum V I = \sqrt{[\sum V I \cos \phi]^2 + [\sum V I \sin \phi]^2}$$

Where  $\sum V I \sin \phi$  is the algebraic sum of the reactive volt-amperes of all individual phases.

$$\therefore \sum V I \sin \phi = V_{ph1} I_{ph1} \sin \phi_1 + V_{ph2} I_{ph2} \sin \phi_2 + V_{ph3} I_{ph3} \sin \phi_3$$

**Numericals:**

**1. A 3-phase, 3-wire, 400V delta-connected load has impedances  $Z_{ab}=10\angle 0^\circ \Omega$ ,  $Z_{bc}=10\angle -30^\circ \Omega$  and  $Z_{ca}=10\angle 30^\circ \Omega$ . The phase sequence is  $abc$ . Determine the phase currents and line currents.**

**Soln. Given Data:**

$$V_{LL}=400 \text{ V}$$

$$Z_{ab}=10\angle 0^\circ \Omega$$

$$Z_{bc}=10\angle -30^\circ \Omega$$

$$Z_{ca}=10\angle 30^\circ \Omega$$

Calculate the Phase Voltages  $V_{ph} = \frac{V_{LL}}{\sqrt{3}}$

$$V_{ab} = V_{bc} = V_{ca} = V_{LL} = 400 \text{ V}$$

Calculate the Phase Currents

$$I_{ab} = \frac{V_{ab}}{Z_{ab}}, \quad I_{bc} = \frac{V_{bc}}{Z_{bc}}, \quad I_{ca} = \frac{V_{ca}}{Z_{ca}}$$

$$I_{ab} = \frac{400\angle 0^\circ}{10\angle 0^\circ} = 40\angle 0^\circ \text{ A}$$

$$I_{bc} = \frac{400\angle -120^\circ}{10\angle -30^\circ} = 40\angle (-120^\circ + 30^\circ) = 40\angle -90^\circ \text{ A}$$

$$I_{ca} = \frac{400\angle 120^\circ}{10\angle 30^\circ} = 40\angle (120^\circ - 30^\circ) = 40\angle 90^\circ \text{ A}$$

Calculate the Line Currents

$$I_a = I_{ab} - I_{ca}, \quad I_b = I_{bc} - I_{ab}, \quad I_c = I_{ca} - I_{bc}$$

$$I_a = 40\angle 0^\circ - 40\angle 90^\circ$$

$$|I_a| = \sqrt{40^2 + 40^2} = \sqrt{3200} \approx 56.57 \text{ A},$$

$$\angle I_a = \tan^{-1} \left( \frac{-40}{40} \right) = -45^\circ$$

$$I_b = 40\angle -90^\circ - 40\angle 0^\circ = -j40 - 40 = -40 - j40 \text{ A}$$

$$|I_b| = \sqrt{40^2 + 40^2} \approx 56.57 \text{ A}, \quad \angle I_b = \tan^{-1} \left( \frac{-40}{-40} \right) = 225^\circ \text{ (or } -135^\circ)$$

$$I_c = 40\angle 90^\circ - 40\angle -90^\circ = j40 + j40 = j80 \text{ A} \quad |I_c| = 80 \text{ A}, \quad \angle I_c = 90^\circ$$

### Summary of Results

- Phase Currents:

$$I_{ab} = 40\angle 0^\circ \text{ A}, \quad I_{bc} = 40\angle -90^\circ \text{ A}, \quad I_{ca} = 40\angle 90^\circ \text{ A}$$

- Line Currents:

$$I_a \approx 56.57\angle -45^\circ \text{ A}, \quad I_b \approx 56.57\angle -135^\circ \text{ A}, \quad I_c = 80\angle 90^\circ \text{ A}$$

**2. A three-phase, 4-wire system with a 150V supply has a Y-connected load with the following impedances:  $Z_A=6\angle 0^\circ \Omega$ ,  $Z_B=6\angle 30^\circ \Omega$ ,  $Z_C=5\angle 45^\circ \Omega$ . The phase sequence is CBA. Obtain all line currents and draw a phasor diagram. (10 Marks).**

#### Soln. Given Data:

Voltage (VL): 150V

Phase Sequence: CBA

Load Impedances

$$Z_A = 6\angle 0^\circ \Omega$$

$$Z_B = 6\angle 30^\circ \Omega$$

$$Z_C = 5\angle 45^\circ \Omega$$

#### Calculate the Phase Voltages

The line voltage is given as 150V.

For a Y-connected system:

$$V_{ph} = \frac{V_{line}}{\sqrt{3}} = \frac{150V}{\sqrt{3}} = 86.6V$$

The phase voltages for the CBA sequence are:

$$V_A = 86.6\angle 0^\circ \text{ V}$$

$$V_B = 86.6\angle -120^\circ \text{ V}$$

$$V_C = 86.6\angle 120^\circ \text{ V}$$

#### Calculate the Line Currents

Using Ohm's Law  $I = \frac{V}{Z}$  for each phase:


For Phase A:  $I_A = \frac{V_A}{Z_A} = \frac{86.6\angle 0^\circ}{6\angle 0^\circ} = 14.43\angle 0^\circ A$

For Phase B:  $I_B = \frac{V_B}{Z_B} = \frac{86.6\angle -120^\circ}{6\angle 30^\circ} = 14.43\angle (-120^\circ - 30^\circ) = 14.43\angle -150^\circ A$

For Phase C:  $I_C = \frac{V_C}{Z_C} = \frac{86.6\angle 120^\circ}{5\angle 45^\circ} = 17.32\angle (120^\circ - 45^\circ) = 17.32\angle 75^\circ A$
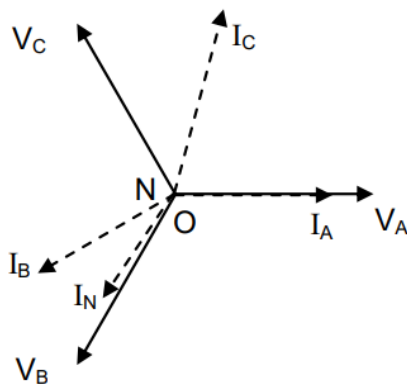
### Draw the Phasor Diagram

- To draw the phasor diagram:
- Start with  $I_A=14.43\angle 0^\circ$  on the positive real axis.
- Draw  $I_B=14.43\angle -150^\circ$ , which will be at 150 degrees counterclockwise from the positive real axis.
- Draw  $I_C=17.32\angle 75^\circ$ , which will be at 75 degrees counterclockwise from the positive real axis.



3. Determine the line current and total power supplied to a delta-connected load with the following impedances:  $Z_{ab}=10\angle 60^\circ \Omega$ ,  $Z_{bc}=20 \Omega \angle 90^\circ$ ,  $Z_{ca}=25\angle 30^\circ \Omega$ . Assume a 3-phase, 400V, ABC system

**Solution:**

#### Determine the Phase Voltages

In a delta-connected system:  $V_L = V_{ph}$   $V_{ph} = V_{line} = 400V$



**Calculate the Phase Currents**

Using Ohm's Law  $I=V/Z$ , we can calculate the phase currents for each impedance.

$$\text{For } Z_{ab}: I_{ab} = \frac{V_{ab}}{Z_{ab}} = \frac{400\angle 0^\circ}{10\angle 60^\circ} = 40\angle -60^\circ \text{ A}$$

$$\text{For } Z_{bc}: I_{bc} = \frac{V_{bc}}{Z_{bc}} = \frac{400\angle -120^\circ}{20\angle 90^\circ} = 20\angle -210^\circ \text{ A}$$

$$\text{For } Z_{ca}: I_{ca} = \frac{V_{ca}}{Z_{ca}} = \frac{400\angle 120^\circ}{25\angle 30^\circ} = 16\angle 90^\circ \text{ A}$$

**Determine the Line Currents**

$$I_a = I_{ab} - I_{ca}$$

$$I_b = I_{bc} - I_{ab}$$

$$I_c = I_{ca} - I_{bc}$$

$$I_a = I_{ab} - I_{ca} = 40\angle -60^\circ - 16\angle 90^\circ$$

$$I_a = 44.49\angle -77.47^\circ \text{ A}$$

$$I_b = I_{bc} - I_{ab} = 20\angle 150^\circ - 40\angle -60^\circ$$

$$I_b = 50.63\angle 154.17^\circ \text{ A}$$

$$I_c = I_{ca} - I_{bc} = 16\angle 90^\circ - 20\angle 150^\circ$$

$$I_c = 21.48\angle 108.43^\circ \text{ A}$$

**Phase-wise Power Calculations:**

$$\text{The power in phase } AB \text{ is: } P_{AB} = \frac{|V_{AB}|^2}{|Z_{AB}|} \cdot \cos(\theta_{AB})$$

$$P_{AB} = \frac{(400)^2}{10} \times \cos(60^\circ) = 16000 \times 0.5 = 8000 \text{ W}$$

$$\text{The power in phase } BC \text{ is: } P_{BC} = \frac{|V_{BC}|^2}{|Z_{BC}|} \cdot \cos(\theta_{BC})$$

$$P_{BC} = \frac{(400)^2}{20} \times 0 = 0 \text{ W}$$

$$\text{The power in phase } CA \text{ is: } P_{CA} = \frac{|V_{CA}|^2}{|Z_{CA}|} \cdot \cos(\theta_{CA})$$

$$P_{CA} = \frac{(400)^2}{25} \times \cos(30^\circ) = 6400 \times \frac{\sqrt{3}}{2} = 5542.5 \text{ W}$$



**Total Power Supplied:**


The total power supplied is the sum of the power in each phase:

$$P_{\text{total}} = P_{AB} + P_{BC} + P_{CA}$$

$$P_{\text{total}} = 8000 + 0 + 5542.5 = 13542.5 \text{ W}$$

The total power supplied to the delta-connected load is **13.5425 kW**.

**4. A 3-phase, 400 V, 4-wire system has a star-connected load with  $Z_A=10\angle 0^\circ \Omega$ ,  $Z_B=(15+j10) \Omega$ ,  $Z_C=(0+j5) \Omega$ . Find the line current and current through the neutral conductor for phase sequence ABC for Fig.**

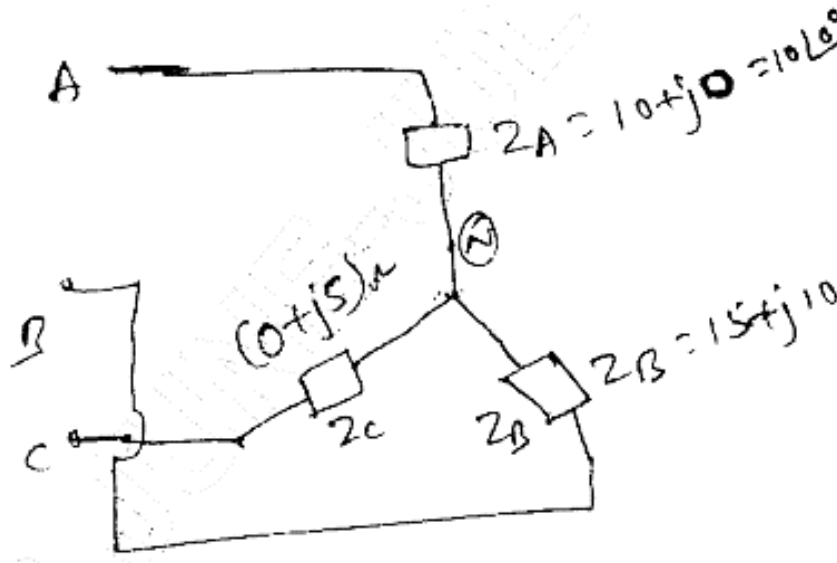**Solution:**

Given:

- $Z_A = 10\angle 0^\circ \Omega$
- $Z_B = 15 + j10 \Omega$
- $Z_C = 0 + j5 \Omega$
- Line-to-neutral voltage  $V_{ph} = \frac{400}{\sqrt{3}} \text{ V}$

**Calculate the Phase Voltages**

The line-to-neutral voltage for a star-connected system is:

$$V_{ph} = \frac{V_{LL}}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 230.94 \text{ V}$$

**Calculate the Phase Currents**

For a star-connected system, the phase current  $I$  in each branch is given by:

$$I = \frac{V_{ph}}{Z}$$

Calculate  $I_A, I_B, I_C$ :

$$I_A = \frac{230.94 \angle 0^\circ}{10 \angle 0^\circ} = 23.094 \angle 0^\circ \text{ A}$$

Given  $Z_B = 15 + j10 \Omega$ , convert to polar form:  $Z_B = 18.03 \angle 33.69^\circ \Omega$

$$I_B = \frac{230.94 \angle -120^\circ}{18.03 \angle 33.69^\circ} = 12.8 \angle -153.69^\circ \text{ A}$$

$Z_C = 0 + j5 \Omega$ , convert to polar form:  $Z_C = 5 \angle 90^\circ \Omega$


$$I_C = \frac{230.94 \angle 120^\circ}{5 \angle 90^\circ} = 46.188 \angle 30^\circ \text{ A}$$

$$I_N = I_A + I_B + I_C$$


$$I_N = 23.094 \angle 0^\circ + 12.8 \angle -153.69^\circ + 46.188 \angle 30^\circ$$

$$I_N = 52.014 + j16.344 \text{ A}$$
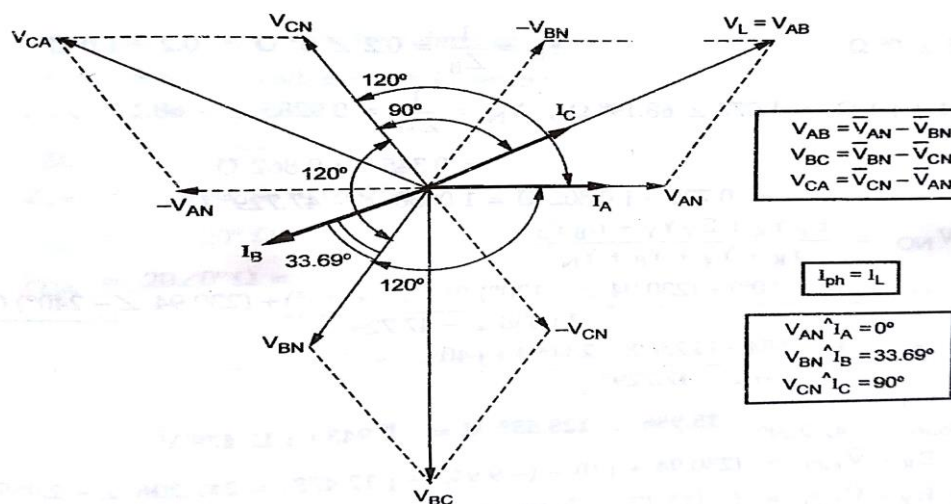
$$I_N = 54.58 \angle 17.55^\circ \text{ A}$$



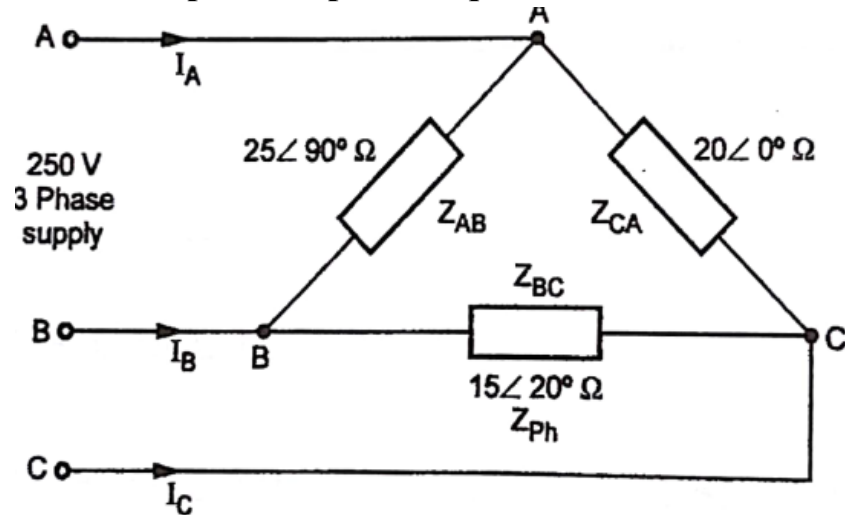5. A 3 phase supply with the line voltage of 250 V has an unbalanced delta connected load as shown in the Fig. Determine line currents, total active and reactive power if phase sequence is ABC.



**Solution:**

$$\bar{V}_{AB} = 250\angle 0^\circ \text{ V} \quad \text{Reference phasor}$$

$$\bar{V}_{BC} = 250\angle -120^\circ \text{ V}$$

$$\bar{V}_{CA} = 250\angle 120^\circ \text{ V}$$

$$Z_{AB} = 25\angle 90^\circ \Omega = 0 + j25 \Omega$$

$$Z_{BC} = 15\angle 20^\circ \Omega = 14.09 + j5.13 \Omega$$

$$Z_{CA} = 20\angle 0^\circ \Omega = 20 + j0 \Omega$$

**Phase currents:**

$$\bar{I}_{AB} = \frac{\bar{V}_{AB}}{Z_{AB}} = \frac{250\angle 0^\circ}{25\angle 90^\circ} = 10\angle -90^\circ \text{ A} = (0 - j10) \text{ A}$$

$$\bar{I}_{BC} = \frac{\bar{V}_{BC}}{Z_{BC}} = \frac{250\angle -120^\circ}{15\angle 20^\circ} = 16.67\angle -140^\circ \text{ A} = (-12.76 - j10.71) \text{ A}$$

$$\bar{I}_{CA} = \frac{\bar{V}_{CA}}{Z_{CA}} = \frac{250\angle 120^\circ}{20\angle 0^\circ} = 12.5\angle 120^\circ \text{ A} = (-6.25 + j10.82) \text{ A}$$

Line currents:

$$\begin{aligned}\bar{I}_A &= \bar{I}_{AB} + \bar{I}_{CA} = (0 - j10) + (-6.25 + j10.82) = -6.25 + j0.82 \\ &= 6.30 \angle 172.52^\circ \text{ A}\end{aligned}$$

$$\begin{aligned}\bar{I}_B &= \bar{I}_{BC} + \bar{I}_{AB} = (-12.76 - j10.71) + (0 - j10) = -12.76 - j20.71 \\ &= 24.32 \angle -121.63^\circ \text{ A}\end{aligned}$$


$$\begin{aligned}\bar{I}_C &= \bar{I}_{CA} + \bar{I}_{BC} = (-6.25 + j10.82) + (-12.76 - j10.71) = -19.01 + j0.11 \\ &= 19.01 \angle 179.66^\circ \text{ A}\end{aligned}$$

$$\begin{aligned}\text{Total active power} &= V_{AB} \cdot I_{AB} \cos(V_{AB} \angle I_{AB}) \\ &\quad + V_{BC} \cdot I_{BC} \cos(V_{BC} \angle I_{BC}) \\ &\quad + V_{CA} \cdot I_{CA} \cos(V_{CA} \angle I_{CA})\end{aligned}$$

$$\begin{aligned}&= (250)(10) \cos(+90^\circ) + (250)(16.67) \cos(+20^\circ) \\ &\quad + (250)(12.5) \cos(0^\circ) = 0 + 3916.16 + 3125 \\ &= 7041.16 \text{ W} = 7.04 \text{ kW}\end{aligned}$$

$$\begin{aligned}\text{Total reactive power} &= V_{AB} \cdot I_{AB} \sin(V_{AB} \angle I_{AB}) \\ &\quad + V_{BC} \cdot I_{BC} \sin(V_{BC} \angle I_{BC}) \\ &\quad + V_{CA} \cdot I_{CA} \sin(V_{CA} \angle I_{CA})\end{aligned}$$
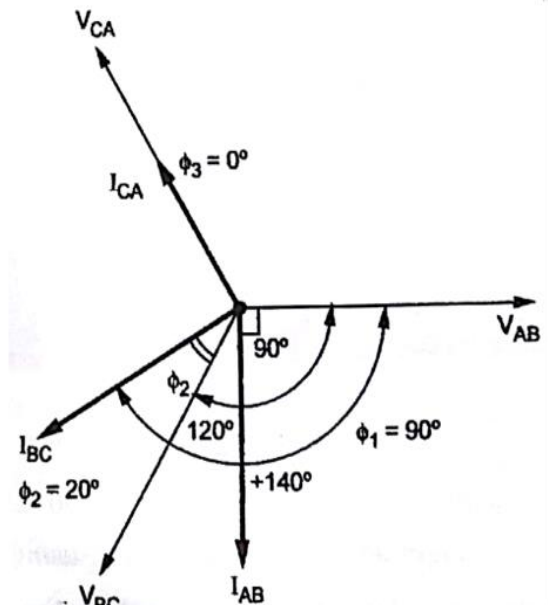
$$\begin{aligned}&= (250)(10) \sin(+90^\circ) + (250)(16.67) \sin(20^\circ) + (250)(12.5) \sin(0^\circ) \\ &= 2500 + 1425.36 \\ &= 3925.36 \text{ VAR} = 3.925 \text{ kVAR}\end{aligned}$$



6. A 3 phase 4-wire CBA system of phase sequence, with effective line voltage of 100 V has a star - connected impedances given by :  $Z_A = 3 \angle 0^\circ \Omega$ ,  $Z_B = 4.5 \angle 56.31^\circ \Omega$ ,  $Z_C = 2.24 \angle 26.57^\circ \Omega$ . Obtain the line currents and current in neutral wire. Draw the phasor diagram.

**Solution :** The given  $V_L = 100 \text{ V}$  and star connection.

$$|V_{ph}| = \frac{V_L}{\sqrt{3}} = \frac{100}{\sqrt{3}} = 57.7350 \text{ V}$$

The phase sequence is CBA. Let phase voltage  $V_{CN}$  be the reference.

$$\therefore V_{CN} = 57.735 \angle 0^\circ \text{ V}, V_{BN} = 57.735 \angle -120^\circ \text{ V}, V_{AN} = 57.735 \angle +120^\circ \text{ V}$$

$\therefore$  The various phase currents are,

$$I_C = \frac{V_{CN}}{Z_C} = \frac{57.735 \angle 0^\circ}{2.24 \angle -26.57^\circ} = 25.7745 \angle +26.57^\circ = 23.0524 + j11.5286 \text{ A}$$


$$I_B = \frac{V_{BN}}{Z_B} = \frac{57.735 \angle -120^\circ}{4.5 \angle +56.31^\circ} = 12.83 \angle -176.31^\circ = -12.8 - j0.8257 \text{ A}$$

$$I_A = \frac{V_{AN}}{Z_A} = \frac{57.735 \angle +120^\circ}{3 \angle 0^\circ} = 19.245 \angle +120^\circ = -9.6225 + j16.667 \text{ A}$$


For star,  $I_L = I_{ph}$

Hence  $I_C$ ,  $I_B$  and  $I_A$  calculated are the respective line currents.
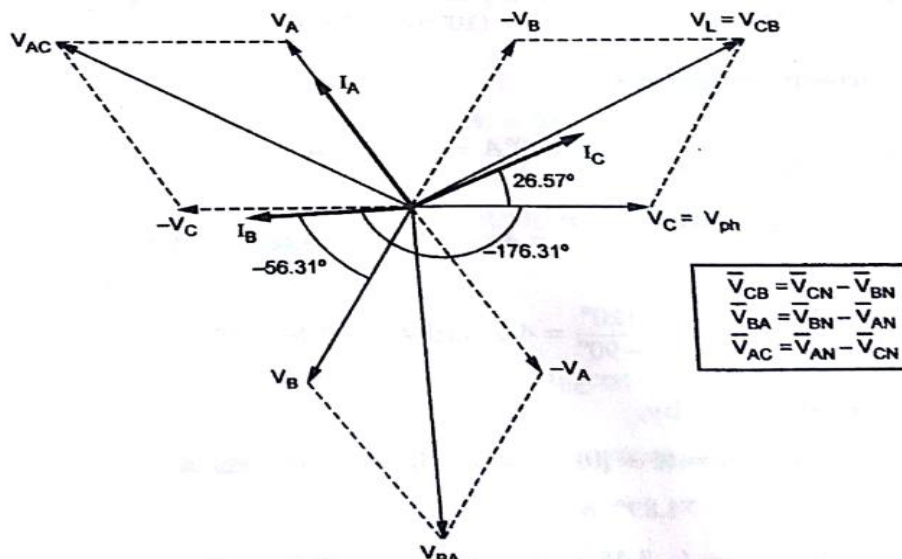
$$\bar{I}_N = \bar{I}_C + \bar{I}_B + \bar{I}_A = 23.0524 + j11.5286 - 12.8 - j0.8257 - 9.6225 + j16.667 \text{ A}$$



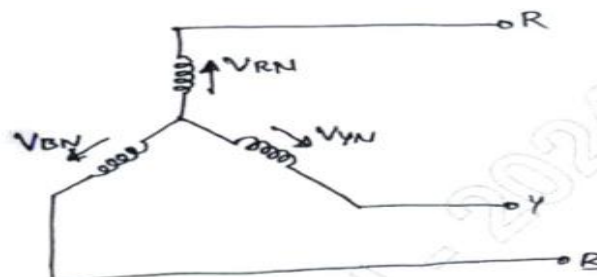7. A symmetrical star-connected system is shown in Fig. Calculate the three-phase line voltage and power given  $V_{RN} = 230 \angle 0^\circ$  Volts. Assume phase sequence is RYB.



Given:

$$V_{RN}=230\angle 0^\circ \text{V}$$

$$V_{YN}=230\angle -120^\circ \text{V}$$

$$V_{BN}=230\angle 120^\circ \text{V}$$

Line Voltage:


$$V_{RY} = \sqrt{3} \times 230\angle 30^\circ = 398.37\angle 30^\circ \text{ V}$$

$$V_{YB} = \sqrt{3} \times 230\angle -90^\circ = 398.37\angle -90^\circ \text{ V}$$

$$V_{BR} = \sqrt{3} \times 230\angle 150^\circ = 398.37\angle 150^\circ \text{ V}$$

Total Power:

$$P = P_{RY} + P_{YB} + P_{BR}$$

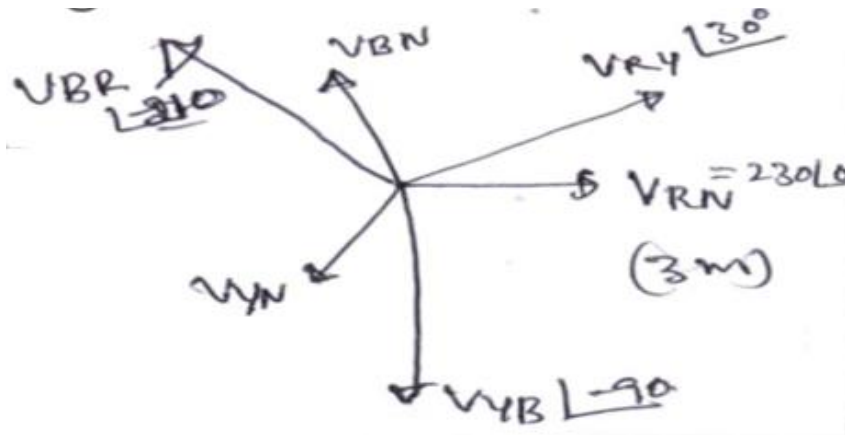

**8. Determine the line currents in an unbalanced star-connected load supplied from a symmetrical 3-phase, 4-wire, 440V system. The branch impedances of the load are:  $Z_A = 5\angle 30^\circ \Omega$ ,  $Z_B = 10\angle 45^\circ \Omega$ ,  $Z_C = 10\angle 60^\circ \Omega$ . The phase sequence is ABC.**

Given:

$$Z_A = 5\angle 30^\circ \Omega, Z_B = 10\angle 45^\circ \Omega, Z_C = 10\angle 60^\circ \Omega$$

$$V_L = 440 \text{ volts}$$

Phase sequence is ABC

$$V_{AN} = \frac{440}{\sqrt{3}}\angle 0^\circ = 254.034\angle 0^\circ \text{ volts}$$

$$V_{BN} = 254.034\angle -120^\circ \text{ volts}, V_{CN} = 254.034\angle 120^\circ \text{ volts}$$



**Phase Currents:**

$$I_A(\text{phase}) = \frac{V_{AN}}{Z_A} = \frac{254.034 \angle 0^\circ}{5 \angle 30^\circ} = 50.81 \angle -30^\circ \text{ A}$$

$$I_B(\text{phase}) = \frac{V_{BN}}{Z_B} = \frac{254.034 \angle -120^\circ}{10 \angle 45^\circ} = 25.4 \angle -165^\circ \text{ A}$$


$$I_C(\text{phase}) = \frac{V_{CN}}{Z_C} = \frac{254.034 \angle 120^\circ}{10 \angle 60^\circ} = 25.4 \angle 60^\circ \text{ A}$$

The line current = phase current.

The line currents are 50.81 A, 25.4 A, and 25.4 A in magnitude.

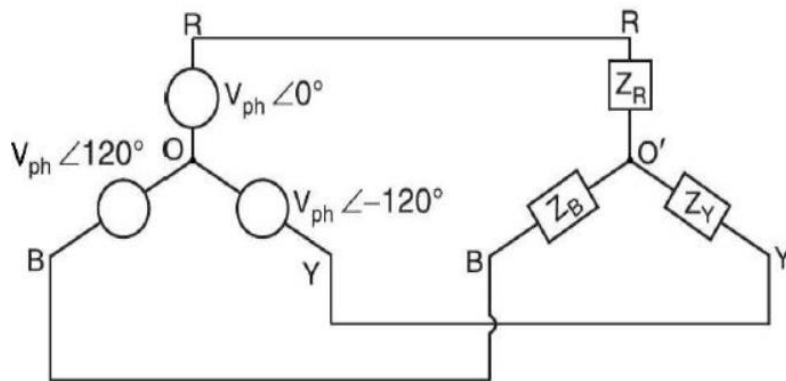**9. Using Millman's theorem, find the phase voltages of a 3-phase, 3-wire unbalanced star-connected load.**

Consider an unbalanced Y load connected to a balanced 3-phase supply as shown



O - star point of the supply (normally at zero potential)

O' -load star point.


Due to load unbalance, the potential of O' is different from that of O.

According to \*Millman's theorem, the voltage  $V_{O'O}$  is given by

$$V_{O'O} = \frac{V_{RO} Y_R + V_{YO} Y_Y + V_{BO} Y_B}{Y_R + Y_Y + Y_B}$$

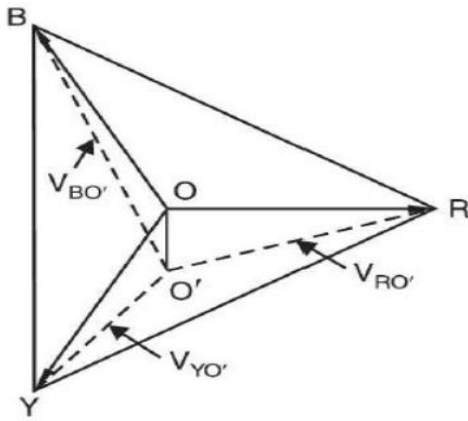where  $V_{RO}$ ,  $V_{YO}$  and  $V_{BO}$  are the phase voltages of the supply and are equal in magnitude but  $120^\circ$  apart in phase. The quantities  $Y_R$ ,  $Y_Y$ , and  $Y_B$  are the admittances of the branches of the unbalanced Y load.





The voltage across load phase R is  $V_{RO'}$ . Using double-subscript notation, this is given by ;

$$\begin{aligned} V_{RO'} &= V_{RO} + V_{OO'} \\ &= V_{RO} - V_{O'O} \end{aligned} \quad \dots$$

Thus load phase voltage  $V_{RO'}$  is obtained by subtracting  $V_{O'O}$  from the supply phase voltage  $V_{RO}$  (phasor difference).

$$\text{Similarly,} \quad V_{YO'} = V_{YO} - V_{O'O} \quad \dots(ii)$$

$$\text{and} \quad V_{BO'} = V_{BO} - V_{O'O} \quad \dots(iii)$$

The line currents in the unbalanced Y load are :

$$I_{RO'} = (V_{RO} - V_{O'O}) Y_R ; \quad I_{YO'} = (V_{YO} - V_{O'O}) Y_Y ; \quad I_{BO'} = (V_{BO} - V_{O'O}) Y_B$$

The point O' is the load star point. Due to load unbalance, O' has some potential w.r.t. O and is shifted away from the centre of the triangle. Such a diagram is very useful in analysing an unbalanced 3-wire star load