

Course – Computer Aided Electrical Drawing
Code- 21EE741


Module-2: SUBSTATION




Prepared by
Maria Sushma S
Asst Professor
EEE


- A substation is a part of an electrical generation, transmission, and distribution system. Substations transform voltage from high to low, or the reverse, or perform any of several other important functions.
- Between the generating station and consumer, electric power may flow through several substations at different voltage levels.
- A substation may include transformers to change voltage levels between high transmission voltages and lower distribution voltages, or at the interconnection of two different transmission voltages.



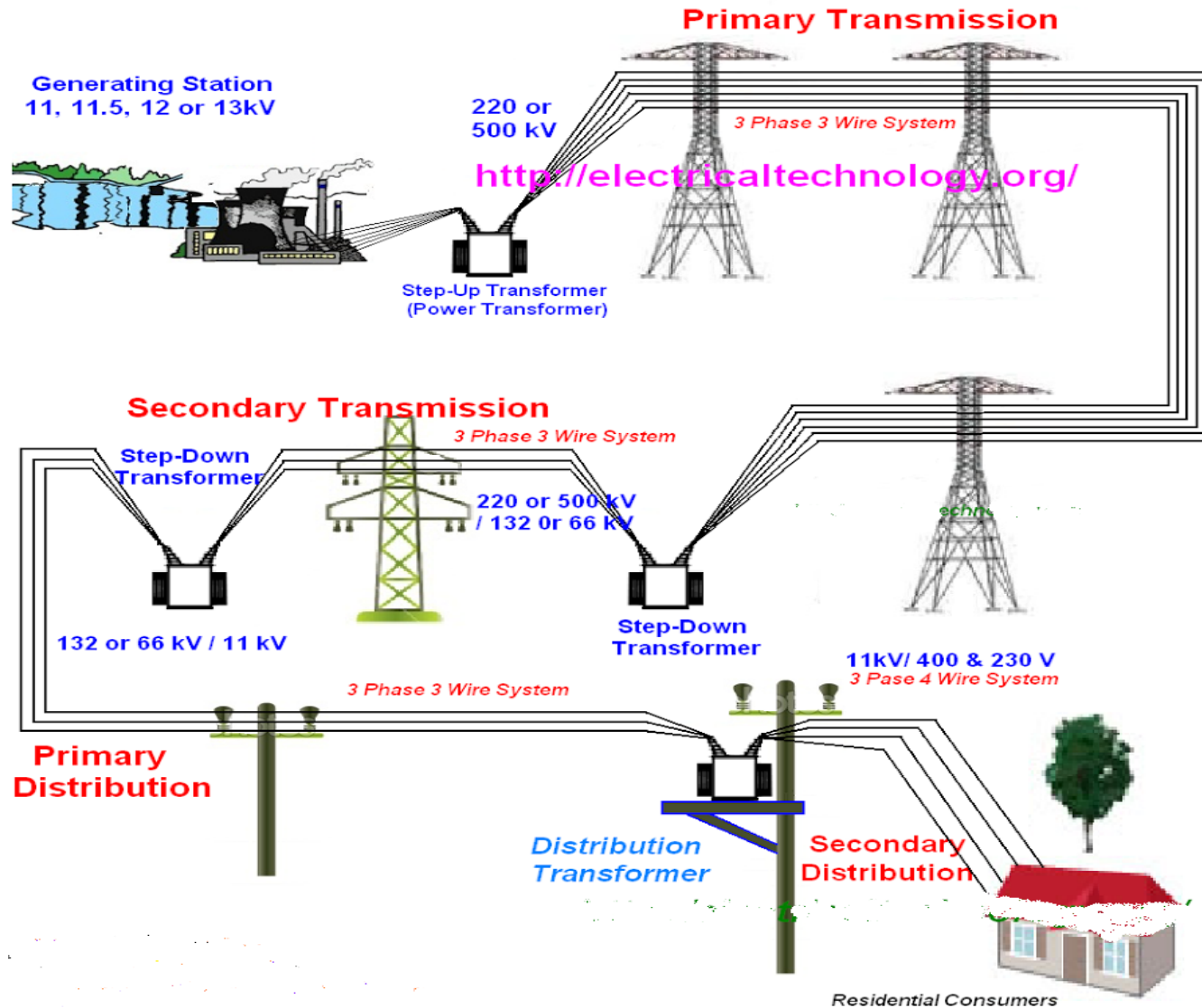


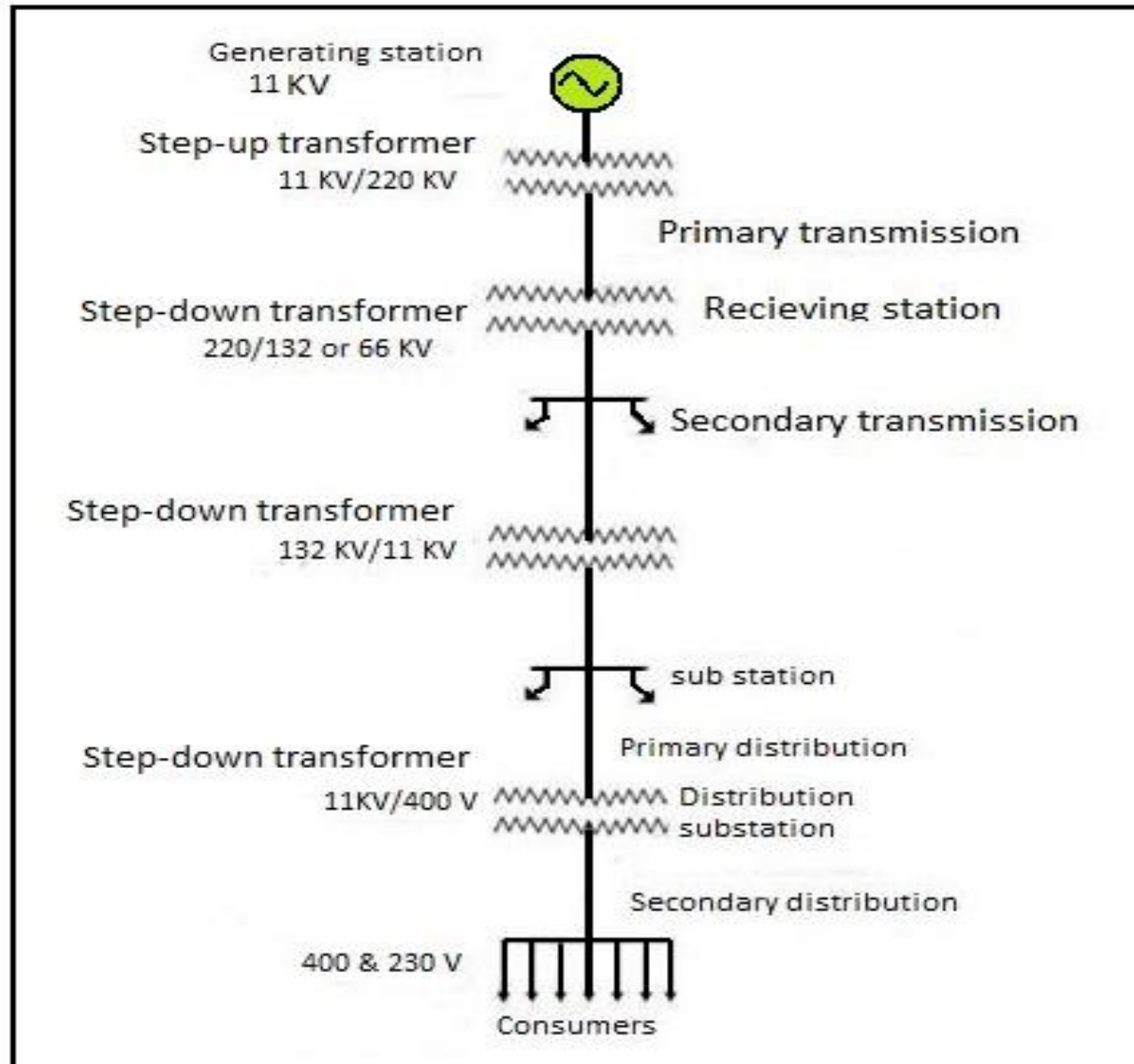


Components of A Sub-Station

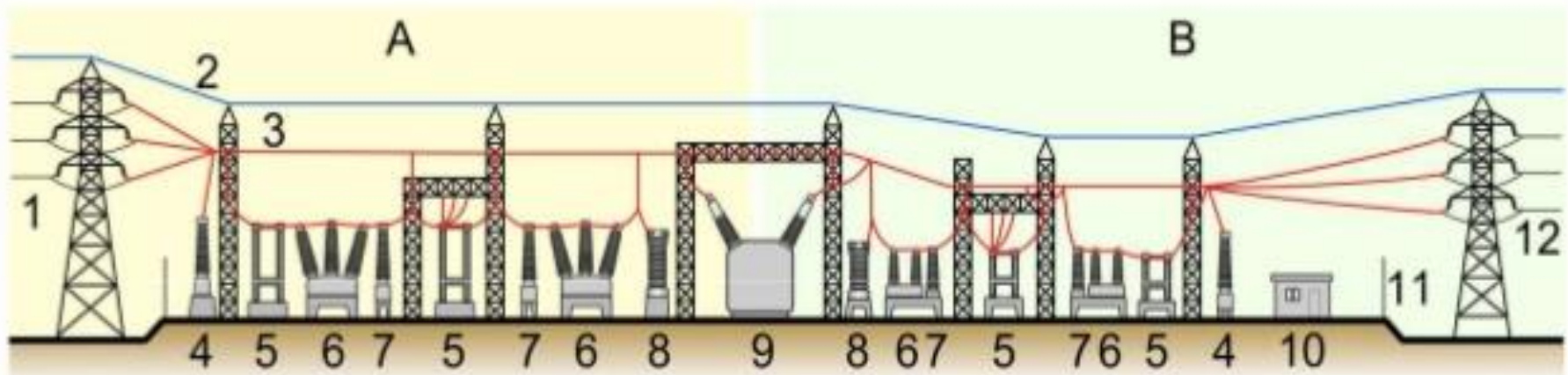

- | | | |
|--|-----------------------|---------------------------|
| 1. Primary power lines | 2. Ground wire | 3. Overhead lines |
| 4. Transformer for measurement of electric voltage | 5. Disconnect switch | 6. Circuit breaker |
| 7. Current transformer | 8. Lightning arrester | 9. Main transformer |
| 10. Control building | 11. Security fence | 12. Secondary power lines |

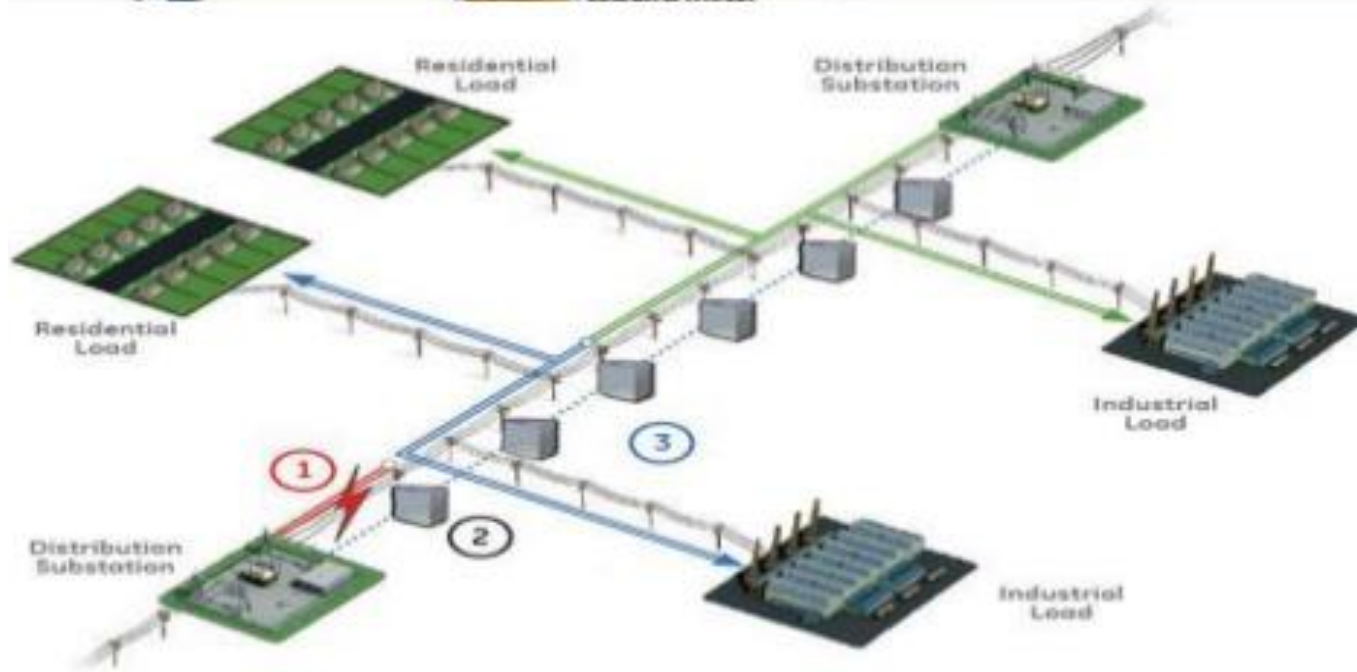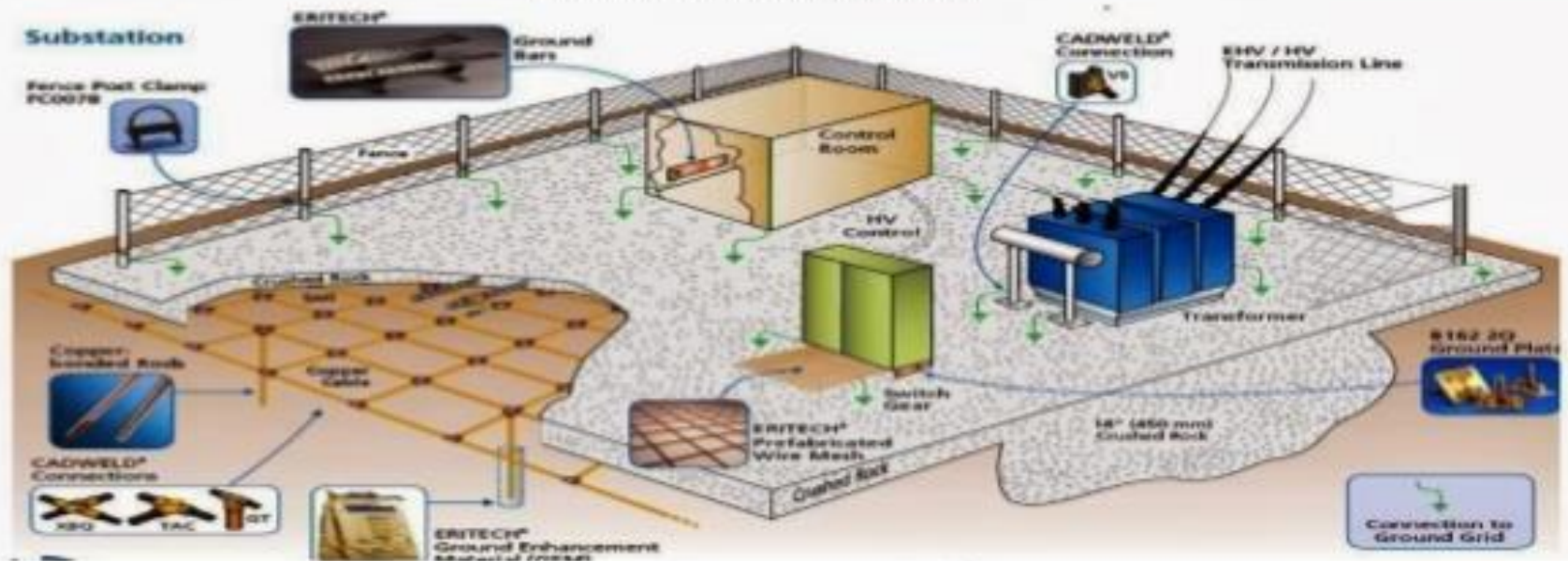Follow Electrical Safety by LAW IEEE80/IEEE998/IEC and National Electric Code



- ① Fault occurs on the line
- ② Local URC Recloser System detects the fault, and isolates the faulted section from the grid
- ③ URCs provide fast system re-configuration to restore power to affected area, via wireless communications

Incoming Subtransmission Lines

Electric power path through substation

Lightning Arresters

Air-break Switches

Outgoing Distribution Lines

Step-down Transformer

Distribution Bus

Cutout
Switches

Oil Circuit Breakers




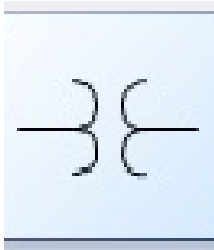
Voltage Regulators





Metal-clad
Switchgear




Control House

7.2 KV out

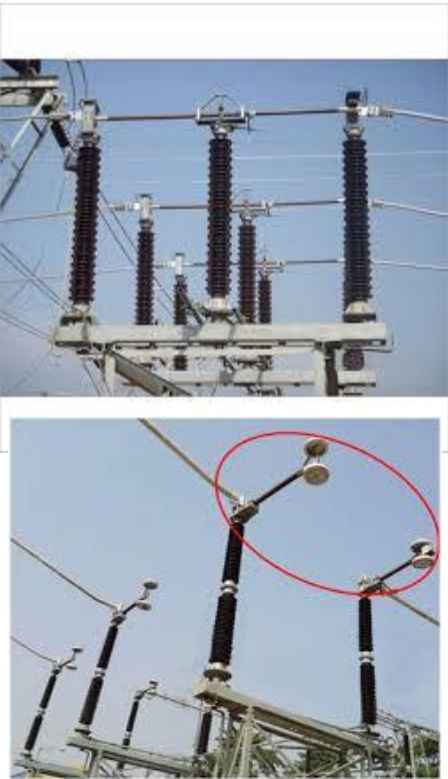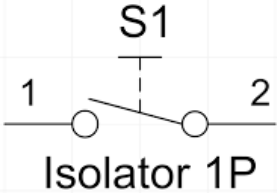

Sl. No	Component Name	Practical Image	Standard Symbol
1	Current Transformer- CT		
2	Potential Transformer- Pt		

Sl. No	Component Name	Practical Image	Standard Symbol
3	Isolator- I		
4	Oil circuit Breaker- OCB		

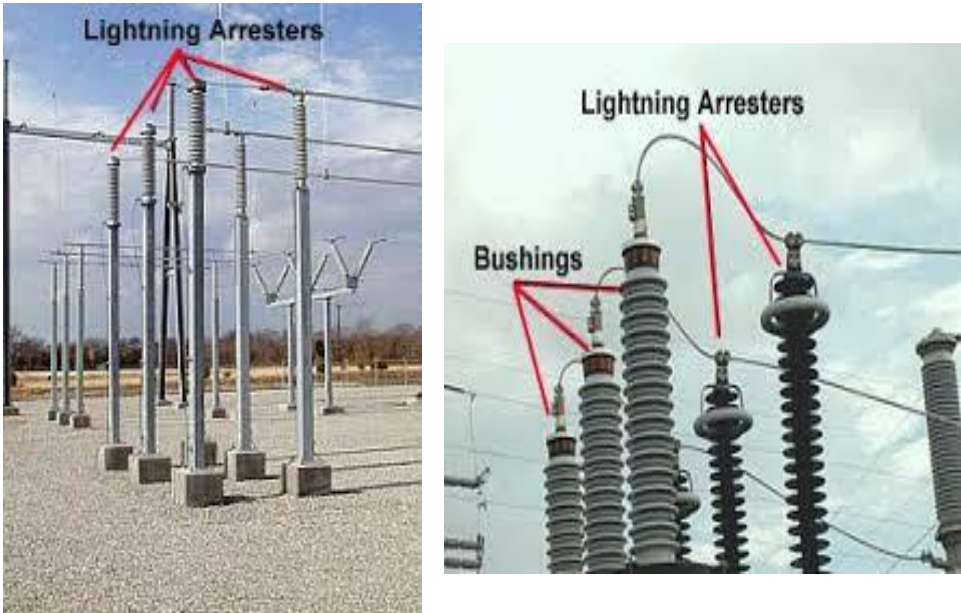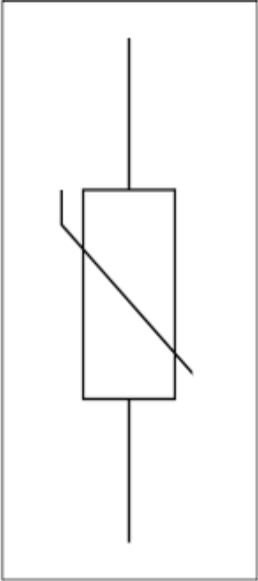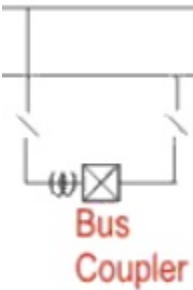Sl. No	Component Name	Practical Image	Standard Symbol
5	Lightning arrester		<p>Fig. 40: Graphic symbol of a varistor</p> 
6	Bus Coupler		

Bus bars


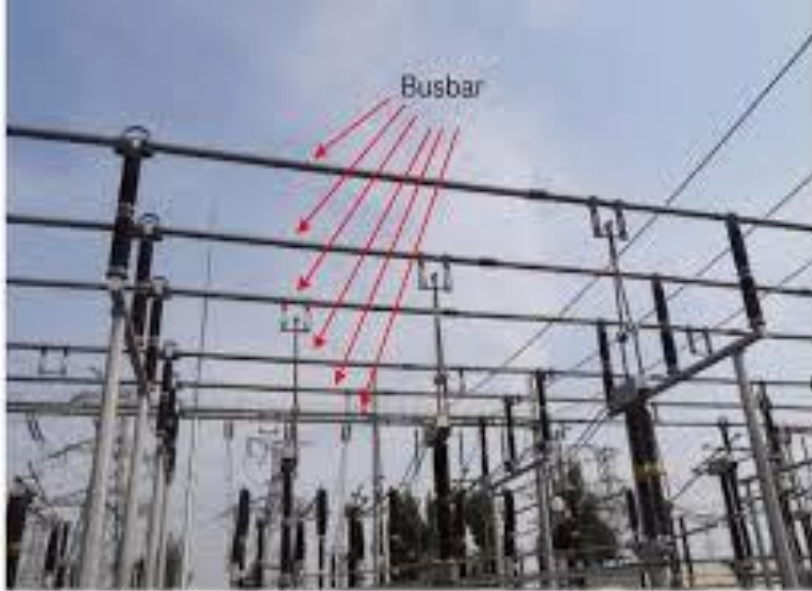


Fig. 1: An image of bus

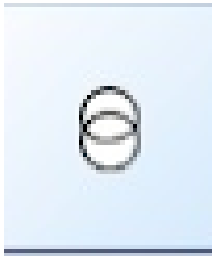
132kv incoming lines through Lightning Arrestor & is connected to the Gantry through insulated discs.



2 winding
transformer



3 winding
transformer

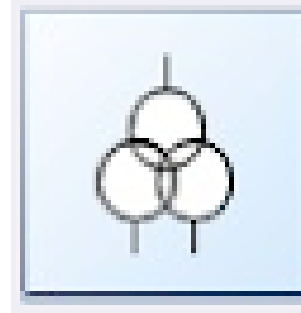

Example : 1

Draw the key diagram or line diagram of a typical 66KV/11KV sub-station. 92/A (NC) 3rd year

Solution Fig. 11.8.

66KV / 11KV. SUB-STATION

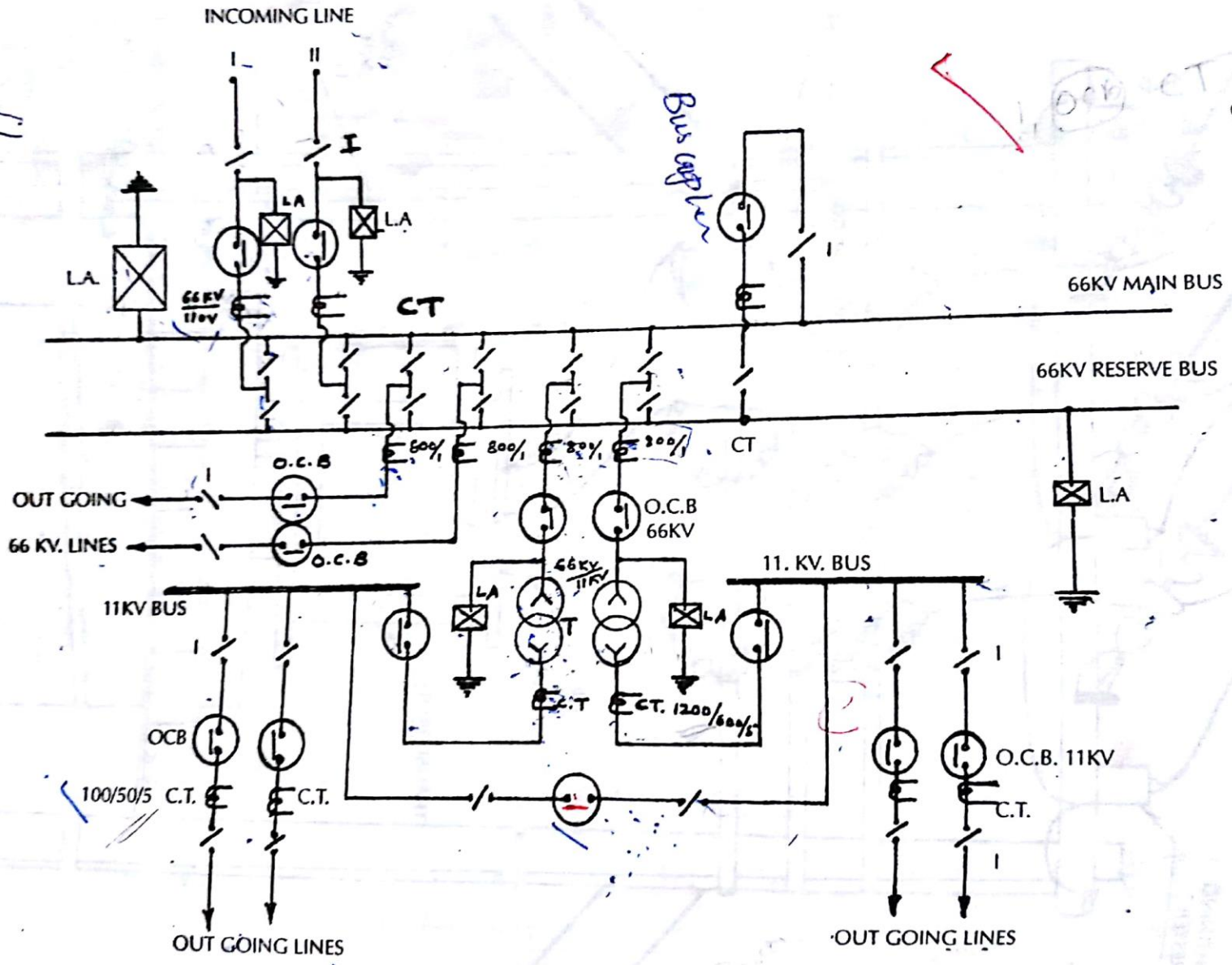


Fig. 11.8

Example : 1

Draw the key diagram or line diagram of a typical 66KV/11KV sub-station. 92/A (NC) 3rd Year.

Solution Fig. 11.8.

66KV / 11KV. SUB-STATION

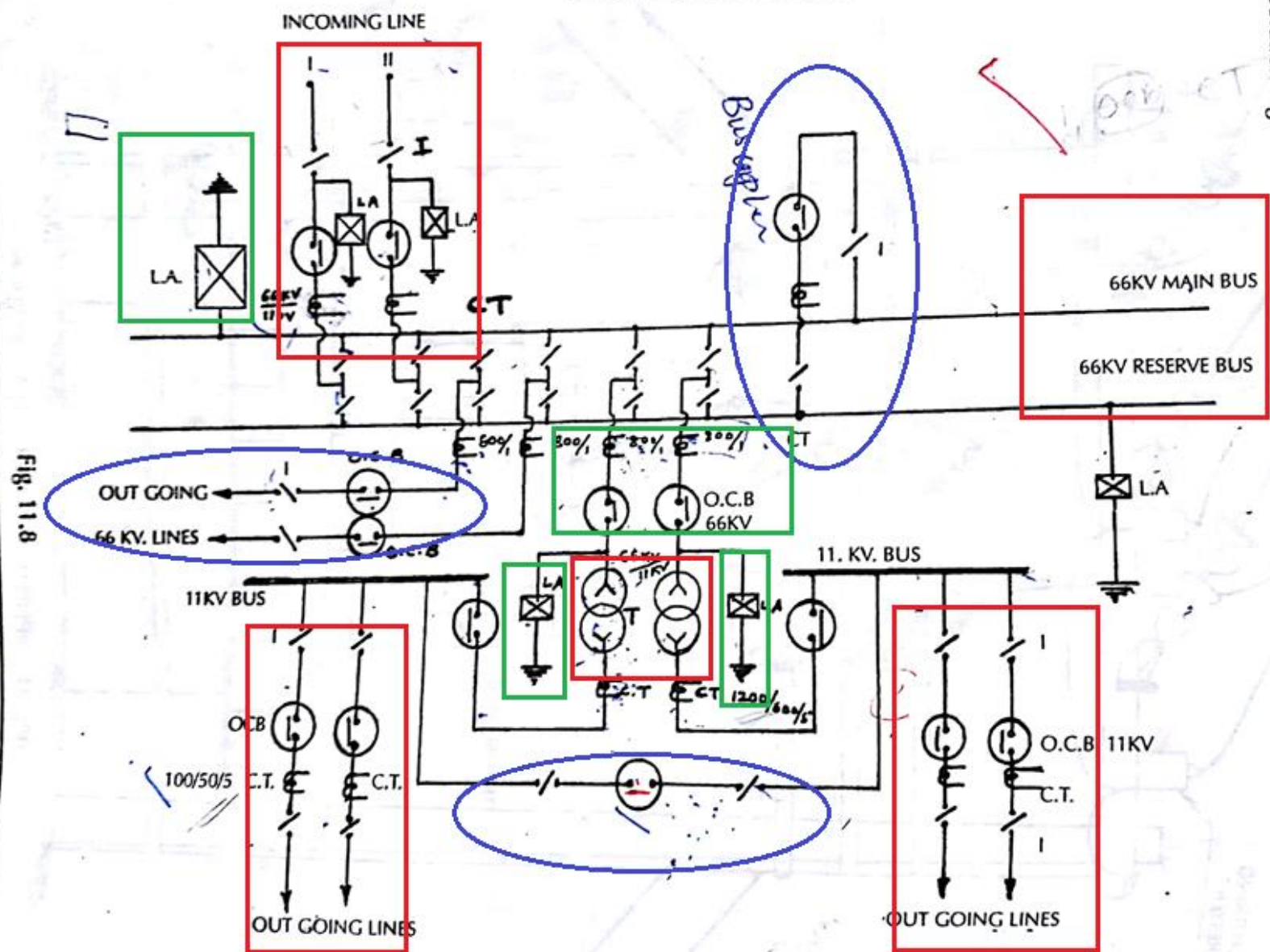


Fig. 11.8

EXAMPLE : 4

8

Draw the single line diagram of a 66/11KV M.U.S.S. with the following details.

1. 66KV, in coming line-2 Nos.
2. Line OCB's 66KV-2 Nos.
3. Step down transformer 66 KV/11KV-2 Nos.
4. OCB's for transformer Bank on L.T. side-2 Nos.
5. Duplicate bus bars for H.T. and L.T. to be provided.
6. Bus coupler for H.T. side only.
7. Feeders, 11KV radiating from L.T. bus 4 Nos.
8. L.T. circuit breakers for feeders- 4 Nos.
9. Position of lightning arresters, isolaters, CT'S and PT'S are to be indicated.

Refer example 1 and 2.

