

AY-2025-26  
Batch: 2022-26

# Power System Analysis-2

## BEE703(IPCC)

*Prepared by*  
*Maria Sushma S*  
*Assistant Professor*  
*Dept of EEE, ATMECE*




## Module-1: Network Topology

1. Introduction
2. Basic definitions of Elementary graph theory
3. Tree, cut-set, loop.
4. Formation of Incidence Matrices.
5. Primitive network-Impedance form and admittance form,
6. Formation of  $Y$  Bus by Singular Transformation.
7.  $Y$  bus by Inspection Method.
8. Illustrative examples.
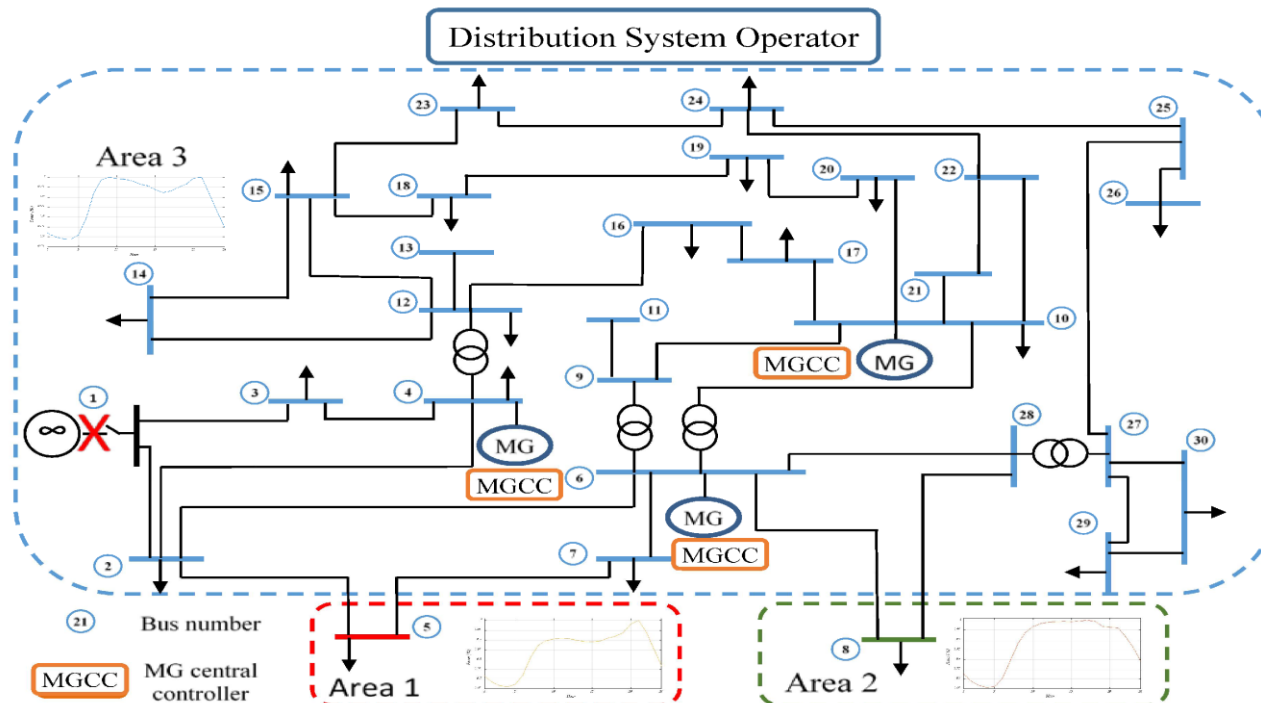
## 1.1 Introduction

- In Power System Analysis–2, we deal with the mathematical modeling and analysis of large electrical power networks
- We represent a complex power system as a network of buses and branches

*Analogy: Google Maps shows a city as a system of roads and junctions.*




*Power Network*
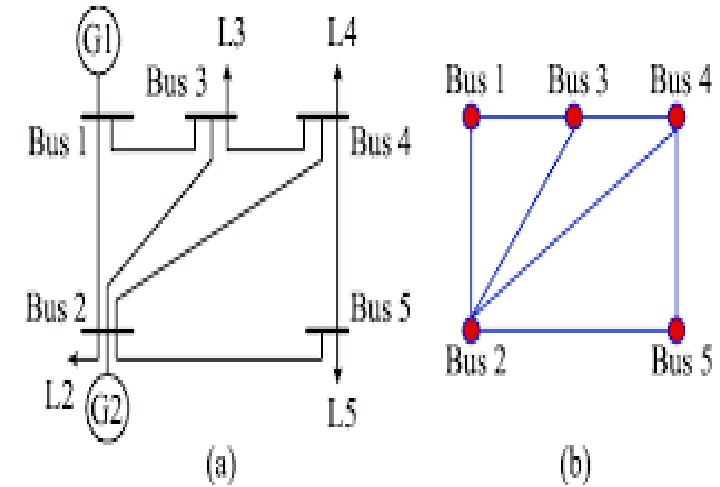
## 1.1 Introduction cntd.

- Practically: Every generating station, transformer substation, and load center in the power grid acts as a **bus (node)**
- Transmission lines or cables - **branches (links)**
- To analyze such systems, we convert physical components like transformers, lines, and loads into mathematical models and use matrix methods like:


- ✓ **Bus Incidence Matrix (A)** – to show how elements connect to buses
- ✓ **Bus Admittance Matrix (Y-bus)** – to understand how currents and voltages flow in the network


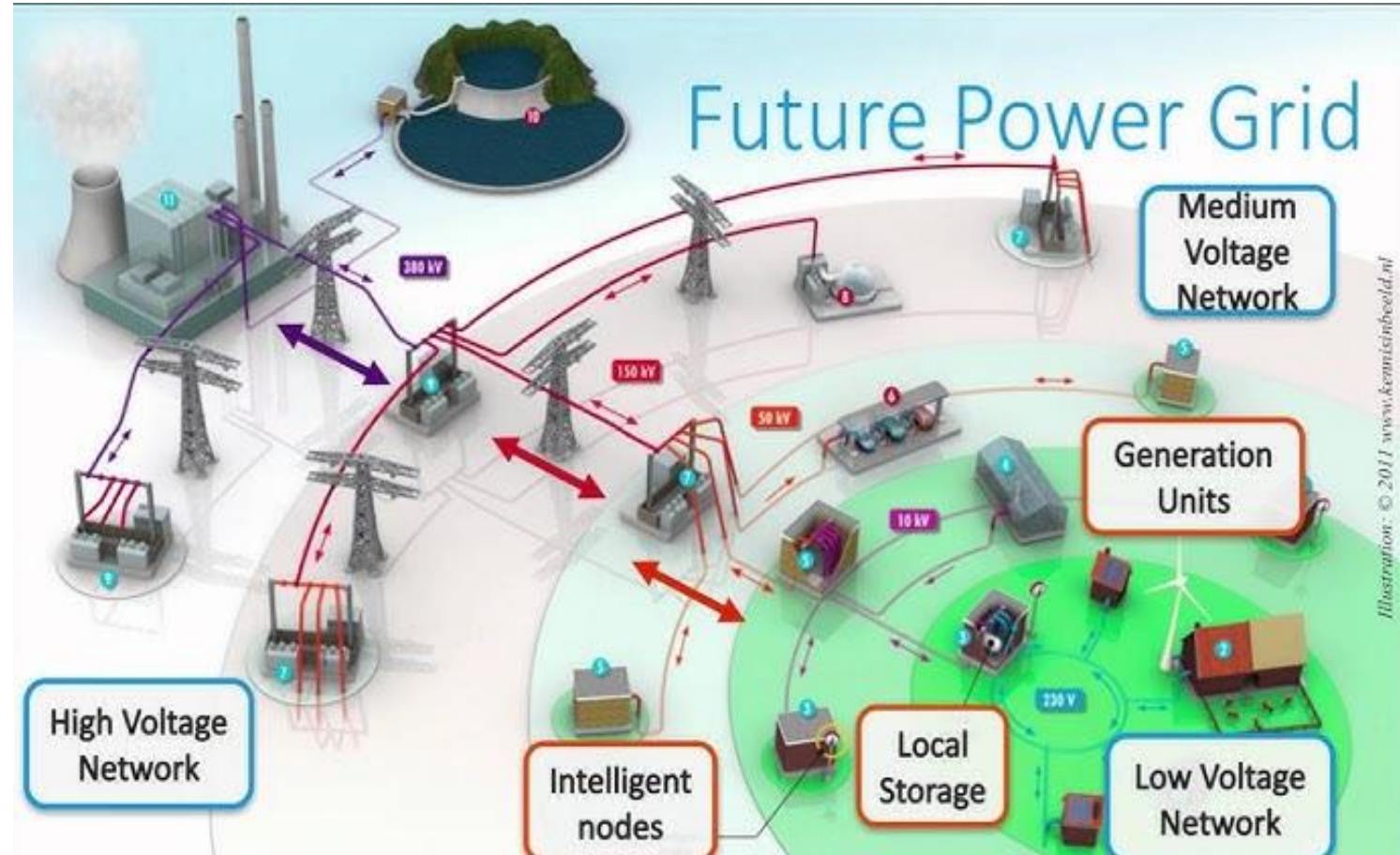
# Why Power System Analysis is important?

This is essential in real life for:

- Power flow studies (what happens when load increases)
- Fault analysis (what happens during short circuits)
- Stability checks (can the grid survive a disturbance?)







- Engineers in control centers monitor & control the power flow using these models.
- During real-time operation, software like SCADA or PSSE (Power System Simulator for Engineers)-uses Y-bus and power flow equations.
- Helps predict overloading and plan upgrades to prevent blackouts.


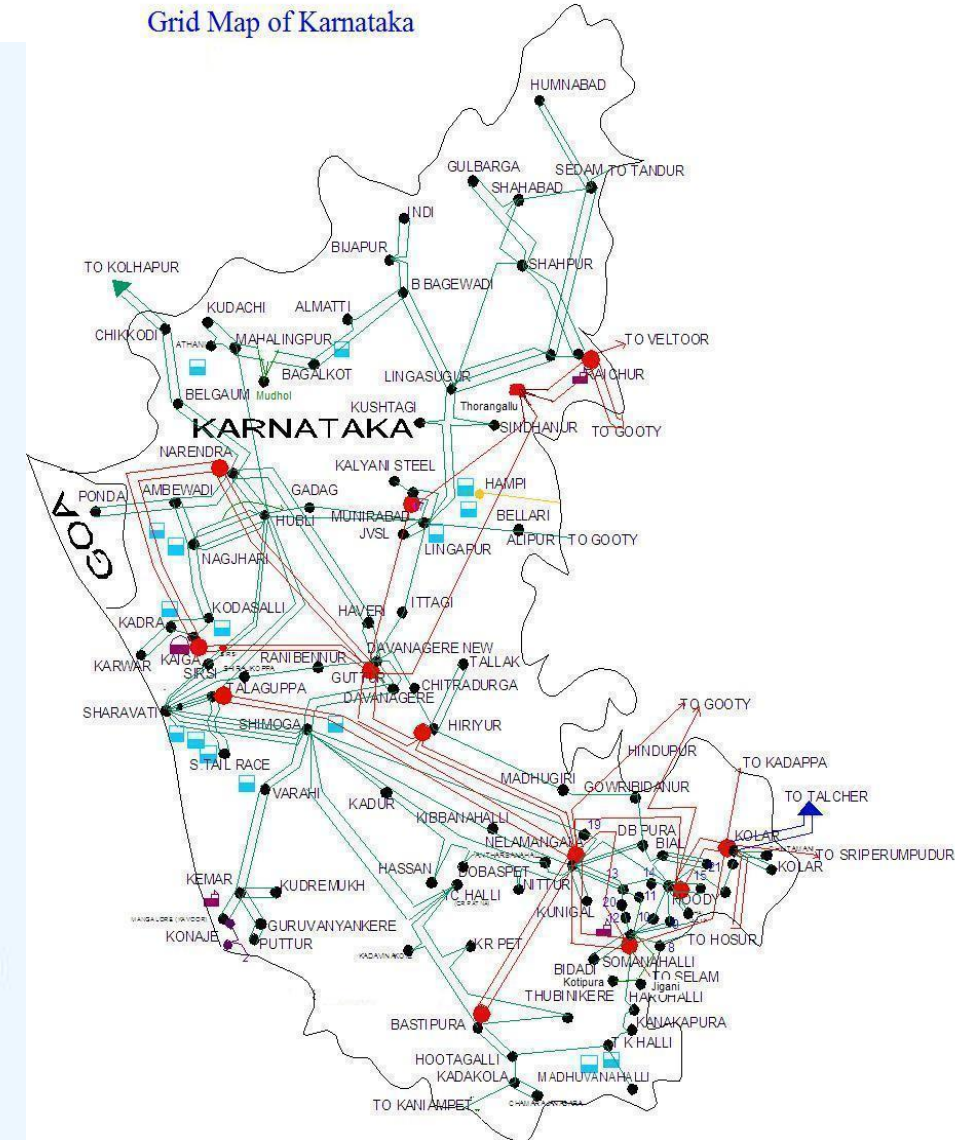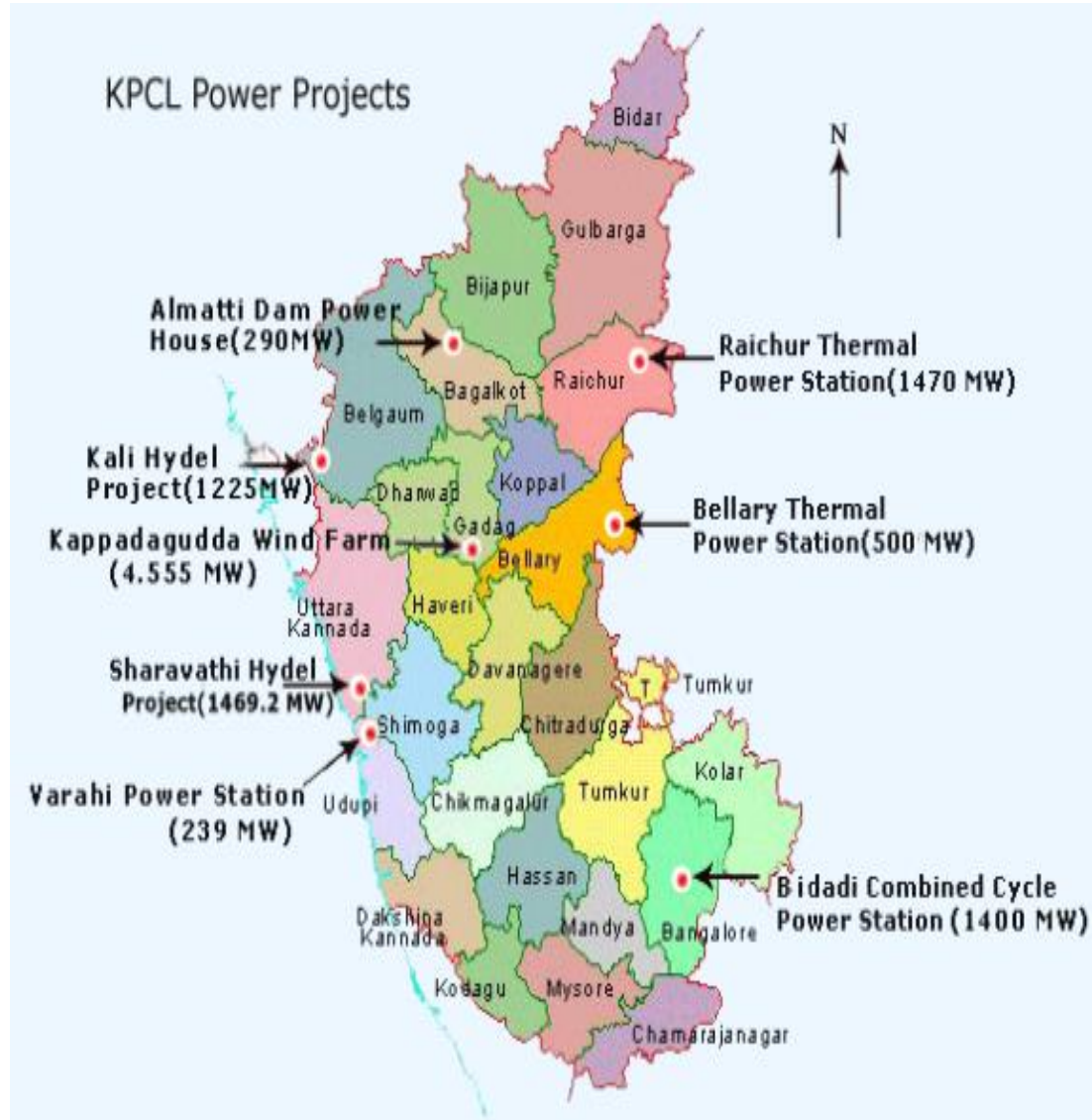
## Real time example

- Imagine Karnataka's grid is receiving power from multiple sources (Sharavathi hydro, Raichur thermal, solar parks).
- Each one is a bus in your system.
- If one line fails, engineers use the Y-bus model to recalculate how power flows through alternate routes — instantly!





## 1.2 Elementary Graph Theory

- Graph:** Geometrical interconnection of elements of a network



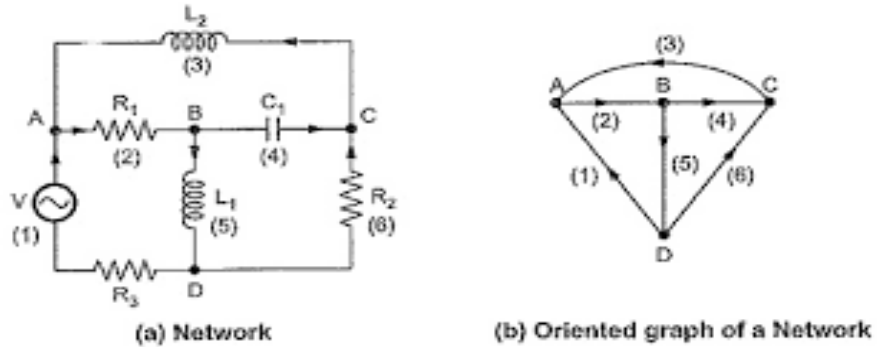


Fig. 5.2 Network and oriented graph

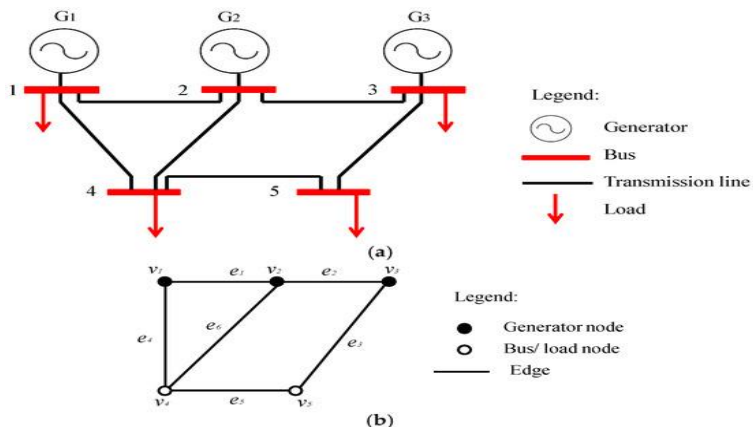

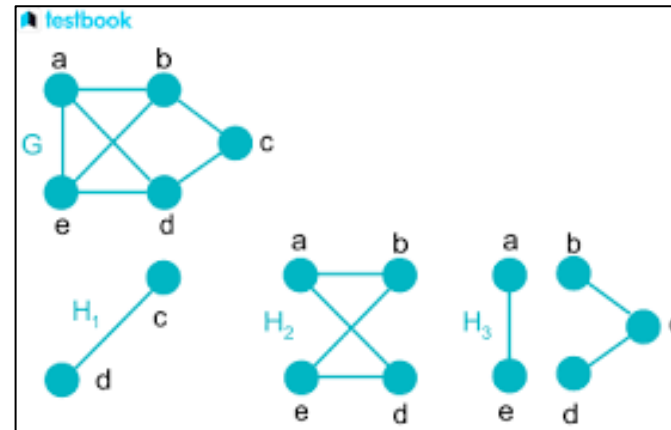- Subgraph:** Smaller part of larger subgraph




- Path:** It is a sequence of lines and nodes that connect two buses without repeating any node.

- Oriented Graph:** If each element of connected graph is assigned with a direction, then it is oriented graph.




# 1.3 Consider the following: 1.


(1) Single line diagram

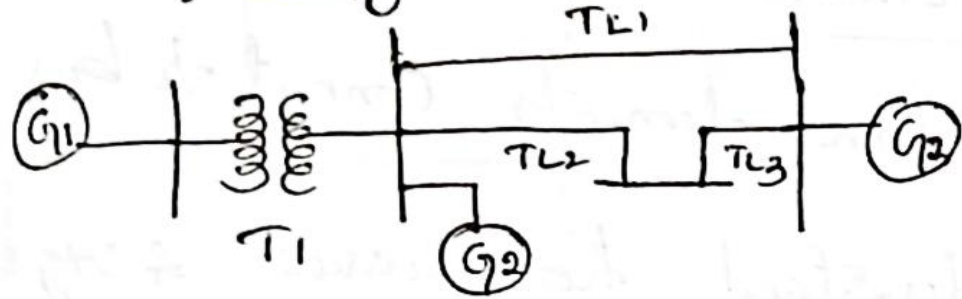

(2) Reactance diagram of fig (1)

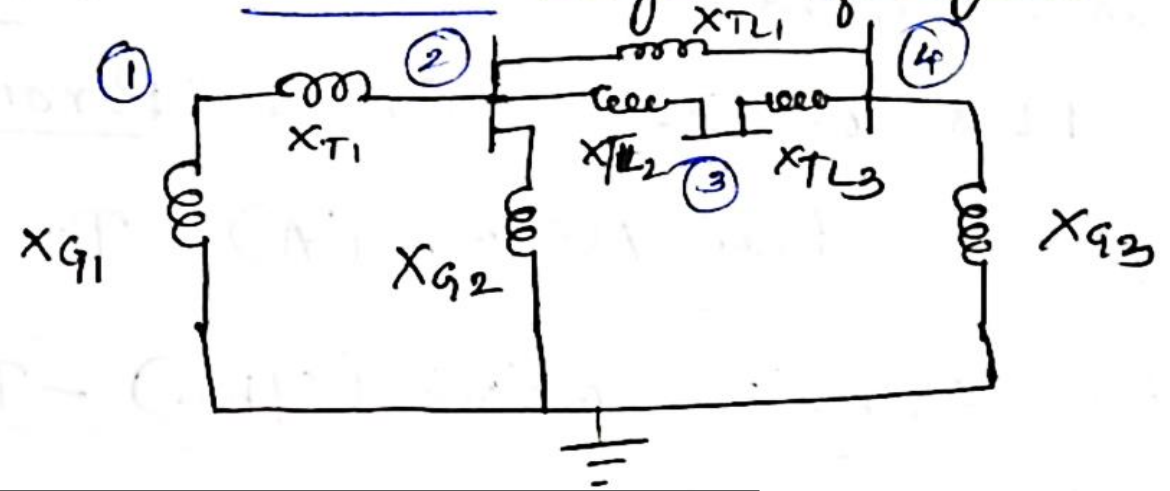

(3) Oriented graph

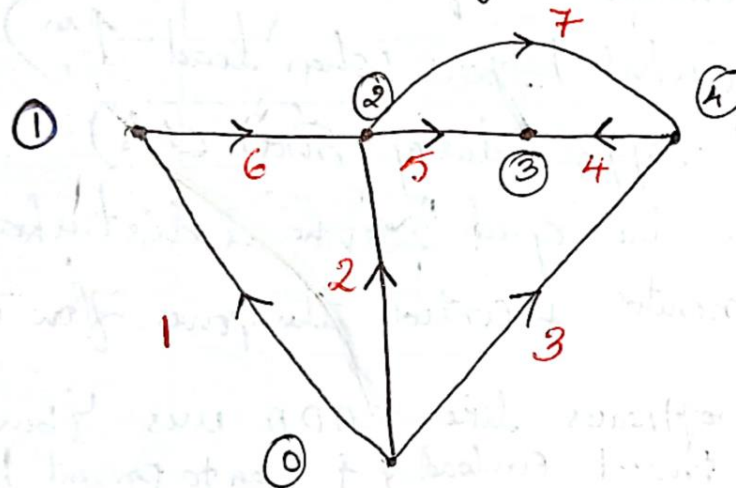

Let,

$n$  - no. of nodes = 5

$e$  - no. of lines or elements = 7

$b$  - no. of branches

$l$  - no. of links

(2)


## 1.4 Tree & Co-tree of the Oriented graph:

\* Tree: A connected subgraph containing all nodes of a graph but no closed path.


\* Branch: The elements of a tree are called branches & form a subset of the elements of the connected graph.

We have  $b = n - 1$  ; where  $n$  - no. of nodes = 5

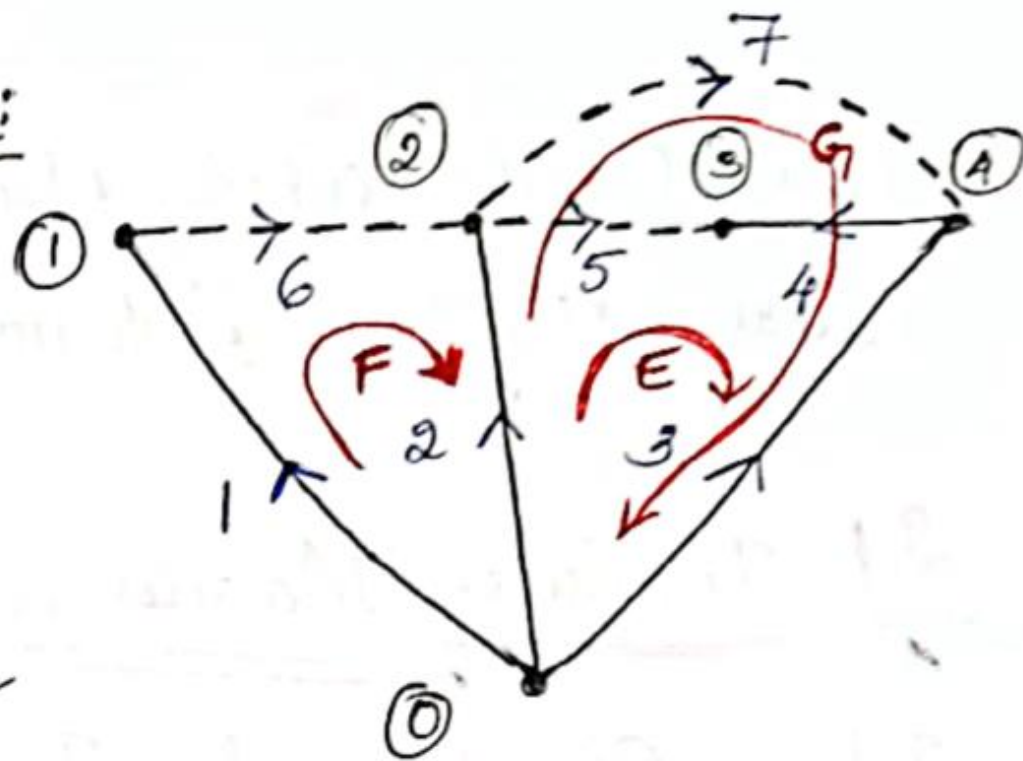$b = 5 - 1 = 4 \Rightarrow$  Branches are 1, 2, 3, 4 (solid lines)



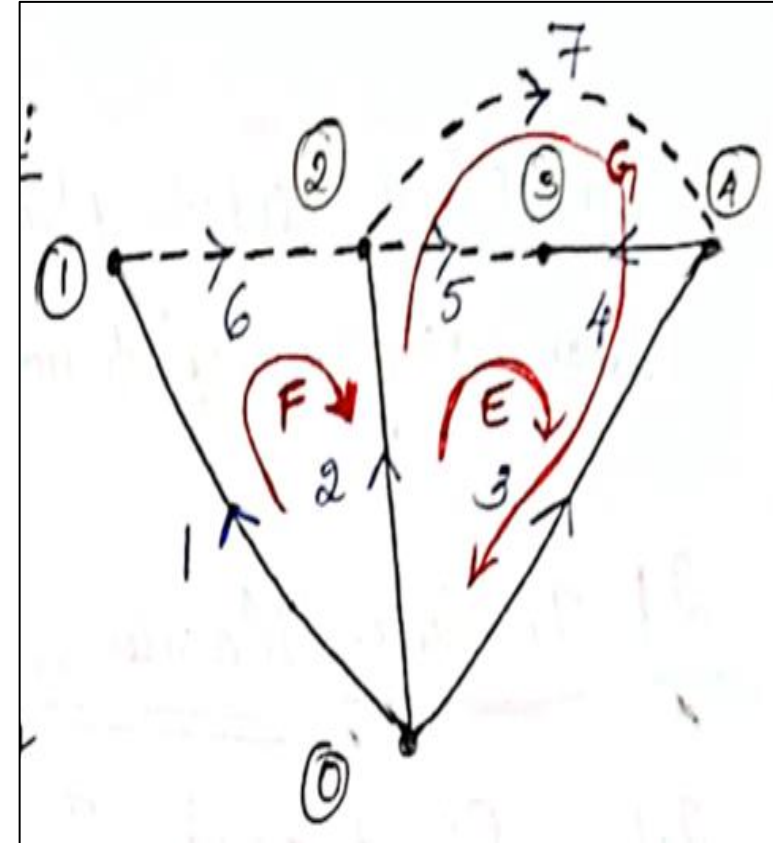\* Links: Those elements of the connected graph that are not included in the tree are called links & forms a subgraph.  
 we have  $l = e - b$  or  $l = e - (n - 1)$  or  $l = e - n + 1$   
 where  $e$  - no. of elements.  
 $\Rightarrow l = 7 - 4 = 3$   
 Links are 5, 6, 7 (dotted lines)



\* Co-tree: It is complement of tree. Links & co-tree are same.

\* Loop: It is a closed path in a graph. It starts & ends at the same node. If a link is added to the tree, the resulting graph contains one closed path.

\* Basic loop: The loops which contain only one link are independent & are called basic loops.

\* No. of loops = No. of links


\* Orientation of a basic loop is chosen - same as that of link



\* Cut-Set: It is a set of elements that, if removed, divides a connected graph into two connected subgraphs.

\* Twig: Elements of a tree are called twigs or tree-branches.

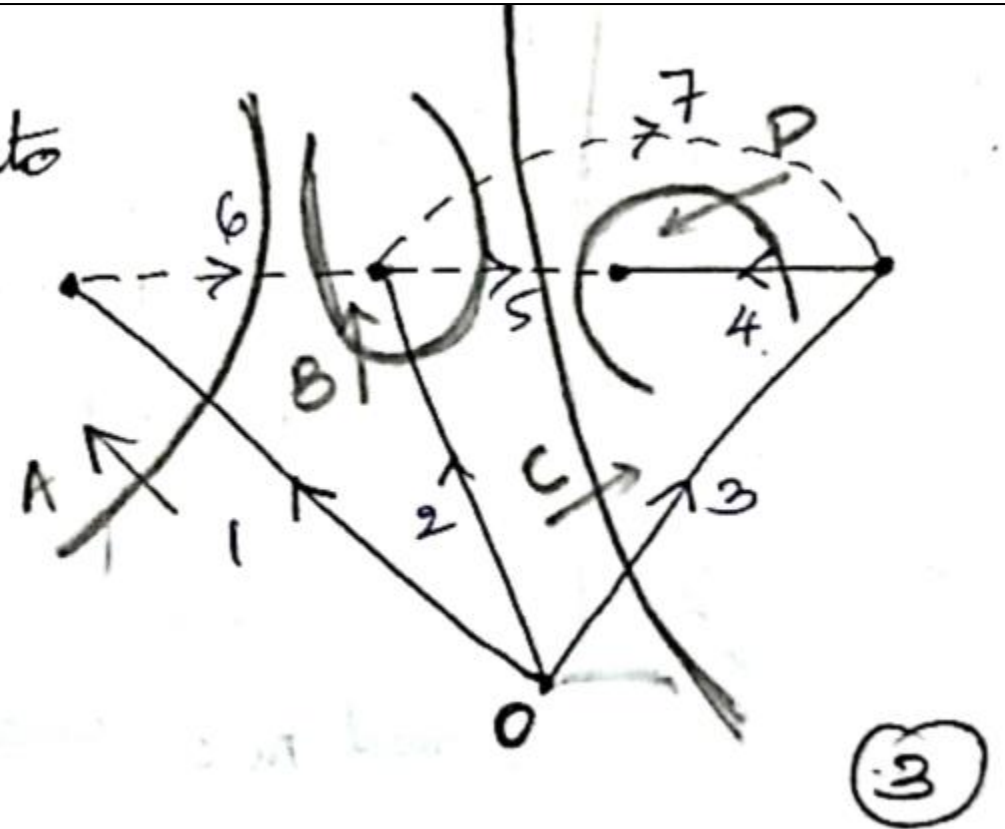Direction of cut-set is same as that of branches



\* Basic Cut set: Cutsets which contain only one twig & remaining links. They are equal to no. of twigs.

## 2. Incidence Matrices:

### 2.1 Element- node Incidence Matrix or Branch node incidence matrix or bus incidence matrix ' $A$ '= $(e \times n)$

\* The incidence of elements to nodes in a connected graph is shown by element-node incidence matrix

\* The elements are obtained as follows.  
e - are placed on rows ; n - are placed on columns in matrix.

$a_{ij} = 1$   $\rightarrow$  If  $i^{\text{th}}$  element is incident to  $j$  oriented away from node

$a_{ij} = -1$   $\rightarrow$  If  $i^{\text{th}}$  element is incident to  $j$  oriented towards the node

$a_{ij} = 0$   $\rightarrow$  If  $i^{\text{th}}$  element is not incident to  $j^{\text{th}}$  node.

\* Dimension of matrix is  $\hat{A} = e \times n$

7

## 2.1 Element- node Incidence Matrix Cntd


\* Dimension of matrix is  $\hat{A} = e \times n$

\*  $\hat{A}$  for oriented graph in 1.3 is

elements  $\downarrow$

$e \backslash n$	Nodes	①	②	③	④
1		1	-1		
2		1		-1	
3		1			-1
4				-1	1
5			1	-1	
6			1	-1	
7				1	-1

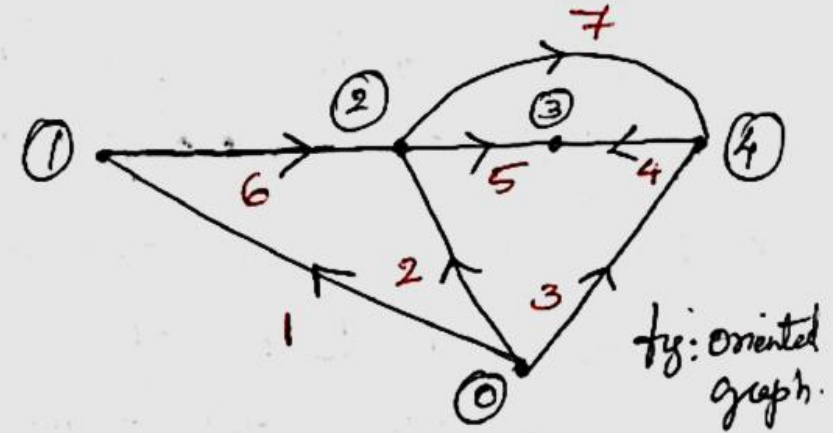Element node incidence matrix -  $\hat{A}$



②

	①	②	③	④
	-1			
	entering			leaving
①	1	-1	0	0
②	1	0	-1	0
③	1	0	0	-1
④	0	0	0	-1
⑤	0	0	1	-1
⑥	0	1	-1	0
⑦	0	0	1	0

④



## 2.1 Bus Incidence Matrix

\* Any nodes of connected graph can be chosen as reference node of the Column corresponding to that node is deleted from  $\hat{A}$ . The matrix so formed is called the Bus-incidence matrix  $A$ .

\* Dimension of  $A = e \times (n-1)$ ; where  $(n-1)$  - rank of matrix.

\* From above example consider the node ⑥ as reference node.

We get matrix  $A$  given by,

$$A = \begin{matrix} & e \backslash n & \text{①} & \text{②} & \text{③} & \text{④} \\ \begin{matrix} i \\ 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \\ 7 \end{matrix} & \begin{bmatrix} -1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 \\ 0 & 1 & -1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & 1 \end{bmatrix} \end{matrix} = \begin{matrix} e \backslash n & \begin{bmatrix} \text{Branch} \\ \text{Link} \end{bmatrix} \\ \begin{matrix} A_b \\ A_l \end{matrix} \end{matrix}$$

\* Above matrix is partitioned into 2 submatrices as shown above:

$$A_b = b \times (n-1)$$

$$A_l = l \times (n-1)$$

## 2.2 Branch- path Incidence matrix ' $k$ ' = ( $b \times \text{paths}$ )

\* The incidence of branches to paths in a tree is shown by the branch-path incidence matrix, where a path is oriented from bus to reference node.

\* Elements of the matrix are:

- $K_{ij} = 1$   $\rightarrow$  If the  $i^{\text{th}}$  branch is in the path from  $j^{\text{th}}$  bus to reference & is oriented in same direction.
- $K_{ij} = -1$   $\rightarrow$  If the  $i^{\text{th}}$  branch is in the path from  $j^{\text{th}}$  bus to reference but oriented in opposite direction.
- $K_{ij} = 0$   $\rightarrow$  If the  $i^{\text{th}}$  branch is not in the path from  $j^{\text{th}}$  bus to reference.


\*  $n = 5$ ,  $b = n - 1 = 5 - 1 = 4$ . Where  $b$  - branch.

\*  $k = b \times \text{path}$ .

## 2.2 Branch- path Incidence matrix 'k' cntd.

$K =$

b \ Path	①	②	③	④
1	-1	0	0	0
2	0	-1	0	0
3	0	0	-1	-1
4	0	0	-1	0

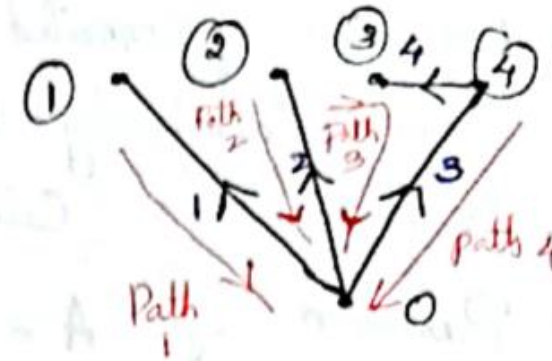

\* Branch-path incidence matrix & Submatrix  $A_b$  relates the branches to paths & branches to buses resp.

$$\therefore A_b \cdot K^T = U$$

$$\therefore K^T = [A_b]^{-1}$$



## 2.3 Basic Cut-set Incidence matrix ' $B'$ '=( $e \times b$ ) cntd.

\* The incidence of elements to basic cut sets of a connected graph is shown by the basic cut-set incidence matrix ' $B$ '.

\* The elements of the matrix are:

$b_{ij} = 1$   $\rightarrow$  If  $i^{\text{th}}$  element is incident to & oriented in the same direction as the  $j^{\text{th}}$  basic cut-set


$b_{ij} = -1$   $\rightarrow$  If  $i^{\text{th}}$  element is incident to & oriented in opposite direction as the  $j^{\text{th}}$  basic cut set

$b_{ij} = 0$   $\rightarrow$  If  $i^{\text{th}}$  element is not incident to  $j^{\text{th}}$  basic cut set

\* Basic cut-set incidence matrix dimension is  $B = e \times b$ .

\* Consider the cut-set graph shown previously.
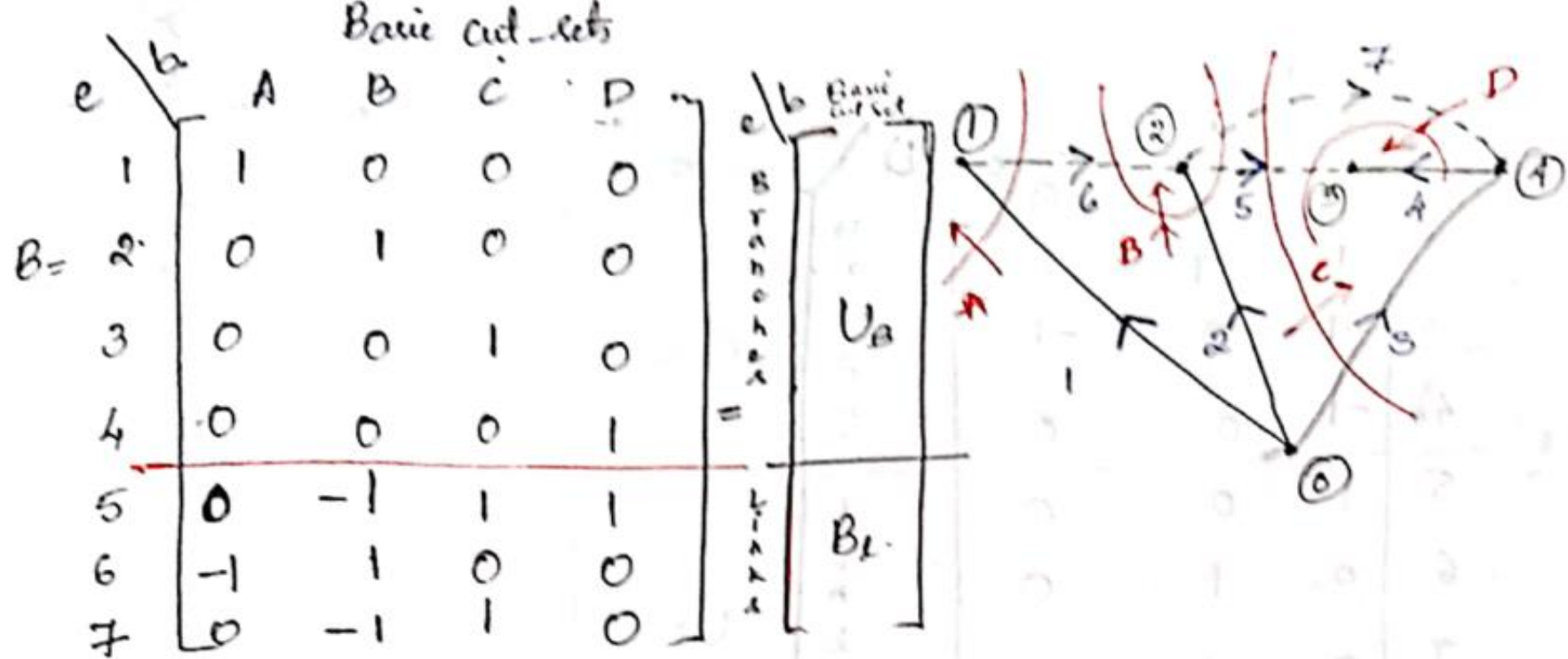
## 2.3 Basic Cut-set Incidence matrix ' $B=(exbc)'$ cntd.



Here  $U_B \rightarrow$  Identity Matrix  $\rightarrow$  Corresponds to branches of cut-sets.

$B_L \rightarrow$  Can be obtained from Bus incidence Matrix as follows.

$$B_L \cdot A_b = A_L$$

$$B_L = A_L \cdot A_b^{-1}$$

$$\text{WKT.} \cdot A_b^{-1} = K^T$$

$$\therefore \boxed{B_L = A_L \cdot K^T} \rightarrow B_L \text{ intensity of Bus incidence matrix.}$$

## 2.3 Basic Loop Incidence matrix '**C**'=(exbl) cntd.

\* The incidence of elements to basic loops of connected graph is shown by basic loop incidence matrix  $C$

\* The elements of the matrix are:

$C_{ij} = 1 \rightarrow$  If the  $i^{\text{th}}$  element is incident to & oriented in the same direction as  $j^{\text{th}}$  basic loop.

$C_{ij} = -1 \rightarrow$  If the  $i^{\text{th}}$  element is incident to & oriented in opposite direction as  $j^{\text{th}}$  basic loop.

$C_{ij} = 0 \rightarrow$  If the  $i^{\text{th}}$  element is not incident to  $j^{\text{th}}$  basic loop.

\* The basic loop incidence matrix dimension is  $C = e \times l$ .



## 2.3 Basic Loop Incidence matrix ' $C$ '=(exbl) cntd.


$$C = \begin{matrix} & \begin{matrix} e \\ l \end{matrix} & \begin{matrix} E \\ F \\ G \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \\ 7 \end{matrix} & \begin{bmatrix} 0 & 1 & 0 \\ 1 & -1 & 1 \\ -1 & 0 & -1 \\ -1 & 0 & 0 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \end{matrix}$$

Basic loops

$$= \begin{matrix} & \begin{matrix} e \\ l \end{matrix} & \begin{matrix} \text{Basic loop} \\ \text{Branches} \\ \text{Links} \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \\ 7 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} \end{matrix}$$

$C_b$

$U_l$

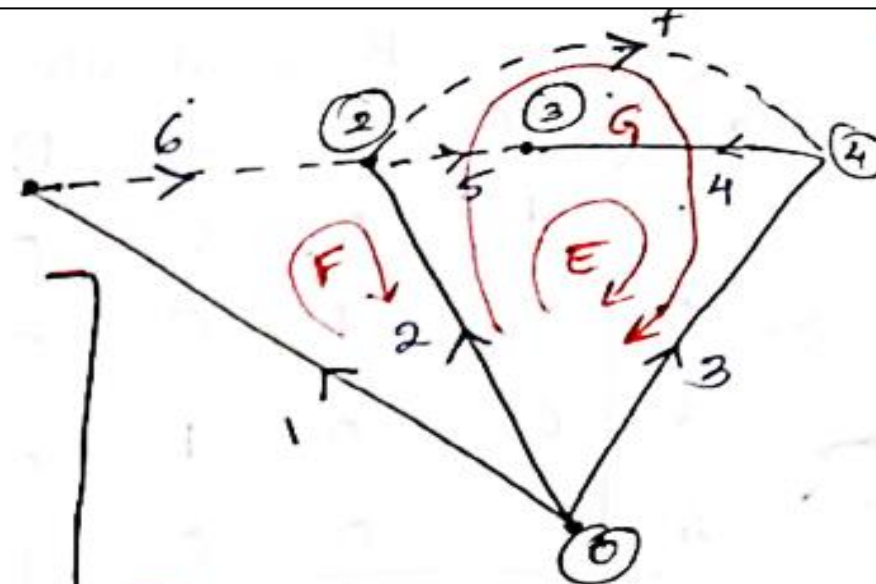

Where  $U_l$  - Identity matrix