

Module - 1 : Network Topology

Syllabus:

- * Introduction & basic definitions of elementary graph theory
- * tree, cut-set, loop.
- * Formation of Incidence Matrices
- * Primitive n/w impedance form & admittance form.
- * Formation of Y bus by Singular Transformation
- * Y bus by Inspection method.
- * Illustrative examples.

1.1 General introduction:

- * In PSA-2 we deal with mathematical modelling & analysis of large electrical power n/w's.
- * M1 - Represents a complex power s/s as a n/w of buses & branches
(Analogy) - Google maps shows a city as a s/s of roads & junctions.
- * Practically - Every generating station, transformer substation & load centre in the power grid acts as - Bus or Node.
TLs or Cables acts as Branches (Links) b/w them
- * Bus Incidence Matrix (A): To show how elements connect to bus.
- * Bus Admittance matrix (Y_{bus}) - To understand how currents & VTs flow in n/w
- * In real life; there are essential due for
 - Power flow studies (what happens when load ↑s)
 - Fault analysis (what happens during short ckt)
 - Stability checks (can the grid survive a disturbance)
- * Engineers in control centres monitor & control the power flow using these Models.
- * During real time operation, softwares like SCADA uses Y_{bus} & power flow eqns which helps to predict & control the power system.

1.2 Elementary Graph Theory:

* Graph: The geometrical interconnection of the various branches is called topology of the n/w. The connection of n/w topology, shown by replacing all physical elements by lines is called Graph.

(or)

A graph shows the geometrical interconnection of the elements of a n/w.

* A subgraph is any subset of elements of the graph.


(or) A subgraph is a smaller part of a larger graph.

* Path: A path is a sequence of lines & nodes that connect ~~two~~ two buses without repeating any node.


* Oriented graph: If each element of connected graph is assigned a direction then it is oriented graph.

1.3 Consider the following:


(1) Single line diagram

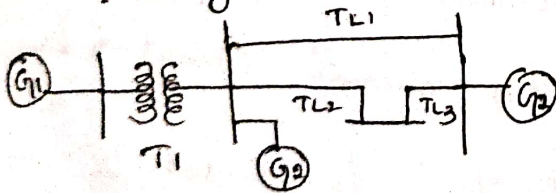

(2) Reactance diagram of fig (1)

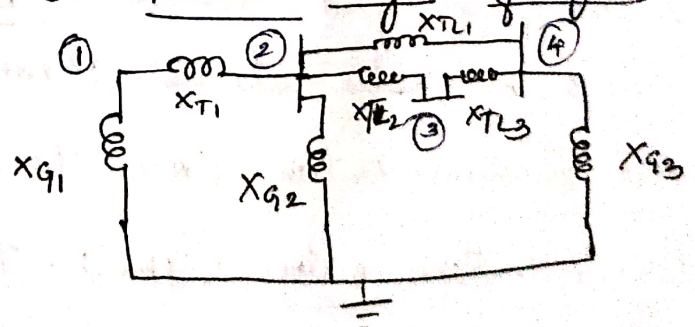

(3) Oriented graph

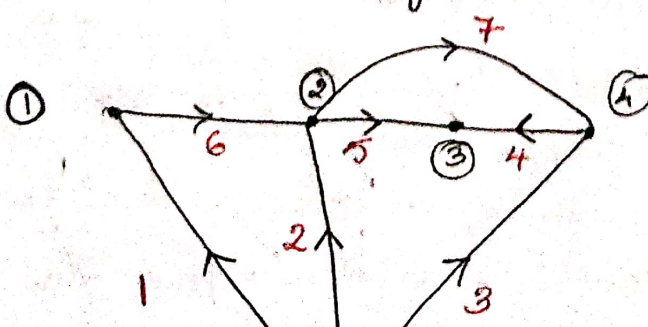

Let,

n - no. of nodes = 5


e - no. of lines or elements = 7

b - no. of branches

l - no. of links



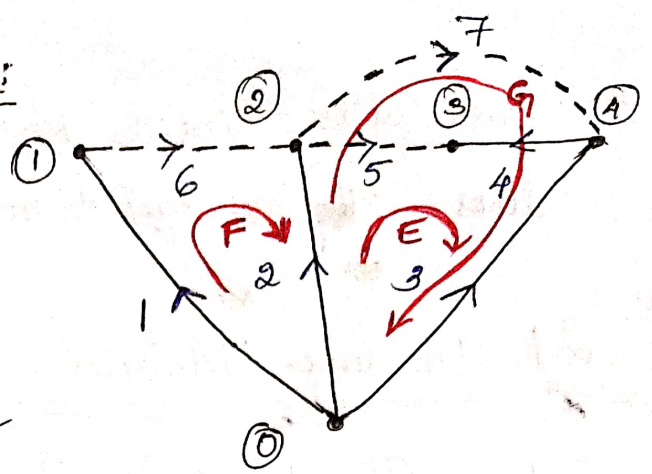1.4 Tree & Co-tree of the Oriented graph:



* Tree: A connected subgraph containing all nodes of a graph but no closed path.

* Branch: The elements of a tree are called branches & form a subset of the elements of the connected graph.

We have $b = n - 1$; where n - no. of nodes = 5

$b = 5 - 1 = 4 \Rightarrow$ Branches are 1, 2, 3, 4 (solid lines)

* Links: Those elements of the connected graph that are not included in the tree are called links & form a subgraph

We have $l = e - b$ or $l = e - (n - 1)$ or $l = e - n + 1$

where e - no. of elements.

$\Rightarrow l = 7 - 4 = 3$

Links are 5, 6, 7 (dotted lines)

* Co-tree: It is complement of tree. Links & co-tree are same.

* Loop: It is a closed path in a graph. It starts & ends at the same node. If a link is added to the tree, the resulting graph contains one closed path.


* Basic loop: The loops which contain only one link are independent & are called basic loops.

* No. of loops = No. of links

* Orientation of a basic loop is chosen - same as that of link

* Cut-Set: It is a set of elements that, if removed, divides a connected graph into two connected subgraphs

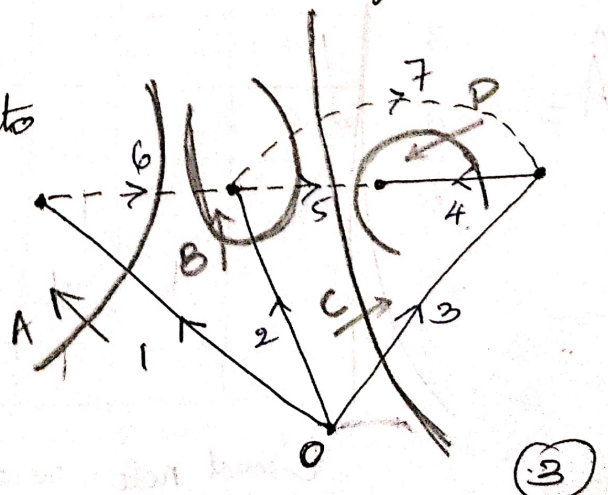* Twig: Elements of a tree are called twigs or tree-branches



- * Basic cut set: cutsets which contain only one twig & spanning links. They are equal to no. of twigs.

2. Incidence Matrices:

2.1 Element - Node Incidence matrix or Branch node incidence matrix or bus incidence matrix $\hat{A} = (e \times n)$

- * The incidence of elements to nodes in a connected graph is shown by element-node incidence matrix

- * The elements are obtained as follows.

e - are placed on rows; n - are placed on columns in matrix.

$a_{ij} = 1 \rightarrow$ If i^{th} element is incident to & oriented away from node

$a_{ij} = -1 \rightarrow$ If i^{th} element is incident to & oriented towards the node.

$a_{ij} = 0 \rightarrow$ If i^{th} element is not incident to j^{th} node.

- * Dimension of matrix is $\hat{A} = e \times n$

- * \hat{A} for for oriented graph in 1.3 is

		Nodes \rightarrow				
elements \downarrow	$e \backslash n$	①	②	③	④	
	1	1	-1			
	2			-1		
	3	1			-1	
	4			-1	1	
	5			1	-1	
	6		1	-1		
	7			1	-1	

Element node incidence matrix - \hat{A}

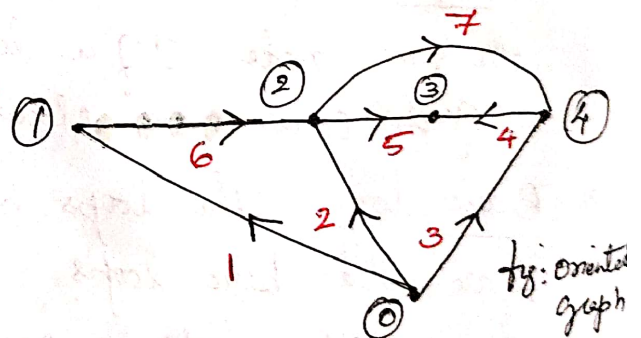


fig: oriented graph

		①	②	③	④	⑤
1 2 3 4 5 6 7	①	-1				
	②		-1			
	③			-1		
	④				-1	
	⑤					-1
	⑥	1	0	0	0	0
	⑦	0	1	0	0	0

* Any nodes of connected graph can be chosen as reference node & the column corresponding to that node is deleted from \hat{A} . The matrix so formed is called the Bus-incidence matrix A .

* Dimension of $A = e \times (n-1)$; where $(n-1)$ - rank of matrix.

* From above example consider the node ⑥ as reference node.

We get matrix A given by,

$$A = \begin{matrix} & \begin{matrix} e \backslash n \end{matrix} & \begin{matrix} ① & ② & ③ & ④ \end{matrix} \\ \begin{matrix} i \\ 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \\ 7 \end{matrix} & \begin{bmatrix} -1 & 0 & 0 & 0 \\ 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & -1 \\ 0 & 0 & -1 & 1 \\ 0 & 1 & -1 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & 1 \end{bmatrix} \end{matrix} = \begin{matrix} & \begin{matrix} e \backslash n \end{matrix} & \\ \begin{matrix} \text{Branches} \\ \text{Links} \end{matrix} & \begin{bmatrix} A_b \\ A_l \end{bmatrix} \end{matrix}$$

* Above matrix is partitioned into 2 submatrices as shown above:

$$A_b = b \times (n-1)$$

$$A_l = l \times (n-1)$$

2.2 Branch-path incidence matrix K

* The incidence of branches to paths in a tree is shown by the branch-path incidence matrix, where a path is oriented from bus to reference node.


* Elements of the matrix are:

- $K_{ij} = 1 \rightarrow$ If the i^{th} branch is in the path from j^{th} bus to reference & is oriented in same direction.
- $K_{ij} = -1 \rightarrow$ If the i^{th} branch is in the path from j^{th} bus to reference but oriented in opposite direction.
- $K_{ij} = 0 \rightarrow$ If the i^{th} branch is not in the path from j^{th} bus to reference.

* $n=5$, $b=n-1=5-1=4$. where b -branch.

⑤

K =	b \ path				
		①	②	③	④
1		-1	0	0	0
2		0	-1	0	0
3		0	0	-1	-1
4		0	0	-1	0

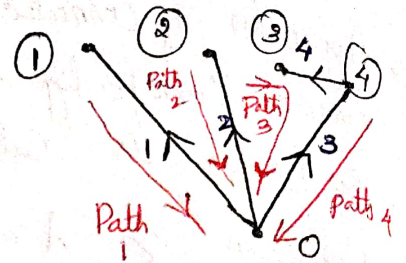

* Branch-path incidence matrix & submatrix A_b relates the branches to paths & branches to buses resp.

$$\therefore A_b \cdot K^T = U$$

$$\therefore K^T = [A_b]^{-1}$$

2.3 Basic Cutset Incidence Matrix 'B'

* The incidence of elements to basic cut sets of a connected graph is shown by the basic cut-set incidence matrix 'B'.

* The elements of the matrix are:


$b_{ij} = 1$ \rightarrow If i^{th} element is incident to & oriented in the same direction as the j^{th} basic cut-set

$b_{ij} = -1$ \rightarrow If i^{th} element is incident to & oriented in opposite direction as the j^{th} basic cut set

$b_{ij} = 0$ \rightarrow If i^{th} element is not incident to j^{th} basic cut set

* Basic cut-set incidence matrix dimension is $B = e \times b$.

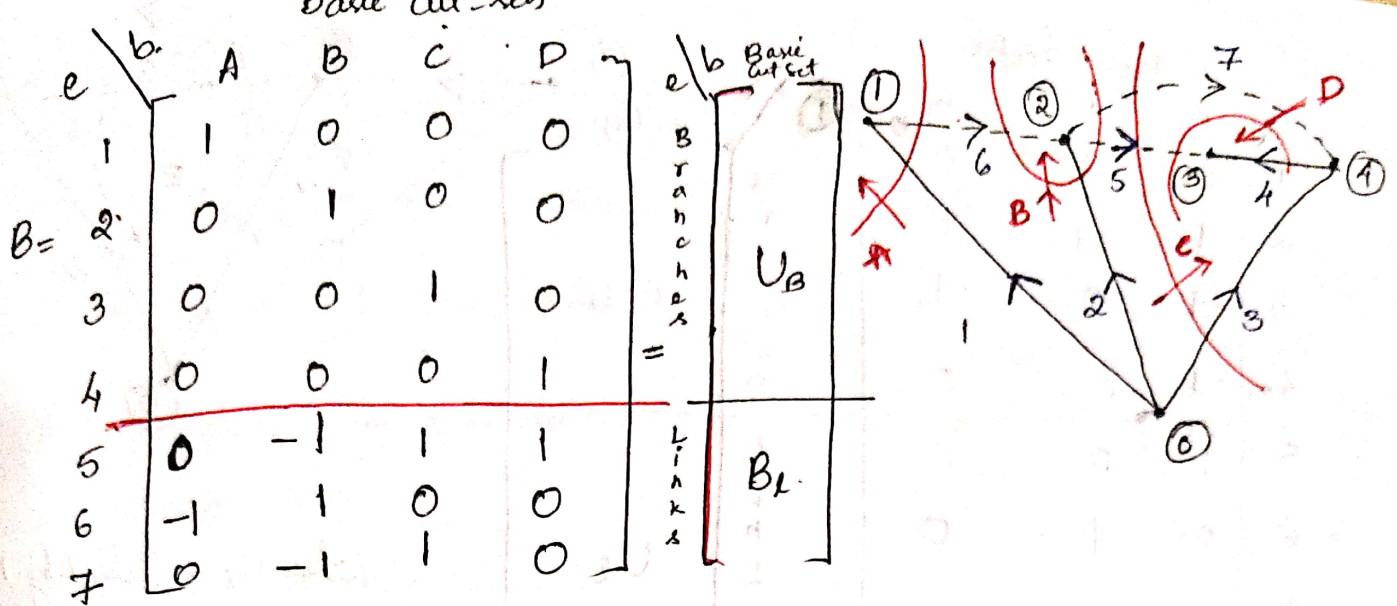* Consider the cut-set graph shown previously.



Here $U_B \rightarrow$ Identity Matrix \rightarrow Corresponds to branches & cut sets.

* $B_L \rightarrow$ Can be obtained from Bus incidence matrix as follows.

$$B_L \cdot A_b = A_L$$

$$B_L = A_L \cdot A_b^{-1}$$

$$\text{WKT: } A_b^{-1} = K^T$$

$$\therefore \boxed{B_L = A_L \cdot K^T} \rightarrow B_L \text{ in terms of Bus incidence matrix.}$$

2.4: Basic loop incidence matrix 'C'

* The incidence of elements to basic loops of connected graph is shown by basic loop incidence matrix C.

* The elements of the matrix are:



$C_{ij} = 1 \rightarrow$ If the i^{th} element is incident to & oriented in the same direction as j^{th} basic loop.

$C_{ij} = -1 \rightarrow$ If the i^{th} element is incident to & oriented in opposite direction as j^{th} basic loop.

$C_{ij} = 0 \rightarrow$ If the i^{th} element is not incident to j^{th} basic loop.

* The basic loop incidence matrix dimension is $C = e \times l$.

	Basic loops	
	E	F
1	0	1
2	1	-1
3	-1	0
4	-1	0
5	1	0
6	0	1
7	0	0

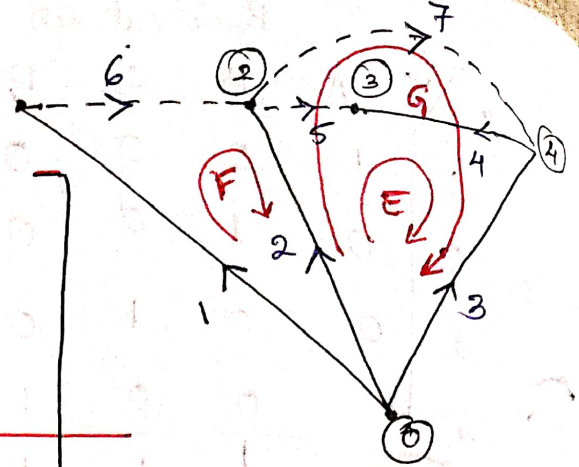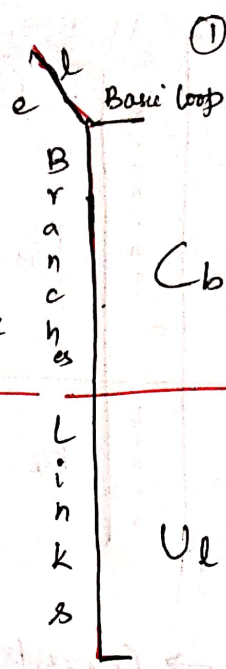

Where U_l - Identity matrix

3. Primitive Network:

- * An element in an electrical n/w is completely characterised by the relationship b/w the current through the element & V_{tg} a/c it.
- * A primitive element is a fundamental element which is not connected to any other element. A set of such unconnected elements is defined as a Primitive network.

- * Primitive n/w components can be represented in both impedance form & admittance form.

* Let,

V_{pq} - V_{tg} a/c the p-q

e_{pq} - Source V_{tg} in series with element p-q

i_{pq} - Current through element p-q

j_{pq} - Source current in parallel with element p-q

Z_{pq} - Self impedance of element p-q


Y_{pq} - Self admittance of element p-q.

- * Each element has 2 Variables, V_{pq} & i_{pq} . In steady state, these variables & the parameters of the elements Z_{pq} & Y_{pq} - real nos for dc ckt
 Z_{pq} & Y_{pq} - are Complex nos. for ac ckt.

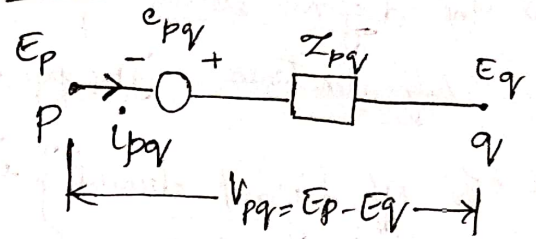(i) primitive n/w components in impedance form:

- * The performance eqn of an element in impedance form is

$$V_{pq} + e_{pq} = Z_{pq} \cdot i_{pq}$$



- * Expressing the Variables as Vectors & Parameters as matrices, the performance eqn in impedance form is,

$$\bar{V} + \bar{e} = [Z] \bar{i}$$

- * The diagonal element of the matrix $[Z]$ of primitive n/w is self impedance $Z_{pq, pq}$


- * off diagonal element \rightarrow mutual impedance $Z_{pq, rs}$
 b/w p-q & r-s

- * The matrix $[Z]$ is a diagonal matrix if there is no mutual coupling b/w elements. In this case self impedances are equal to the reciprocals of corresponding self admittances.

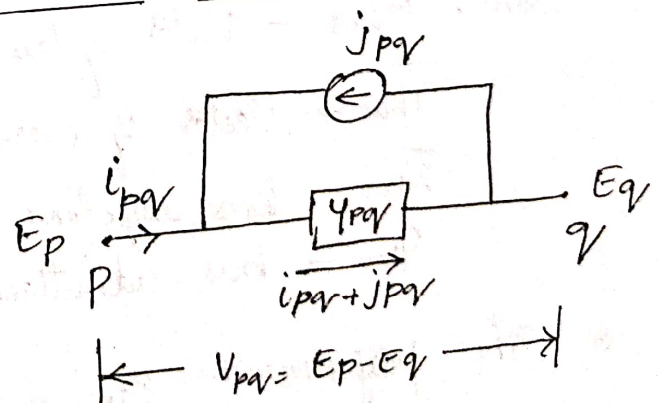(ii) Primitive n/w components in admittance form:

- * The performance eqn of an element in admittance form is

$$i_{pq} + j_{pq} = Y_{pq} \cdot V_{pq}$$



- * The parallel source current in admittance form is related to series source vsg in impedance form by

$$j_{pq} = -Y_{pq} \cdot e_{pq}$$

(9)

* expressing variables as vectors & parameters as matrices, the performance eqn in admittance form is

$$\vec{i} + \vec{j} = [Y] \vec{V}$$

* The diagonal element of the matrix $[Y]$ of the primitive n/w is Self admittance $Y_{pq,pq}$.

* The off diagonal element is \rightarrow Mutual admittance $Y_{pq,rs}$
b/w p-q & r-s

* The matrix $[Y]$ is a diagonal matrix if there is no mutual coupling b/w elements. In this case, the Self-impedances are equal to the reciprocals of corresponding Self admittances

* The primitive admittance matrix $[Y]$ can be obtained by inverting the primitive impedance matrix $[Z]$

4. Formation of Y_{bus} by Singular Transformation method

* The performance equations relating the bus voltages to bus current injections are given by

$$\vec{E}_{bus} = Z_{bus} \cdot \vec{I}_{bus} \rightarrow (1)$$

$$\vec{I}_{bus} = Y_{bus} \cdot \vec{E}_{bus} \rightarrow (2)$$

Where, \vec{E}_{bus} - Vector of bus voltages measured wrt reference bus

\vec{I}_{bus} - Vector of currents injected into the bus.

Z_{bus} - bus impedance matrix

Y_{bus} - bus admittance matrix

* The performance eqn of primitive n/w in admittance form is,

$$\vec{i} + \vec{j} = [Y] \cdot \vec{V} \rightarrow (3)$$

Pre multiplying (3) by A^T

$$A^T [\bar{i}] + A^T [\bar{j}] = A^T [Y] [\bar{V}] \rightarrow (4)$$

From KCL, Sum of currents at junction is equal to 0.

$$\therefore A^T [\bar{i}] = 0 \rightarrow (5)$$

$A^T [\bar{j}] \rightarrow$ is the algebraic sum of source currents @ each bus equal to vector of impressed bus current.

$$\therefore A^T [\bar{j}] = \bar{I}_{bus} \rightarrow (6)$$

Substitute (5) & (6) in (4), $\bar{I}_{bus} = A^T [Y] [\bar{V}] \rightarrow (7)$

The power into the n/w is,

$$[\bar{I}_{bus}^*]^T \cdot [\bar{E}_{bus}]$$

Sum of power in primitive n/w is,

$$[\bar{j}^*]^T \cdot \bar{V}$$

Power in primitive N/w = power in the interconnected N/w.

$$[\bar{I}_{bus}^*]^T \cdot [\bar{E}_{bus}] = [\bar{j}^*]^T \cdot \bar{V} \rightarrow (8)$$

Taking the conjugate transpose of (6)

$$[(A^T)^*]^T \cdot [\bar{j}^*]^T = [\bar{I}_{bus}^*]^T \rightarrow (9)$$

Substitute (9) in (8),

$$[\bar{E}_{bus}] \times [(A^T)^*]^T \cdot [\bar{j}^*]^T = [\bar{j}^*]^T [\bar{V}]$$

$$[\bar{E}_{bus}] \cdot A^* = [\bar{V}] \rightarrow (10)$$

$[A]$ is a real matrix, hence $A^* = A$

$$(10) \Rightarrow [A] [\bar{E}_{bus}] = [\bar{V}] \rightarrow (11)$$

(11)

Pre multiplying (3) by A^T

$$A^T [\bar{i}] + A^T [\bar{j}] = A^T [Y] \cdot [\bar{V}] \rightarrow (4)$$

From KCL, Sum of currents at junction is equal to 0.

$$\therefore A^T [\bar{i}] = 0 \rightarrow (5)$$

$A^T [\bar{j}] \rightarrow$ is the algebraic sum of source currents @ each bus equal to vector of impressed bus current.

$$\therefore A^T [\bar{j}] = \bar{I}_{bus} \rightarrow (6)$$

Substitute (5) & (6) in (4), $\bar{I}_{bus} = A^T [Y] [\bar{V}] \rightarrow (7)$

The power into the n/w is,

$$[\bar{I}_{bus}^*]^T \cdot [\bar{E}_{bus}]$$

Sum of power in primitive n/w is,

$$[\bar{j}^*]^T \cdot \bar{V}$$

Power in primitive N/w = power in the interconnected N/w.

$$[\bar{I}_{bus}^*]^T \cdot [\bar{E}_{bus}] = [\bar{j}^*]^T \cdot \bar{V} \rightarrow (8)$$

Taking the conjugate transpose of (6)

$$[(A^T)^*]^T \cdot [\bar{j}^*]^T = [\bar{I}_{bus}^*]^T \rightarrow (9)$$

Substitute (9) in (8)

$$[\bar{E}_{bus}] \times [(A^T)^*]^T \cdot [\bar{j}^*]^T = [\bar{j}^*]^T [\bar{V}]$$

$$[\bar{E}_{bus}] \cdot A^* = [\bar{V}] \rightarrow (10)$$

$[A]$ is a real matrix, hence $A^* = A$

$$(10) \Rightarrow [A] \cdot [\bar{E}_{bus}] = [\bar{V}] \rightarrow (11)$$

(11)

The performance Eqn can be obtained by Eqn (7) & (11)

$$\text{i.e. } [\bar{E}_{bus}] \times [A] = [\bar{V}]$$

$$\bar{I}_{bus} = A^T [Y] [\bar{V}]$$

Combining the above 2 Eqns,

$$\bar{I}_{bus} = A^T [Y] \cdot [\bar{E}_{bus}] \times [A]$$

Re-arranging above eqn : $\frac{\bar{I}_{bus}}{\bar{E}_{bus}} = A^T [Y] \cdot A$

From ohm's law: $V = IZ \Rightarrow$

$$\therefore \boxed{Y_{bus} = A^T [Y] \cdot A}$$

5. Formation of Y_{bus} by Inspection method:

* Let 'N' be the no. of major nodes in a n/w.

* Let, $V_1, V_2, V_3, \dots, V_n \rightarrow$ Node Voltages of nodes 1, 2, 3, ..., n resp.

$I_{11}, I_{22}, I_{33}, \dots, I_{nn} \rightarrow$ Sum of current sources connected to nodes 1, 2, 3, ..., n resp.

$Y_{ii} =$ Sum of admittances connected to node-i

$Y_{ij} =$ Negative of sum of admittances connected b/w nodes i & j.

* For N bus s/w with n no. of nodal Eqns, we have.

$$Y_{11} V_1 + Y_{12} V_2 + Y_{13} V_3 + \dots + Y_{1n} V_n = I_{11}$$

$$Y_{21} V_1 + Y_{22} V_2 + Y_{23} V_3 + \dots + Y_{2n} V_n = I_{22}$$

$$Y_{31} V_1 + Y_{32} V_2 + Y_{33} V_3 + \dots + Y_{3n} V_n = I_{33} \rightarrow \textcircled{1}$$

$$\vdots$$

$$Y_{n1} V_1 + Y_{n2} V_2 + Y_{n3} V_3 + \dots + Y_{nn} V_n = I_{nn}$$

Eqn ① in matrix form,

$$\begin{bmatrix} Y_{11} & Y_{12} & Y_{13} & \dots & Y_{1n} \\ Y_{21} & Y_{22} & Y_{23} & \dots & Y_{2n} \\ Y_{31} & Y_{32} & Y_{33} & \dots & Y_{3n} \\ \vdots & \vdots & \vdots & \ddots & \vdots \\ Y_{n1} & Y_{n2} & Y_{n3} & \dots & Y_{nn} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ \vdots \\ V_n \end{bmatrix} = \begin{bmatrix} I_{11} \\ I_{22} \\ I_{33} \\ \vdots \\ I_{nn} \end{bmatrix} \rightarrow \textcircled{2}$$

$$\textcircled{2} \Rightarrow Y V = I \rightarrow \textcircled{3}$$

In power s/s, Y matrix is designated as Y_{bus} \rightarrow Bus admittance
Nodes Vgcs \rightarrow Bus Voltages

\therefore Eqn ③ can be written as, $Y_{bus} \cdot V = I$

where, Y_{bus} - symmetrical around principal diagonal.


$Y_{11}, Y_{22}, Y_{33}, \dots, Y_{nn} \rightarrow$ Self admittances \rightarrow Diagonal elements
Other Elements \rightarrow Mutual admittances \rightarrow off diagonal elements

6.1 Problems of Elementary graph Theory:

8M

1. For the n/w shown, formulate the oriented graph, tree, bus incidence matrix (A), branch-path incidence matrix (K), Basic cut set incidence matrix (B), basic loop incidence matrix (C).
Choose elements (1, 2, 3, 4) as tree-branches.

J-24

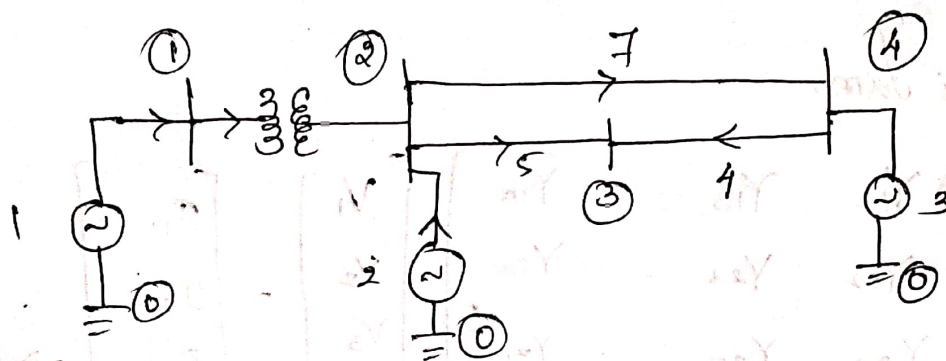


Soln: Solved in concept (1.3)

2. Obtain the primitive impedance matrix & primitive admittance matrix using the data shown below.

J-24

$[Z] \rightarrow$ impedances (self) of elements (e)

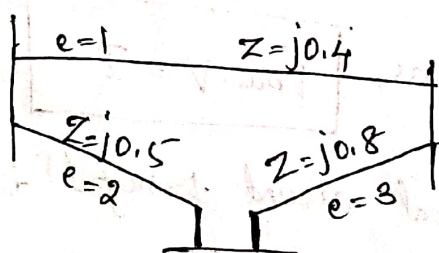$Z_m \rightarrow$ mutual impedances (in pu) b/w $e=1$ & $e=2$, $Z_m = 0.1 j$ pu.



Soln, To find $[Z_{prim}]$ & $[Y_{prim}]$

For above n/w, $n=3$, $\therefore [Z_{prim}] = \begin{bmatrix} Z_1 & Z_m & 0 \\ Z_m & Z_2 & 0 \\ 0 & 0 & Z_3 \end{bmatrix}$

Here $Z_{prim} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix} \Rightarrow$

Here: Diagonal elements $Z_{11} = Z_1$
Off diagonal element $Z_{12} = Z_{21} = Z_m$
 $Z_{22} = Z_2$
 $Z_{33} = Z_3$

$\therefore [Z_{prim}] = \begin{bmatrix} j0.4 & j0.1 & 0 \\ j0.1 & j0.5 & 0 \\ 0 & 0 & j0.8 \end{bmatrix}$

(14)



Primitive admittance matrix $Y_{prim} = [Z_{prim}]^{-1}$

$$Y_{prim} = \begin{bmatrix} j0.4 & j0.1 & 0 \\ j0.1 & j0.5 & 0 \\ 0 & 0 & j0.8 \end{bmatrix}^{-1}; \quad [X]^{-1} = \frac{1}{|X|} \cdot \text{adj}[X]$$

$$|X| = j(0.4) [j0.5 \times j0.8] - j0.1 [j0.1 \times j0.8] + 0 = -0.152j$$

$$\text{adj}[X] = \begin{bmatrix} +(-0.4) & -(-0.08) & +0 \\ -(-0.08) & +(-0.32) & -0 \\ +0 & -0 & +(-0.19) \end{bmatrix} = \begin{bmatrix} -0.4 & 0.08 & 0 \\ 0.08 & -0.32 & 0 \\ 0 & 0 & -0.19 \end{bmatrix}$$

$$Y_{prim} = \frac{1}{|X|} \cdot \text{adj}[X] = \frac{1}{-0.152j} \times \begin{bmatrix} -0.4 & 0.08 & 0 \\ 0.08 & -0.32 & 0 \\ 0 & 0 & -0.19 \end{bmatrix} = \begin{bmatrix} -j2.63 & -j0.526 & 0 \\ j0.5263 & -j2.105 & 0 \\ 0 & 0 & -j1.25 \end{bmatrix}$$

3) What is primitive n/p? Obtain primitive impedance matrix & primitive admittance matrix for the elements given in table below. JL-23

Element no.	Self impedance $Z_{pq,pq}$		Mutual impedance $Z_{pq,rs}$	
	Bus code p-q	Impedance in pu	Bus code r-s	Impedance in pu
1	1-2	$j0.2$	-	-
2	2-3	$j0.4$	1-2	$j0.1$
3	1-3	$j0.3$	2-3	$j0.1$

Soln: $n=3, \therefore Z_{prim} = n \times n = 3 \times 3; \quad Z_{prim} = \begin{bmatrix} Z_{11} & Z_{12} & Z_{13} \\ Z_{21} & Z_{22} & Z_{23} \\ Z_{31} & Z_{32} & Z_{33} \end{bmatrix}$

$$Z_{prim} = \begin{bmatrix} j0.2 & j0.1 & 0 \\ j0.1 & j0.4 & j0.1 \\ 0 & j0.1 & j0.3 \end{bmatrix}$$

Given: $Z_{11} = j0.2$
 $Z_{22} = j0.4$
 $Z_{33} = j0.3$

$Z_{12} \text{ \& } Z_{21} = j0.1 \rightarrow \text{off diagonal}$
 $Z_{23} \text{ \& } Z_{32} = j0.1 \rightarrow \text{off diagonal}$

WKT $Y_{prim} = [Z_{prim}]^{-1} = \begin{bmatrix} j0.2 & j0.1 & 0 \\ j0.1 & j0.4 & j0.1 \\ 0 & j0.1 & j0.3 \end{bmatrix}^{-1}$; WKT $[X]^{-1} = \frac{1}{|X|} \cdot \text{adj}[X]$

$$|X| = j(0.2) [(j0.4 \times j0.3) - (j0.1 \times j0.1)] - j0.1 (j0.1 \times j0.3 - 0) + 0$$


$$|X| = \underline{\underline{-0.019j}}$$

$$\text{adj}[X] = \begin{bmatrix} +(-0.11) & -(-0.03) & +(-0.01) \\ -(-0.03) & +(-0.06) & -(-0.02) \\ +(-0.01) & -(-0.02) & +(-0.07) \end{bmatrix}$$

$$[X]^{-1} = \frac{1}{|X|} \cdot \text{adj}[X] = \frac{1}{-0.019j} \times \begin{bmatrix} -0.11 & 0.03 & -0.01 \\ 0.03 & -0.06 & 0.02 \\ -0.01 & 0.02 & -0.07 \end{bmatrix}$$

$$Y_{prim} = \begin{bmatrix} -5.78j & 1.57j & -0.526j \\ 1.57j & -3.157j & 1.052j \\ -0.526j & 1.052j & -3.684j \end{bmatrix}$$

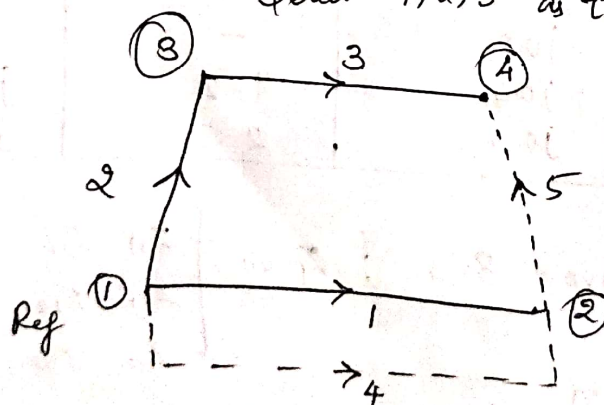4) Form the incidence matrices A, B, C for the graph shown & 8M Prove that $B'C = 0$. Select 1, 2, 3 as tree, node ① as reference.



Soln: From above graph: $n=4$
 $e=5$
 $b=n-1=3$
 $l=e-n=5-3=2$

* Element node incidence matrix : \hat{A}

$$\hat{A} = \begin{matrix} & e \backslash n & \textcircled{1} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} 1 & -1 & 0 & 0 \\ 1 & 0 & -1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & -1 & 0 & 0 \\ 0 & 1 & 0 & -1 \end{bmatrix} \end{matrix}$$


Node $\textcircled{1} \rightarrow$ reference node, weight

$$A = \begin{matrix} & e \backslash \text{bus} & \textcircled{2} & \textcircled{3} & \textcircled{4} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \\ -1 & 0 & 0 \\ 1 & 0 & -1 \end{bmatrix} \end{matrix}$$

* Basic cut-set incidence matrix - B ,

$$B = \begin{matrix} & e \backslash b & \textcircled{A} & \textcircled{B} & \textcircled{C} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ 1 & 0 & 0 \\ -1 & 1 & 1 \end{bmatrix} \end{matrix}$$


→ Basic cut sets

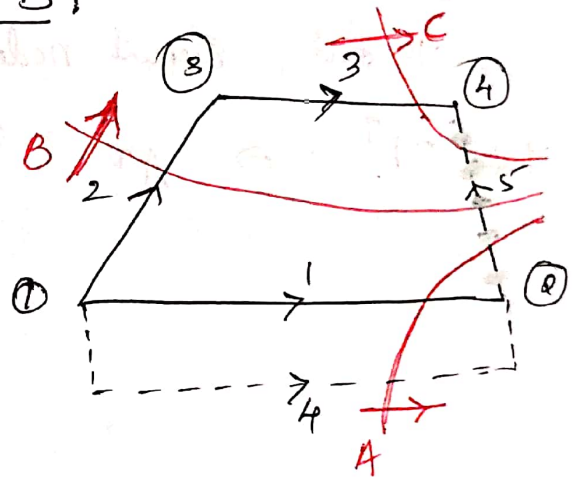

* Basic loop incidence matrix - C :

$$C = \begin{matrix} & e \backslash l & \textcircled{D} & \textcircled{E} \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \end{matrix} & \begin{bmatrix} -1 & 1 \\ 0 & -1 \\ 0 & -1 \\ 1 & 0 \\ 0 & 1 \end{bmatrix} \end{matrix}$$

→ loops

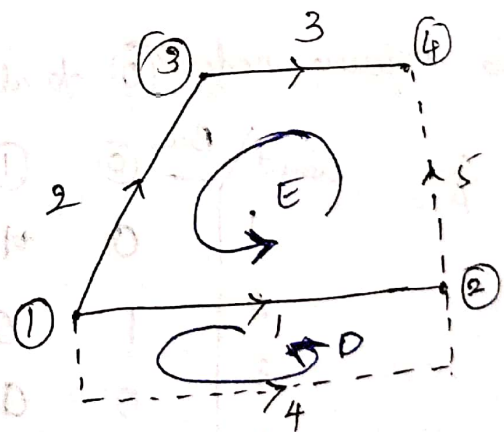

5. The bus incidence matrix of a power system is shown below.

6M

$$A = \begin{array}{c|cccccccc} & \text{elements} & & & & & & \\ \text{Buses} & & & & & & & \\ \hline 1 & 1 & 0 & 0 & -1 & 0 & 0 & 1 \\ 2 & -1 & -1 & -1 & 0 & 0 & 0 & 0 \\ 3 & 0 & 0 & 1 & 0 & -1 & 1 & 0 \\ 4 & 0 & 0 & 0 & 0 & 0 & -1 & -1 \end{array}$$

Il-23

Obtain element node incidence matrix. Hence draw the oriented graph.

Soln: Given: Bus incidence Matrix - A

To find Element node incidence matrix \hat{A} .

Take $A^T \Rightarrow A^T =$

element	Bus ①	②	③	④
1	1	-1	0	0
2	0	-1	0	0
3	0	-1	1	0
4	-1	0	0	0
5	0	0	-1	0
6	0	0	1	-1
7	1	0	0	-1

Add reference node ⑤ to above matrix to get \hat{A}


$$\therefore \hat{A} = \begin{array}{c|cccccc} & \text{element} & & & & & \\ \text{Bus} & & & & & & \\ \hline ⑤ & 0 & 1 & -1 & 0 & 0 & 0 \\ 1 & 1 & 0 & -1 & 0 & 0 & 0 \\ 2 & 0 & -1 & 1 & 0 & 0 & 0 \\ 3 & 1 & -1 & 0 & 0 & 0 & 0 \\ 4 & 1 & 0 & 0 & -1 & 0 & 0 \\ 5 & 0 & 0 & 0 & 1 & -1 & -1 \\ 6 & 0 & 0 & 0 & 0 & 1 & -1 \\ 7 & 0 & 1 & 0 & 0 & 0 & -1 \end{array}$$

Note: Column ⑤ i.e Bus ⑤ is filled considering the summation of each row to be zero.

(18)



Oriented graph of \hat{A} :-

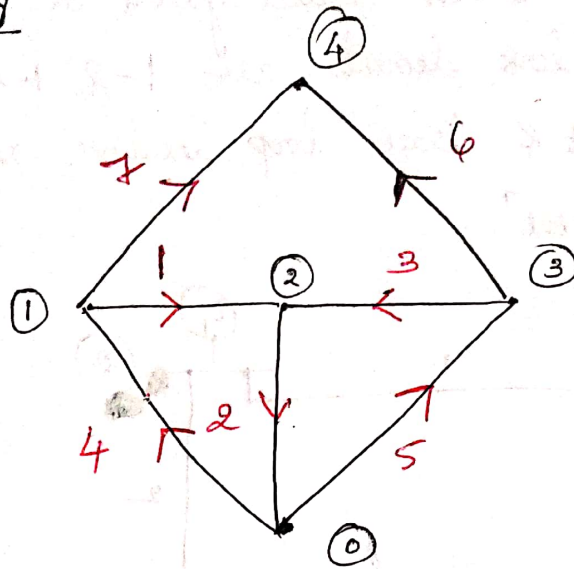

6. The bus incidence matrix A for a n/w of 8 elements & 5 nodes (buses) is given in table below. Reconstruct the oriented graph. Hence obtain the one-line diagrams of the s/z indicating the generator position.

$A =$

	1	2	3	4	5	6	7	8
①	1	0	0	0	-1	0	-1	0
②	0	1	0	0	1	-1	0	-1
③	0	0	1	-1	0	1	0	0
④	0	0	0	1	0	0	1	1

$J=23$

Soln: ^{Step 1} Given bus incidence matrix - A .

^{Step 2} * To find element node incidence matrix \hat{A} to find oriented graph

^{Step 3} Take $A^T \Rightarrow$


A^T

element	node ①	②	③	④
1	1	0	0	0
2	0	1	0	0
3	0	0	1	0
4	0	0	-1	1
5	-1	1	0	0
6	0	-1	1	0
7	-1	0	0	1
8	0	-1	0	1

\hat{A}

e	node ①	②	③	④
1	-1	1	0	0
2	-1	0	1	0
3	-1	0	0	1
4	0	0	0	-1
5	0	-1	1	0
6	0	0	-1	1
7	0	-1	0	0
8	0	0	-1	0


^{Step 5} Orient graph

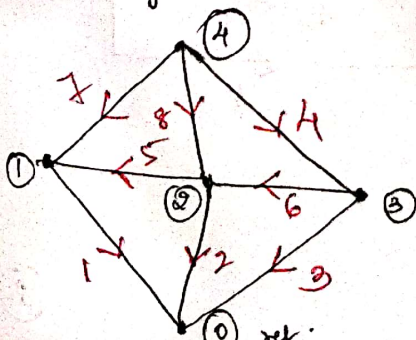


←
Oriented graph.

(19)

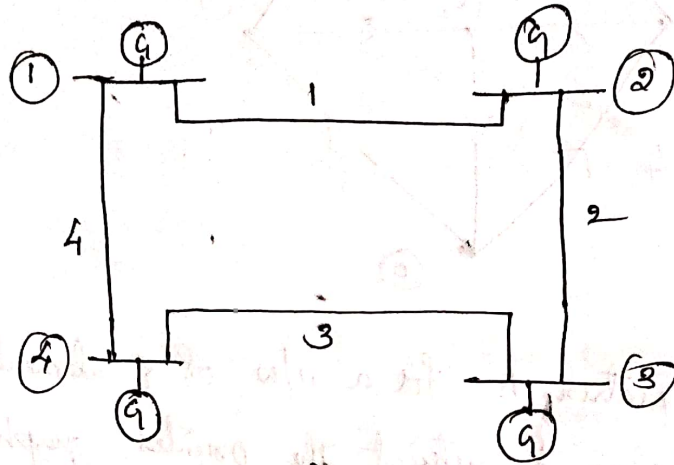7) For the power s/s shown, Select ground as reference & a tree for which link elements are 1-2, 1-4, 2-3, 3-4. Obtain basic cut set & basic loop incidence matrices. Verify the relation $C_b = -B_l^T$. JL-22



Soln: Convert the given n/w to graph.

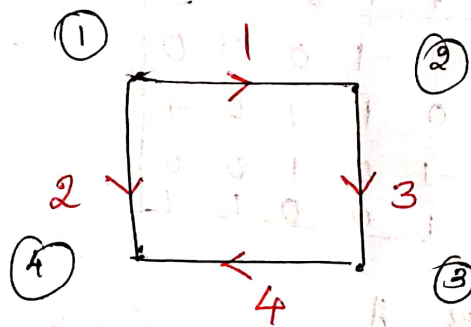


Here $e = 4$
 $n = 4$
 links $l = e - n + 1$
 $l = 4 - 4 + 1$
 $l = 1$

No. of loops = no. of links = 1

No. of basic cut set = $n - 1 = 4 - 1 = 3$

Basic loop incidence matrix: C

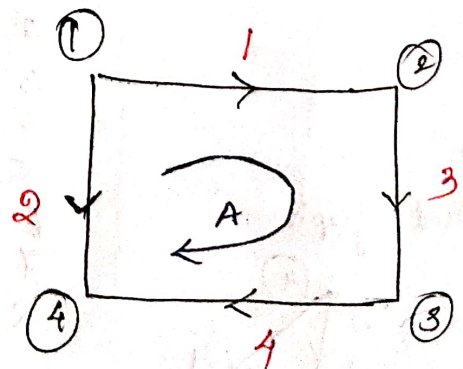
$$C = \begin{matrix} & \begin{matrix} \text{loops} \\ A \end{matrix} \\ \begin{matrix} e \\ 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} 1 \\ -1 \\ 1 \\ 1 \end{bmatrix} \end{matrix} = \begin{bmatrix} C_b \\ [u_c] \end{bmatrix}$$



* last element in graph is always link


Basic cut set - incidence matrix 'B':
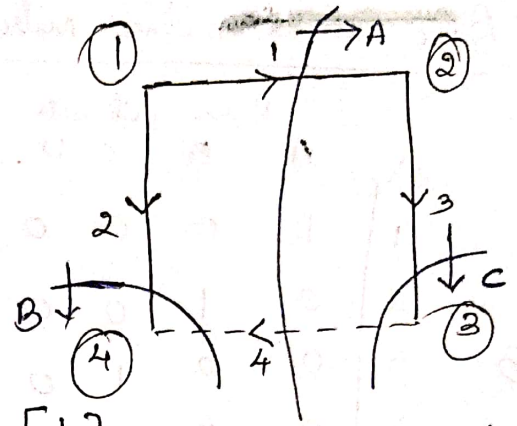
$$B = \begin{matrix} & \text{Cutsets} \\ e \backslash & A & B & C \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \end{matrix} & \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & 1 & -1 \end{bmatrix} \end{matrix} = \begin{bmatrix} U_B \\ B_L \end{bmatrix}$$



Take $[B_L]^T = \begin{bmatrix} -1 \\ 1 \\ 1 \end{bmatrix} \rightarrow \text{Take } [B_L]^T = \begin{bmatrix} 1 \\ -1 \\ 1 \end{bmatrix} = C_b \rightarrow \text{Hence proved.}$

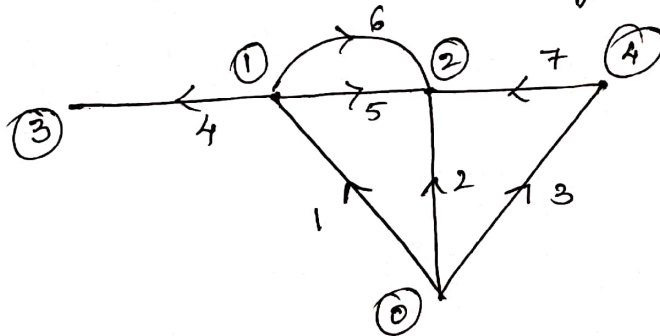8. The Oriented Connected graph of a s/s is show. Obtain basic cutset & basic loop incidence matrices. Hence verify the relation
(i) $BL = AK^T$ (ii) $B^T C = 0$. Take ground as reference.



Soln: Here

$$n = 5$$

$$e = 7$$

$$\text{links} = l = e - n + 1 = 7 - 5 + 1 = 3$$


* - last elements in graph.
(elements : 5, 6, 7)

$$\text{No. of loops} = \text{No. of links} = 3.$$

$$\text{No. of basic cutset} = n - 1 = 5 - 1 = 4.$$

Basic loop incidence matrix 'C' :-
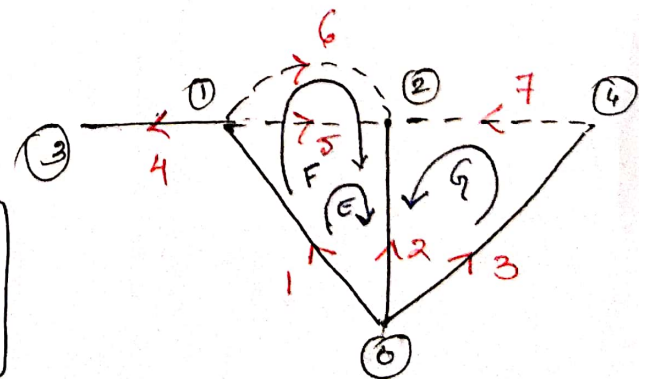
$$C = \begin{matrix} & \text{Loops} \\ e \backslash & E & F & G \\ \begin{matrix} 1 \\ 2 \\ 3 \\ 4 \\ 5 \\ 6 \\ 7 \end{matrix} & \begin{bmatrix} 1 & 1 & 0 \\ -1 & -1 & -1 \\ 0 & 0 & -1 \\ 0 & 0 & 0 \\ 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \end{matrix} = \begin{bmatrix} C_b \\ U_C \end{bmatrix}$$




loop orientation is same as link orientation

(21)

Basic Cut Set Incidence matrix 'B':

$$B = \begin{array}{c|cccc} & \text{Basic cut sets} \\ & A & B & C & D \\ e \backslash & & & & \\ \hline 1 & 1 & 0 & 0 & 0 \\ 2 & 0 & 1 & 0 & 0 \\ 3 & 0 & 0 & 1 & 0 \\ 4 & 0 & 0 & 0 & 1 \\ \hline 5 & -1 & 1 & 0 & -1 \\ 6 & -1 & 0 & 0 & -1 \\ 7 & 0 & 1 & -1 & 0 \end{array} = \begin{bmatrix} U_B \\ B_1 \end{bmatrix}$$

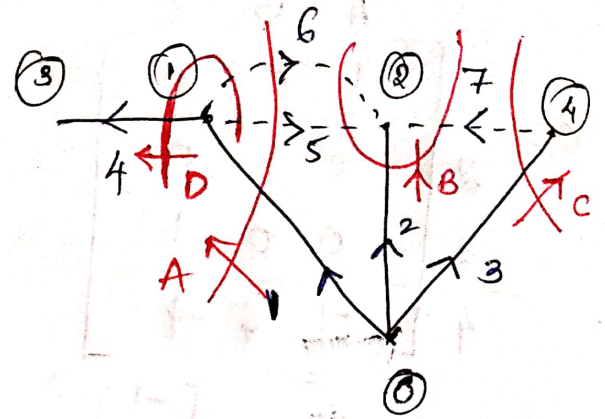

Cut set - Direction is same as branch/twigs