

ACADEMIC YEAR -2025-26 (ODD SEM)

**SUBJECT: Digital Design & Computer
Organization**

SUBJECT CODE: BCS302

MODULE -1

Prepared by:
Mr Kalathma M K,
Asst prof, Dept. of CSE
ATMECE

Contents

Introduction

Logic gates

Boolean Rules & Laws

Minterms and Maxterms


K-Map

Introduction to Verilog

Introduction

- **Analog signal** is a signal whose amplitude can take any value between given limits. An **analog circuits** operates on continuous signals.
- **Digital signal** is a signal whose amplitude can have only given discrete values between defined limits. A **digital circuits** operates on discrete signals.
- **Clock** is a periodic, rectangular waveform used as a basic timing signal.
- A **table** that shows all of the input output possibilities of a logic circuit is called **truth table**.


Clock

 

- A **digital circuit** having one or more input signals but only one output signal is called a gate.
- The most **basic gates** are -the **NOT** gate (inverter), the **OR** gate and the **AND** gate.
- Any logic function/ logic circuit can be implemented using only one kind of gate then such gates are called **universal logic gates**. **NOR** gate and **NAND** gate are called universal logic gates.
- The other logic gates are **XOR** and **XNOR** gate.


Logic gates

Buffer

 

Input	Output
0	0
1	1

Inverter

 


Input	Output
0	1
1	0

AND




A	B	Output
0	0	0
1	0	0
0	1	0
1	1	1

NAND

 


A	B	Output
0	0	1
1	0	1
0	1	1
1	1	0

OR

 

A	B	Output
0	0	0
1	0	1
0	1	1
1	1	1

NOR

 

A	B	Output
0	0	1
1	0	0
0	1	0
1	1	0

XOR



A	B	Output
0	0	0
1	0	1
0	1	1
1	1	0

XNOR



A	B	Output
0	0	1
1	0	0
0	1	0
1	1	1

Boolean Rules & Laws

Table 5-3: Summary of Rules and Laws of Boolean Algebra


Reference	Rule or Law	Reference	Rule or Law
Rule 1	$A + 0 = A$	Rule 10	$A + AB = A$
Rule 2	$A + 1 = 1$	Rule 11	$A + A'B = A$
Rule 3	$A \cdot 0 = 0$	Rule 12	$(A + B)(A + C) = A + BC$
Rule 4	$A \cdot 1 = A$	Commutative Law	$A + B = B + A$
Rule 5	$A + A = A$		$AB = BA$
Rule 6	$A + A' = 1$	Associative Law	$A + (B + C) = (A + B) + C$
Rule 7	$A \cdot A = A$		$A(BC) = (AB)C$
Rule 8	$A \cdot A' = 0$	Distributive Law	$A(B + C) = AB + AC$
Rule 9	$(A')' = A$		

De Morgan's Theorem

$$\overline{A + B} = \bar{A} \cdot \bar{B}$$

The **First** theorem states that “The complement of the sum of all the terms is equal to the product of the complement of each term”.

De Morgan's first theorem

 


A	B	$\overline{A + B}$	\bar{A}	\bar{B}	$\bar{A} \cdot \bar{B}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0

The **First** theorem states that “The complement of the product of all the terms is equal to the sum of the complement of each term”.

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

De Morgan's second theorem

 

A	B	\overline{AB}	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0

Minterms and Maxterms for Three Variables

Row No.	A B C	Minterms	Maxterms
0	0 0 0	$A'B'C' = m_0$	$A + B + C = M_0$
1	0 0 1	$A'B'C = m_1$	$A + B + C' = M_1$
2	0 1 0	$A'BC' = m_2$	$A + B' + C = M_2$
3	0 1 1	$A'BC = m_3$	$A + B' + C' = M_3$
4	1 0 0	$AB'C' = m_4$	$A' + B + C = M_4$
5	1 0 1	$AB'C = m_5$	$A' + B + C' = M_5$
6	1 1 0	$ABC' = m_6$	$A' + B' + C = M_6$
7	1 1 1	$ABC = m_7$	$A' + B' + C' = M_7$

- A **minterm** is a **product** of “n” literals
- A **maxterm** is a **sum** of “n” literals
- **Sum Of Products (SOP)**: A Boolean equation that is the logical sum of logical products. This type of equation applies to an AND-OR circuit.
- **Product Of Sums (POS)**: A Boolean equation that is the logical product of logical sums. This type of equation applies to an OR-AND circuit.

Steps to get SOP

- 1) Locate each output 1 in truth table
- 2) Write the respective **minterm**
- 3) Apply OR operation to the **minterms**

A	B	C	Y	
0	0	0	0	
0	0	1	1	$\bar{A}.\bar{B}.C$
0	1	0	1	$\bar{A}.B.\bar{C}$
0	1	1	1	$\bar{A}.B.C$
1	0	0	0	
1	0	1	0	
1	1	0	1	$A.B.\bar{C}$
1	1	1	0	

SOP:

$$\bar{A}.\bar{B}.C + \bar{A}.B.\bar{C} + \bar{A}.B.C + A.B.\bar{C}$$

$$\Sigma m(1, 2, 3, 6)$$

Steps to get POS

- 1) Locate each output 0 in truth table
- 2) Write the respective **maxterm**
- 3) Apply AND operation to the **maxterms**

A	B	C	Y	
0	0	0	0	$A+B+C$
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	0	$\overline{A}+B+C$
1	0	1	0	$\overline{A}+B+\overline{C}$
1	1	0	1	$\overline{A}+\overline{B}+C$
1	1	1	0	$\overline{A}+\overline{B}+\overline{C}$

POS:

$$(A+B+C). (\overline{A}+B+C). (\overline{A}+B+\overline{C}). (\overline{A}+\overline{B}+\overline{C}) = \prod M(0, 4, 5, 7)$$

The various Boolean expression simplification techniques are


- 1) Algebraic techniques
- 2) Karnaugh Map/K-Map Method
- 3) Quine McCluskey Method
- 4) Entered Variable Map/ MEV/EMV Method

Karnaugh map/K map is a method simplifying and manipulating switching functions.

K map method is faster and easier to apply than other simplification methods.


Two Variable K-Map

 The number of cells in 2 variable K-map is four (2X2), since the number of variables is two. The following figure shows 2 variable K-map and location of minterms on a 2 variable K-map



Example: Convert following truth table into K map.
 $Y = F(A, B) = \sum m(2, 3)$

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	1

 

	\overline{B}	B
\overline{A}	0 ₀	0 ₁
A	1 ₂	1 ₃

Three Variable K-Map

The number of cells in 3 variable K-map is eight (2³), since the number of variables is 3. The following figure shows 3 variable K-map and location of minterms on a 3 variable K-map.

BC	00	01	11	10
A				
0	000	001	011	010
1	100	101	111	110

	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
\overline{A}	$\overline{A}\overline{B}\overline{C}$	$\overline{A}\overline{B}C$	$\overline{A}BC$	$\overline{A}B\overline{C}$
A	$A\overline{B}\overline{C}$	$A\overline{B}C$	ABC	$AB\overline{C}$

	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
\overline{A}	0	1	3	2
A	4	5	7	6

Convert following truth table into K map.

$$Y = F(A, B, C) = \Sigma m (2, 6, 7)$$

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



	$\overline{B}\overline{C}$	$\overline{B}C$	BC	$B\overline{C}$
\overline{A}	0 ₀	0 ₁	0 ₃	1 ₂
A	0 ₄	0 ₅	1 ₇	1 ₆

Four-Variable Karnaugh Maps

The number of cells in 4 variable K-map is sixteen (2^4), since the number of variables is 4. The following figure shows 4 variable K-map and location of min terms on a 4 variable K-map.

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$		$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$						
$\overline{A}\overline{B}$	$\overline{A}\overline{B}\overline{C}\overline{D}$	$\overline{A}\overline{B}\overline{C}D$	$\overline{A}\overline{B}C\overline{D}$	$\overline{A}\overline{B}CD$	$\overline{A}\overline{B}$	0	1	3	2	$\overline{A}\overline{B}$	00	0000	0001	0011	0010
$\overline{A}B$	$\overline{A}B\overline{C}\overline{D}$	$\overline{A}B\overline{C}D$	$\overline{A}BC\overline{D}$	$\overline{A}BCD$	$\overline{A}B$	4	5	7	6	$\overline{A}B$	01	0100	0101	0111	0110
AB	$AB\overline{C}\overline{D}$	$AB\overline{C}D$	$ABC\overline{D}$	$ABCD$	AB	12	13	15	14	AB	11	1011	1101	1111	1110
$A\overline{B}$	$A\overline{B}\overline{C}\overline{D}$	$A\overline{B}\overline{C}D$	$A\overline{B}C\overline{D}$	$A\overline{B}CD$	$A\overline{B}$	8	9	11	10	$A\overline{B}$	10	1000	1001	1011	1010


Convert following truth table into K map.
 $Y = F(A, B, C, D) = \Sigma m(1,6,7,14)$

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0

	$\overline{C}\overline{D}$	$\overline{C}D$	CD	$C\overline{D}$
$\overline{A}\overline{B}$	0 <small>0</small>	1 <small>1</small>	0 <small>3</small>	0 <small>2</small>
$\overline{A}B$	0 <small>4</small>	0 <small>5</small>	1 <small>7</small>	1 <small>6</small>
AB	0 <small>12</small>	0 <small>13</small>	0 <small>15</small>	1 <small>14</small>
$A\overline{B}$	0 <small>8</small>	0 <small>9</small>	0 <small>11</small>	0 <small>10</small>

Pairs, Quads and Octets

 - Two adjacent 1's in the K-map is called a **pair** and it eliminate one **variable**.



- A **quad** is a group of four 1's that are horizontally or vertically adjacent and a quad eliminates two variables and their complements.

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	0	0	0
$\bar{A}B$	1	1	1	1
AB	0	0	0	0
$A\bar{B}$	0	0	0	0

Red box highlights the quad in the $\bar{A}B$ row, labeled $\bar{A}\bar{B}$.

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	0	1	0	0
$\bar{A}B$	0	1	0	0
AB	0	1	0	0
$A\bar{B}$	0	1	0	0

Red box highlights the quad in the $\bar{C}D$ column, labeled $\bar{C}\bar{D}$.





	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	0	1
$\bar{A}B$	1	0	0	1
AB	0	1	1	0
$A\bar{B}$	0	1	1	0

Red boxes highlight two quads: one in the $\bar{C}\bar{D}$ column labeled $\bar{A}\bar{D}$, and one in the CD column labeled AD .

	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	0	0	1
$\bar{A}B$	0	1	1	0
AB	0	1	1	0
$A\bar{B}$	1	0	0	1

Red boxes highlight two quads: one in the $\bar{C}\bar{D}$ column labeled $\bar{B}\bar{D}$, and one in the CD column labeled BD .

    - An *octet* is a group of 8 1s that are horizontally or vertically adjacent and an octet eliminates three variables and their complements.



Simplify the following Boolean expression using the 4-variable K-map.

$$f(A, B, C, D) = \sum m(2, 3, 6, 7, 8, 10, 13, 15)$$

CD \ AB	00	01	11	10
00	0	1	1	1
01	4	5	1	1
11	12	1	1	14
10	1	8	9	1

So the simplified SOP expression is,

$$f(A, B, C, D) = \bar{A}C + A\bar{B}D + AB\bar{D}$$

Minimize the following Boolean expression using the 4-variable K-map.

$$f(A, B, C, D) = \prod M(4, 6, 11, 14, 15)$$

CD \ AB	00	01	11	10
00	0	1	3	2
01	0			0
11			0	0
10			0	

So, the reduced POS expression of the given Boolean function is,

$$f(A, B, C, D) = (A + \bar{B} + D)(\bar{A} + \bar{C} + \bar{D})(\bar{A} + \bar{B} + \bar{C})$$



Determination of Minimum Expressions using Essential Prime Implicants

- Any single 1 or any group of 1's which can be combined together on a map of the function F represents a product term which is called an implicant of F .
- A product term implicant is called a prime implicant if it cannot be combined with another term to eliminate a variable.

The following procedure can then be used to obtain a minimum sum of products from a Karnaugh map

- 1) Choose a minterm (a 1) which has not yet been covered.
- 2) Find all 1's and X's adjacent to that minterm.
- 3) If a single term covers the minterm and all of the adjacent 1's and X's, then that term is an essential prime implicant, so select that term
- 4) Repeat steps 1, 2, and 3 until all essential prime implicants have been chosen.
- 5) Find a minimum set of prime implicants which cover the remaining 1's on the map.

XOR & XNOR gates using NAND gates

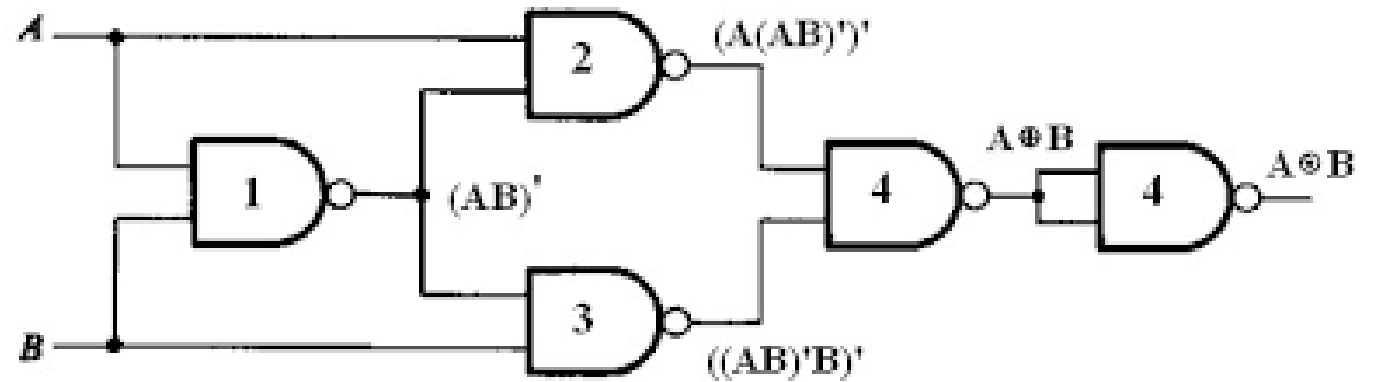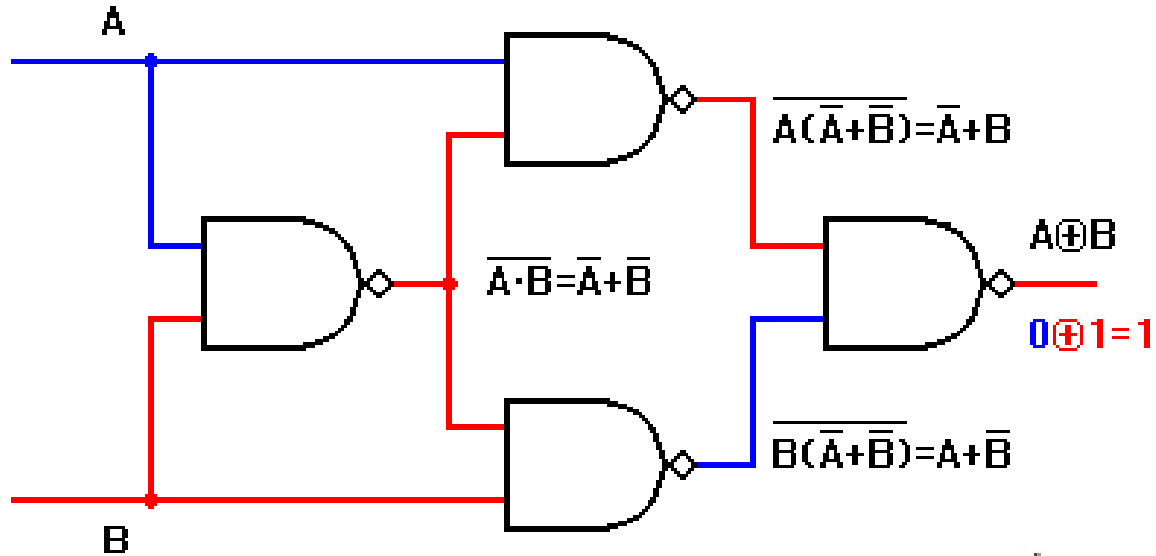

X-NOR

VERILOG

Hardware Description Language

About Verilog

- Along with VHDL, Verilog is among the most widely used HDLs.
- Main differences:
 - VHDL was designed to support system-level design and specification.
 - Verilog was designed primarily for digital hardware designers developing FPGAs and ASICs.

Concept of Verilog “Module”

In Verilog, the basic unit of hardware is called a module.

Basic Syntax of Module Definition

```
module module_name (list_of_ports);  
  
    input/output declarations;  
  
    local net declarations;  
  
    parallel statements;  
  
endmodule
```

Example 1 :: simple AND gate

```
module simpleand (f, x, y);  
    input x, y;  
    output f;  
    assign f = x & y;  
endmodule
```

Verilog Language Features

Operators

Arithmetic Operators:

+	unary (sign) plus
-	unary (sign) minus
+	binary plus (add)
-	binary minus (subtract)
*	multiply
/	divide
%	modulus
**	exponentiation

Examples:

$-(b + c)$
 $(a - b) + (c * d)$
 $(a + b) / (a - b)$
 $a \% b$
 $a ** 3$

Operators

Logical Operators:

!	logical negation
&&	logical AND
	logical OR

Examples:

```
(done && ack)
(a || b)
!(a && b)
((a > b) || (c == 0))
((a > b) && !(b > c))
```


Operators

Bitwise Operators:

~	bitwise NOT
&	bitwise AND
	bitwise OR
^	bitwise exclusive-OR
~^	bitwise exclusive-NOR

Examples:

```
wire a, b, c, d, f1, f2, f3, f4;  
assign f1 = ~a | b;  
assign f2 = (a & b) | (b & c) | (c & a);  
assign f3 = a ^ b ^ c;  
assign f4 = (a & ~b) | (b & c & ~d);
```

Operators

Relational Operators:

<code>!=</code>	not equal
<code>==</code>	equal
<code>>=</code>	greater or equal
<code><=</code>	less or equal
<code>></code>	greater
<code><</code>	less

Examples:

```
(a != b)
((a + b) == (c - d))
((a > b) && (c < d))
(count <= 0)
```

Operators

Shift Operators:

>>	shift right
<<	shift left
>>>	arithmetic shift right

Examples:

```
wire [15:0] data, target;  
assign target = data >> 3;  
assign target = data >>> 2;
```

AND Gate Using Data Flow Modelling

```
module and_gate_d(a,b,y);  
input a,b;  
output y;  
  
assign y = a & b;  
  
endmodule
```

AND Gate Using Behavioral Modelling

```
module AND_gate_b(a,b,y);  
input a,b;  
output y;  
  
always @ (a,b)  
y = a & b;  
  
endmodule
```

AND Gate Using Structural Modelling

```
module and_gate_s(a,b,y);  
input a,b;  
output y;  
  
and(y,a,b);  
  
endmodule
```

Data Flow

```
module and_gate_d(a,b,y);  
input a,b;  
output y;  
  
assign y = a & b;  
  
endmodule
```

Behavioral

```
module AND_gate_b(a,b,y);  
input a,b;  
output y;  
  
always @ (a,b)  
y = a & b;  
  
endmodule
```

Structural

```
module and_gate_s(a,b,y);  
input a,b;  
output y;  
  
and(y,a,b);  
  
endmodule
```


Thank you