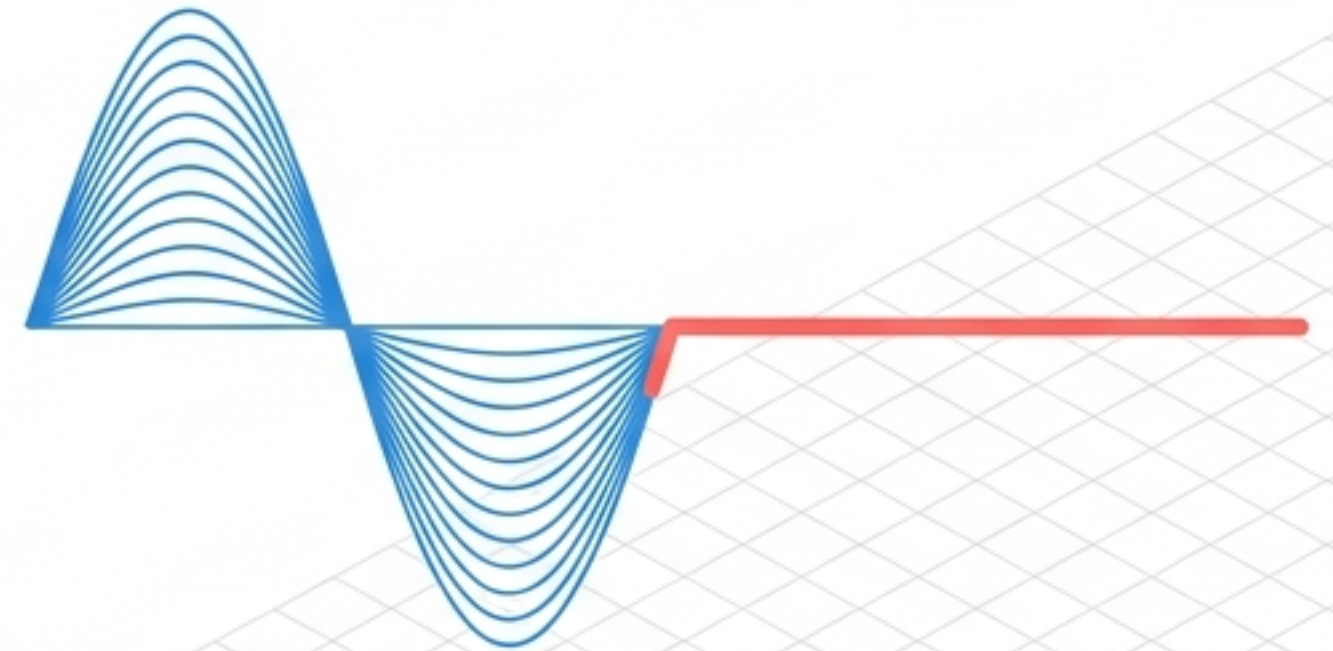


Simulation Report: Single Phase Half-Wave Diode Rectifier

A virtual prototyping study using
MATLAB Simulink



INPUT SUPPLY

100 V / 50 Hz

AC Sinusoidal

LOAD PARAMETER

50 Ω

Resistive (R)

PLATFORM

Simulink

Power Systems Blockset

Core Function and Project Scope

Rectifiers are the fundamental bridge between Alternating Current (AC) and Direct Current (DC). This simulation models the simplest form of this conversion: the Half-Wave Rectifier.



Mechanism: The circuit utilizes a single diode to allow only one half-cycle of the AC source to pass.




Application: Foundational model for understanding power electronics.



Setup: Implementation relies on a basic pairing of a diode and a resistive load.

The Gatekeeper Concept

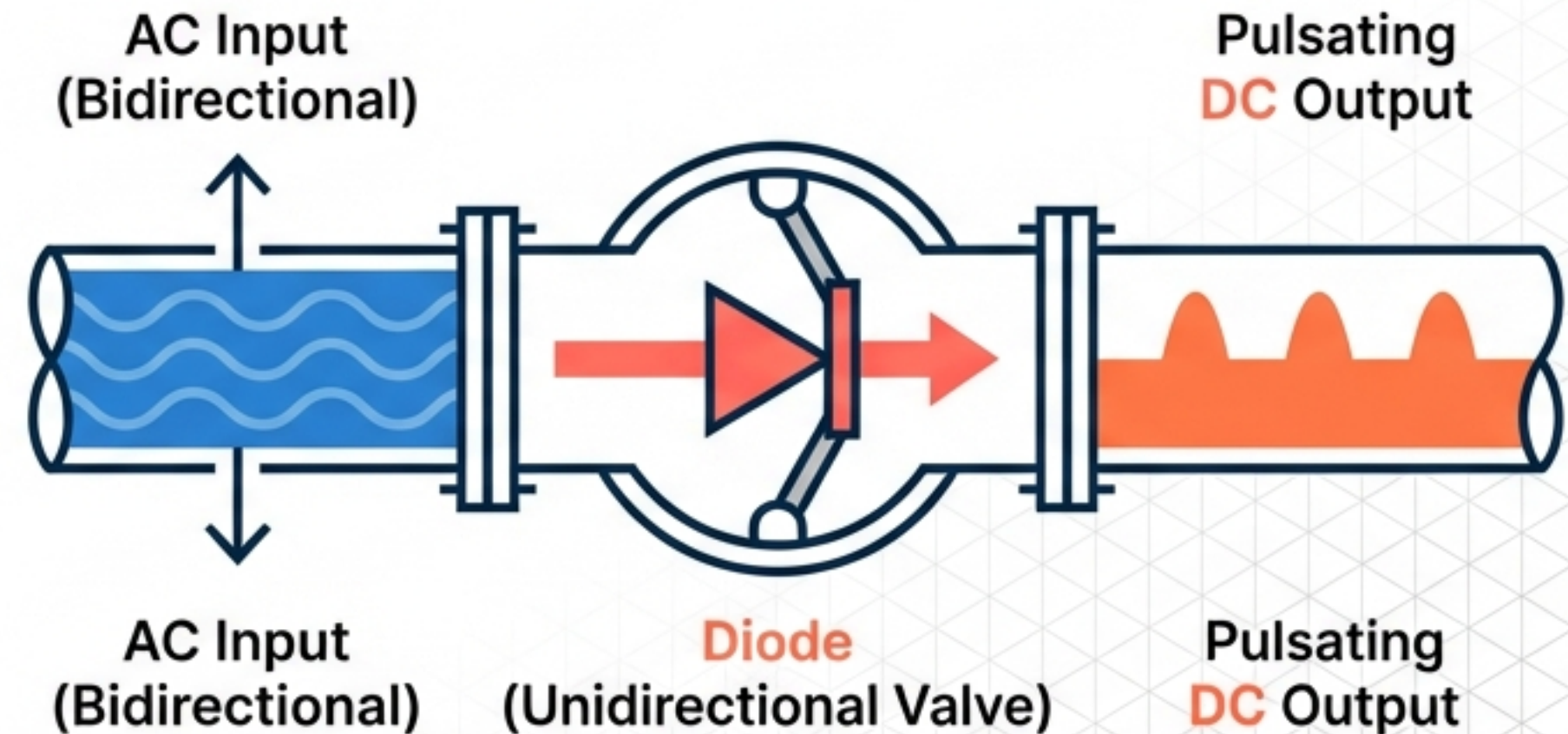

Simulation Objectives and Specifications

Objectives


1. Model a single-phase half-wave diode rectifier.
2. Visualize and compare input vs. output waveforms.
3. Analyze voltage/current behavior across the load.
4. Verify the rectification process within Simulink.

Technical Constraints

Specification	Value
Source	AC Voltage (100 V Peak, 50 Hz)
Switching Element	Single Diode
Load	50 Ω Resistor
Measurement	Voltage across Load



Theoretical Circuit Topology

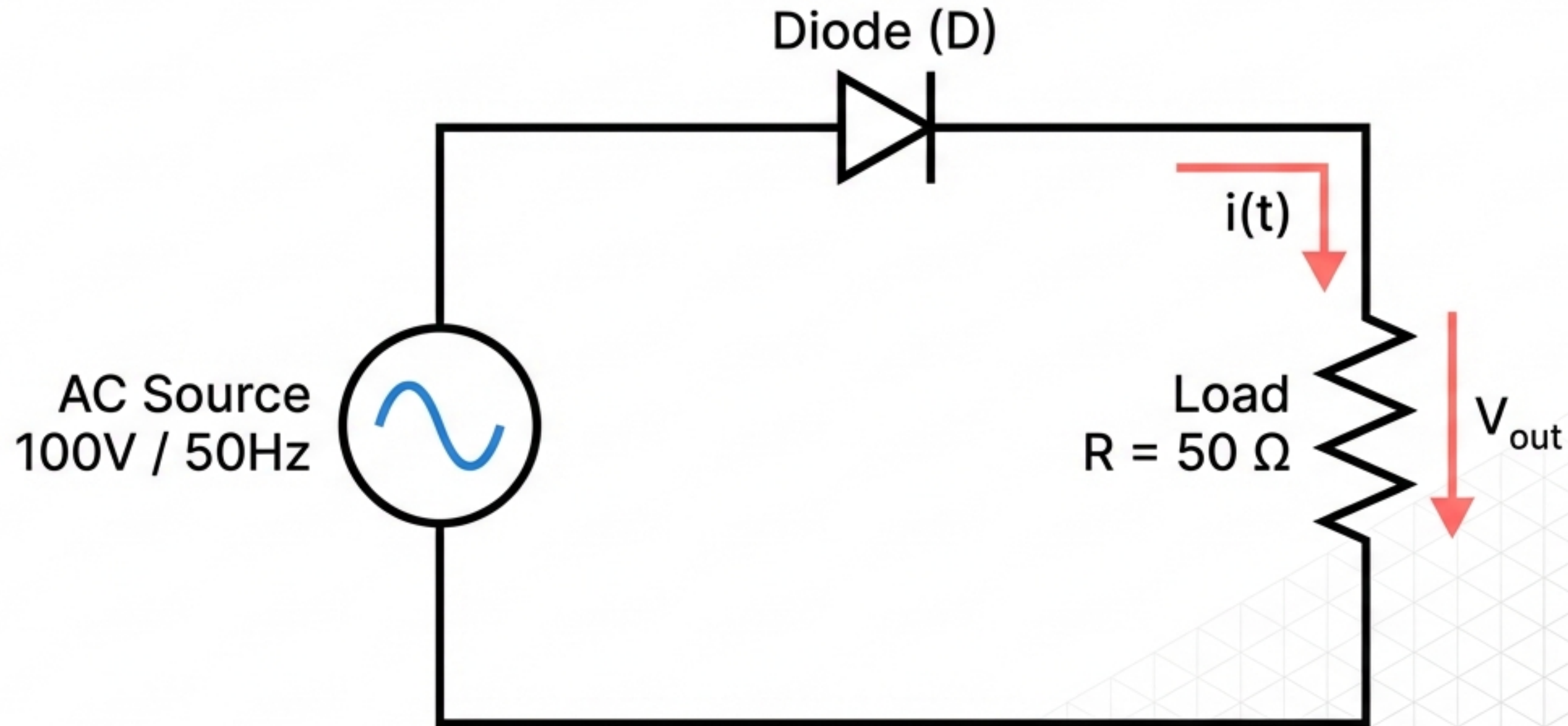


JetBrains Mono (JetBrains (Inter) #466) (Irev'in:Inter Tgrey (#EtBrains Mono. The architecture places the diode in series with the load. The diode acts as a gatekeeper, conducting current only when the **anode is positive** relative to the cathode (Forward Bias).

Simulink Component Inventory


Power Components



AC Voltage Source

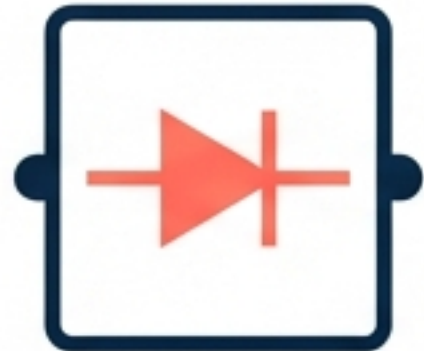

Diode

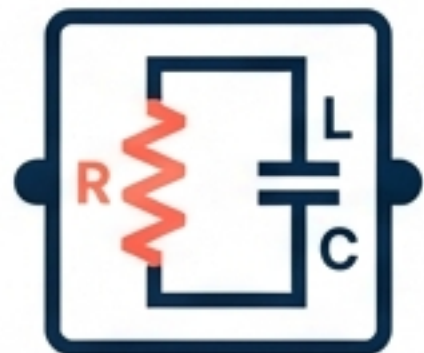

Series RLC Branch
(Set to R)


Instrumentation



Voltage Measurement



Current Measurement

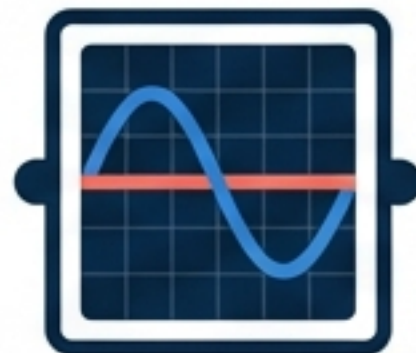

Scope


Simulation Engine



Powergui

Essential for discrete simulation solver.

Model Architecture and Signal Flow

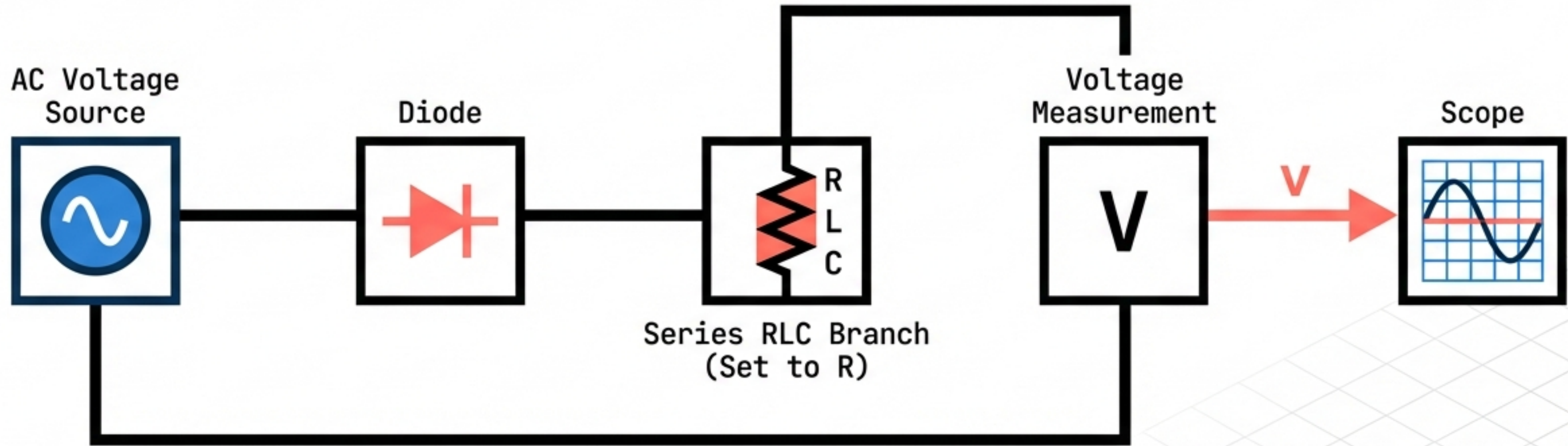


1. Series Connection: Source → Diode → Load
2. Parallel Sensing: Voltage Measurement spans the Load
3. Data Capture: Signal fed to Scope for analysis

Input Signal Characterization

Analysis Data

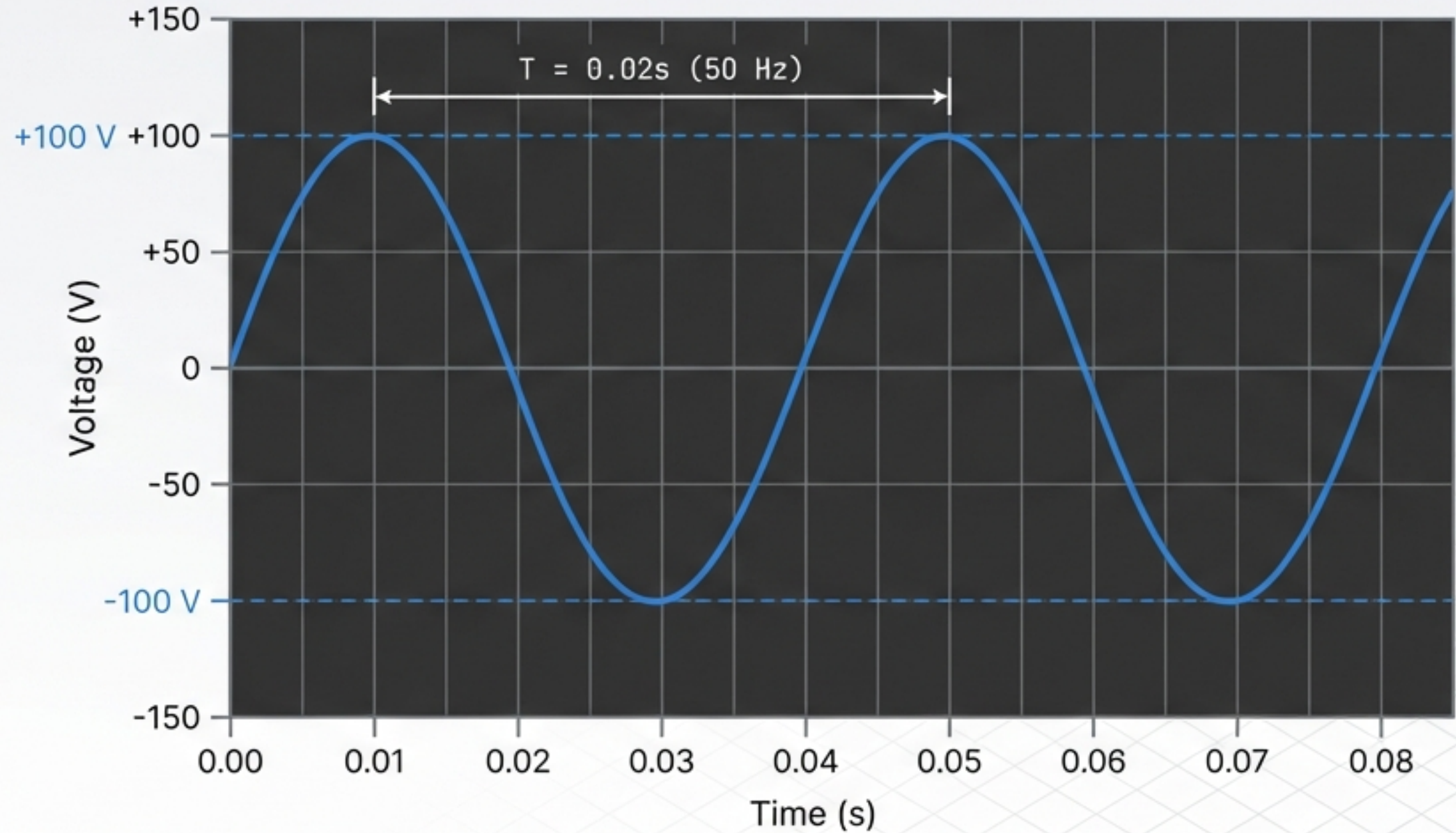
- Waveform: Sinusoidal AC
- Amplitude: 100 V Peak
- Frequency: 50 Hz
- Polarity: Symmetrical (+/-)




Output Signal Verification

Analysis Data

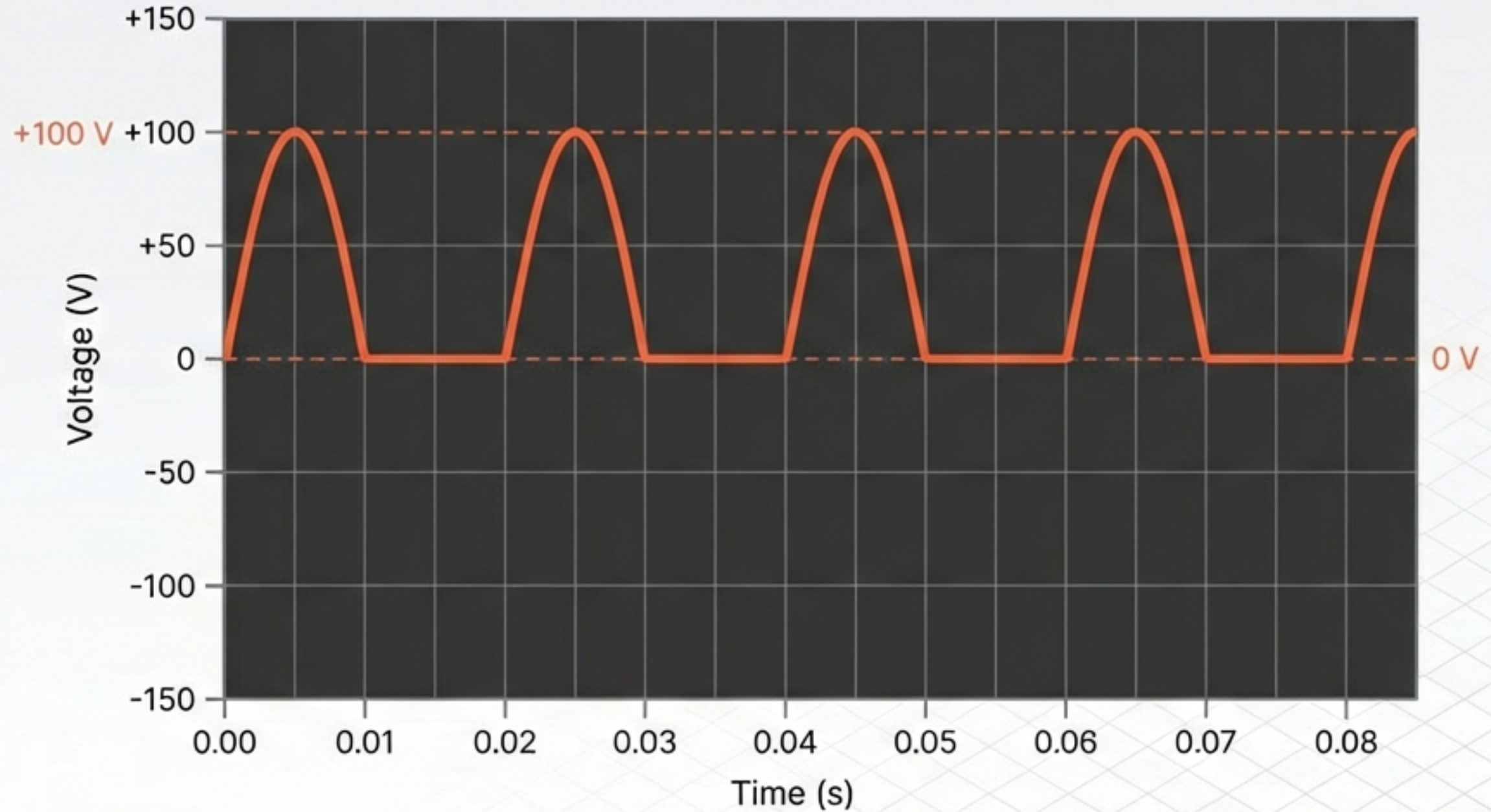- Waveform: **Pulsating DC**
- Positive Cycle: **Conducts**
- Negative Cycle: **Blocked (Clipped)**
- Current Flow: **Unidirectional**




The Rectification Process Visualized

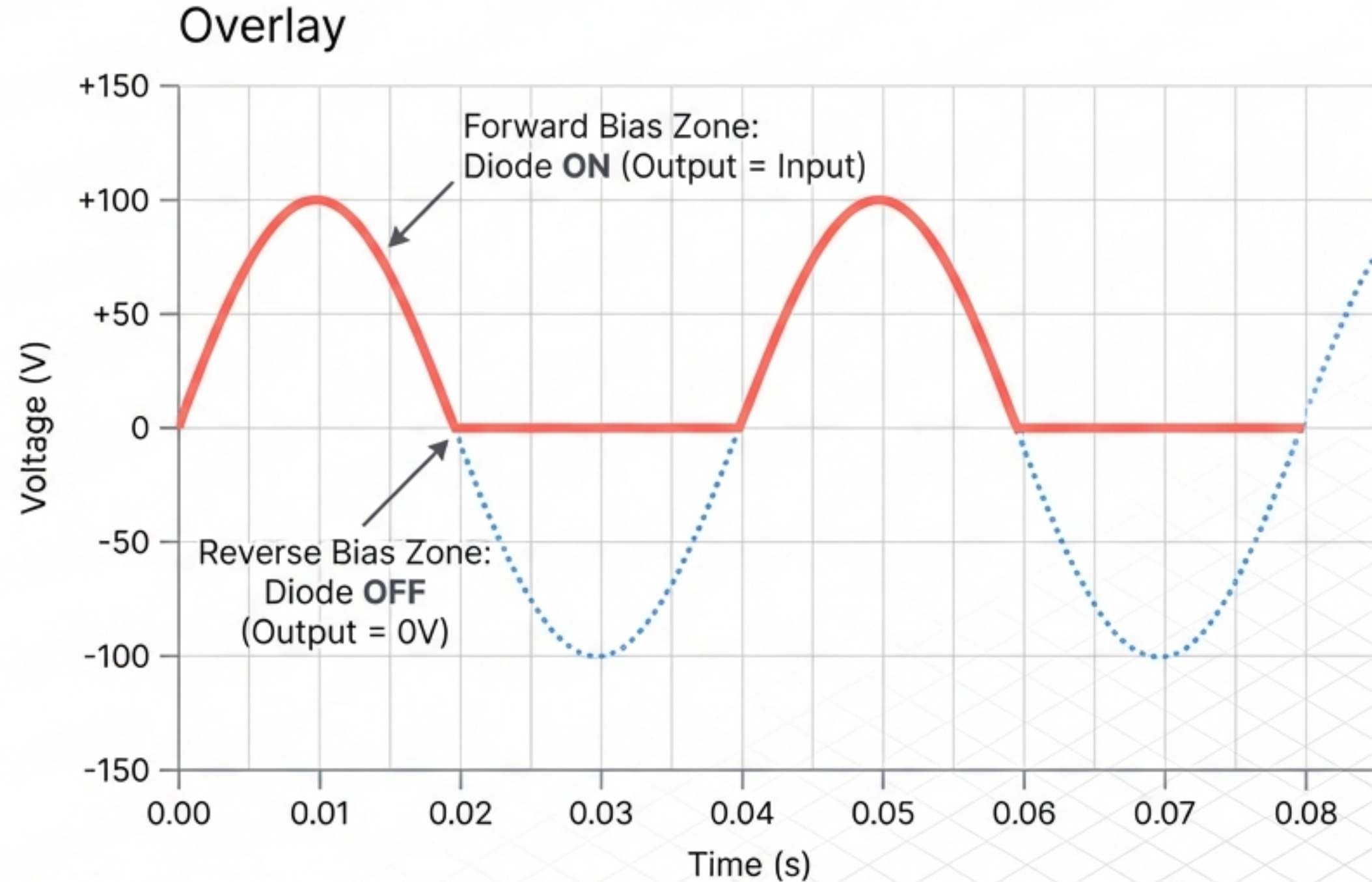


Visual confirmation of the 'Clipping' effect. The diode acts as an open switch during the negative half-cycle.

Evaluating Output Quality

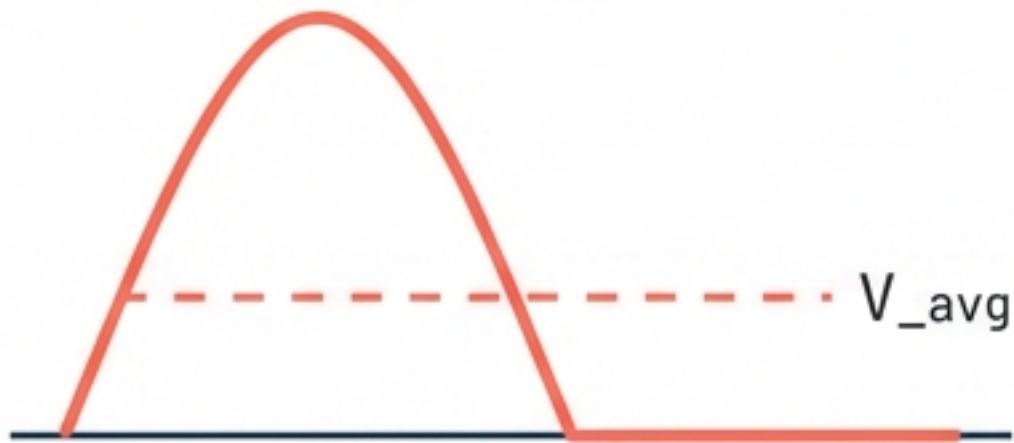


Reduced Average Voltage

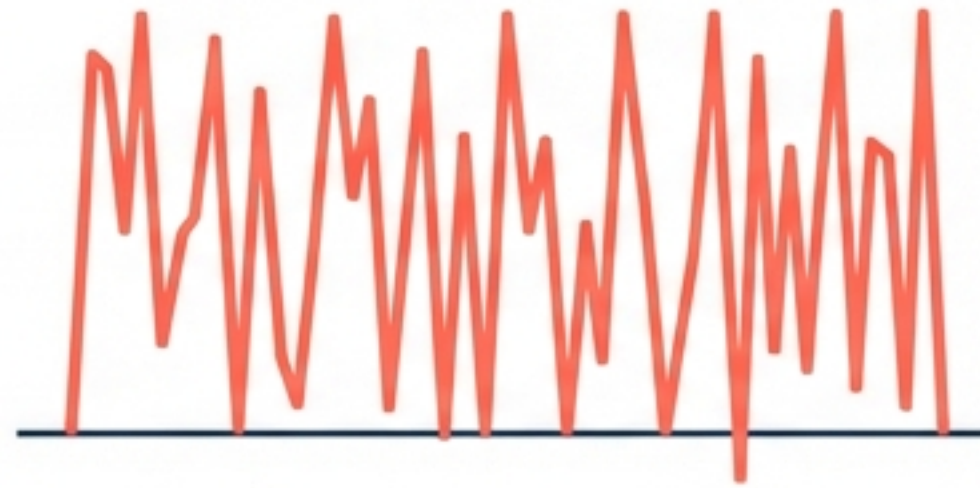Because energy is delivered only 50% of the time, the average DC voltage is significantly lower than the input peak voltage (approx 31.8% of V_{peak}).



High Ripple Factor

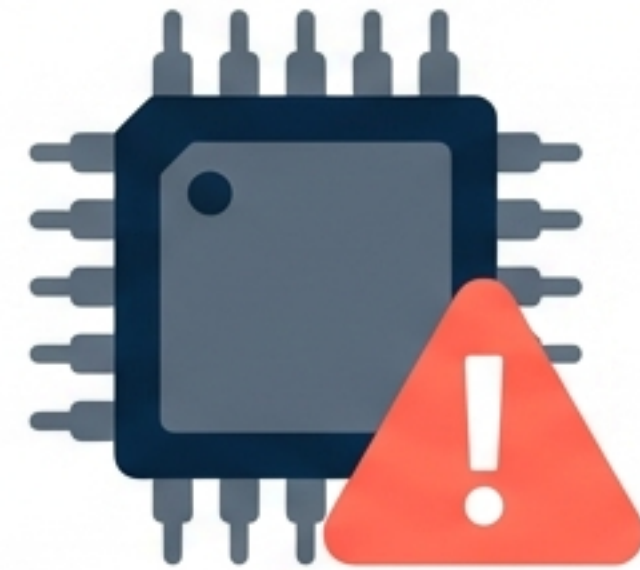The output is not a steady line. It pulses from 0 to 100V and back. This extreme fluctuation is called "Ripple".



Implication for Load


Raw pulsating DC is unsuitable for sensitive electronics without further smoothing (capacitors).

Strategic Advantages and Limitations



Advantages

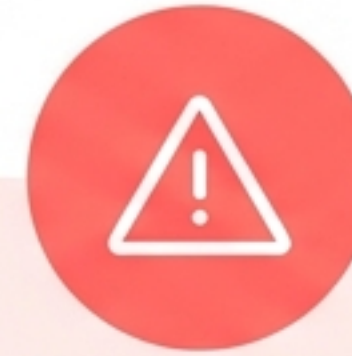- **Simplicity:** Minimal component count (1 Diode).
- **Cost Effective:** Extremely low implementation cost.
- **Robustness:** Fewer points of failure.



Limitations

- **Signal Quality:** High ripple requires heavy filtering.
- **Efficiency:** Low (utilizes only half the AC signal).
- **System Impact:** DC saturation risk for transformers.

Final Engineering Assessment

Summary of Findings

- The Single Phase Half-Wave Rectifier was successfully modeled and simulated.
- Waveform analysis confirms the blocking of negative half-cycles.
- **MATLAB Simulink** provides an accurate "glass box" environment for visualizing power electronics theory.



Status: VERIFIED & COMPLETE