

Simulation of Single Phase Full-Wave Bridge Rectification

Implementation and Analysis using MATLAB Simulink


KEY SIMULATION PARAMETERS

Input Voltage: **100 V**

Frequency: **50 Hz**

Load: **50 Ω (Resistive)**

Topology: **4-Diode Bridge**

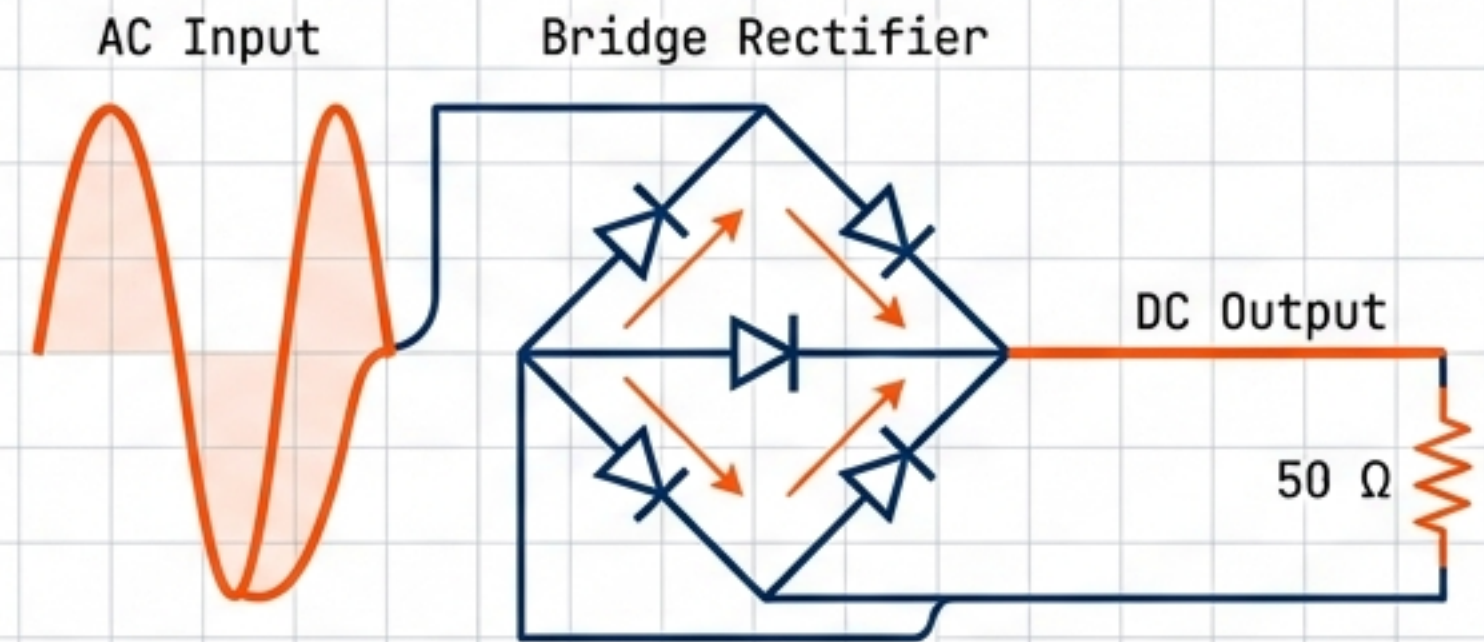

Course: Simulation and Control of Power Electronics Circuits (BEEL657B)

Department of Electrical and Electronics Engineering

Presenter: Dr. Sathish K R

Experiment Objectives and Fundamental Concepts

PRIMARY GOAL

To model a single-phase full-wave bridge rectifier within the Simulink environment to create a 'digital twin' of a physical circuit.

SPECIFIC OBJECTIVES


1. **Model:** Construct the circuit using standard Simulink Simscape components.
2. **Observe:** Capture input and output waveforms to verify rectification.
3. **Analyze:** Evaluate the rectified DC output characteristics across a $50\ \Omega$ load.

CONTEXTUAL NOTE

Rectifiers are foundational to DC power supplies, utilizing AC line voltage to produce unidirectional current. While half-wave rectifiers only utilize one half-cycle, the full-wave bridge maximizes efficiency by utilizing both.

Operational Theory: The Physics of Rectification

Positive Half Cycle

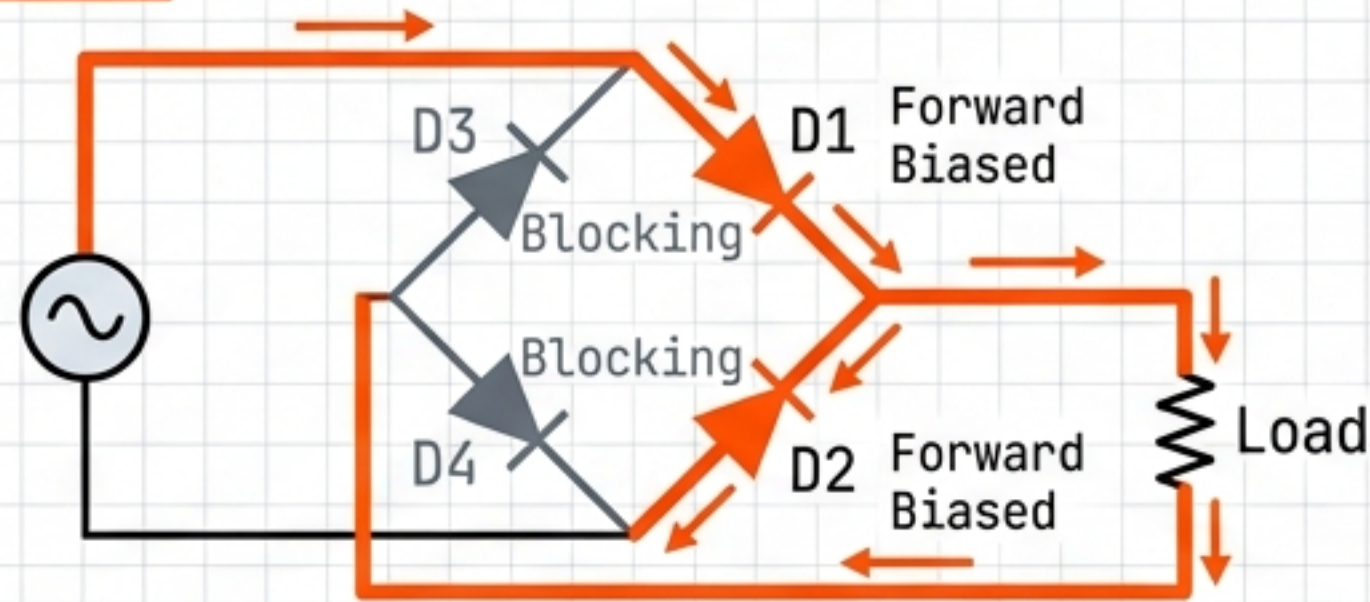


Diodes D1 & D2: Conducting

Diodes D3 & D4: Blocking

Path: Source → D1 → Load → D2 → Return




Negative Half Cycle

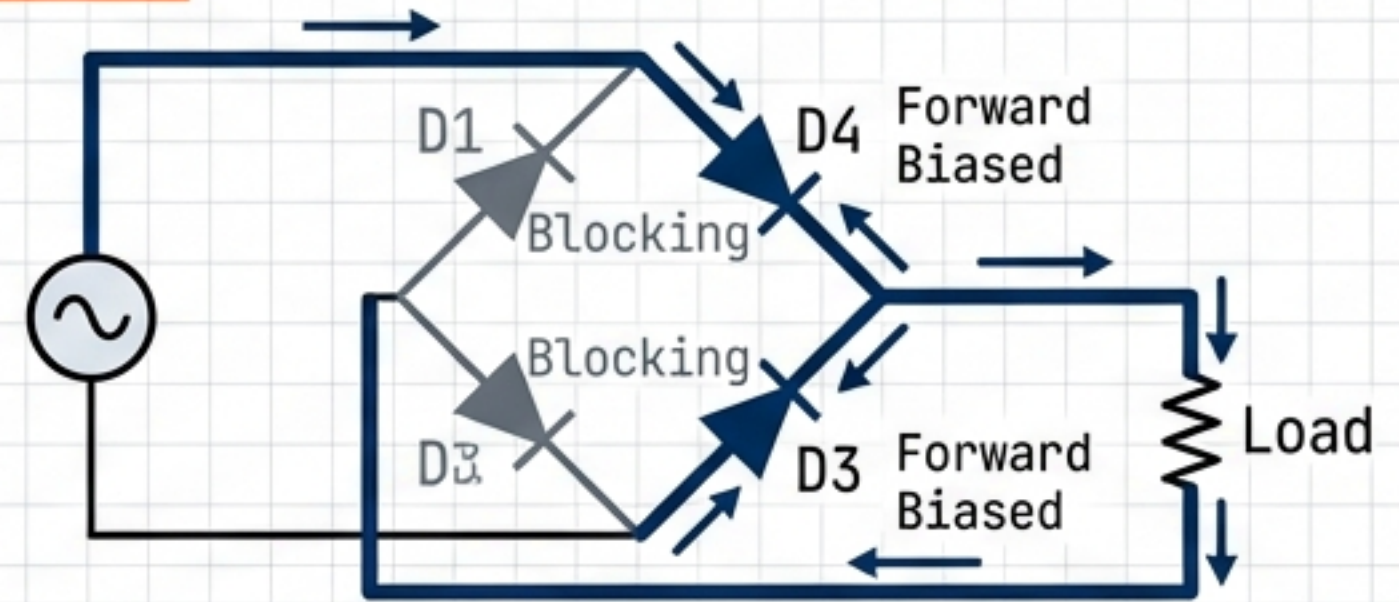

Diodes D3 & D4: Conducting

Diodes D1 & D2: Blocking


Path: Source → D3 → Load → D4 → Return

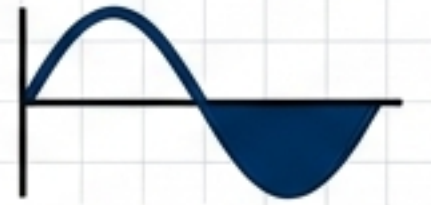

KEY TAKEAWAY

Despite the alternating input, the load current flows in the same direction during both cycles.


Schematic Diagram: The Bridge Topology

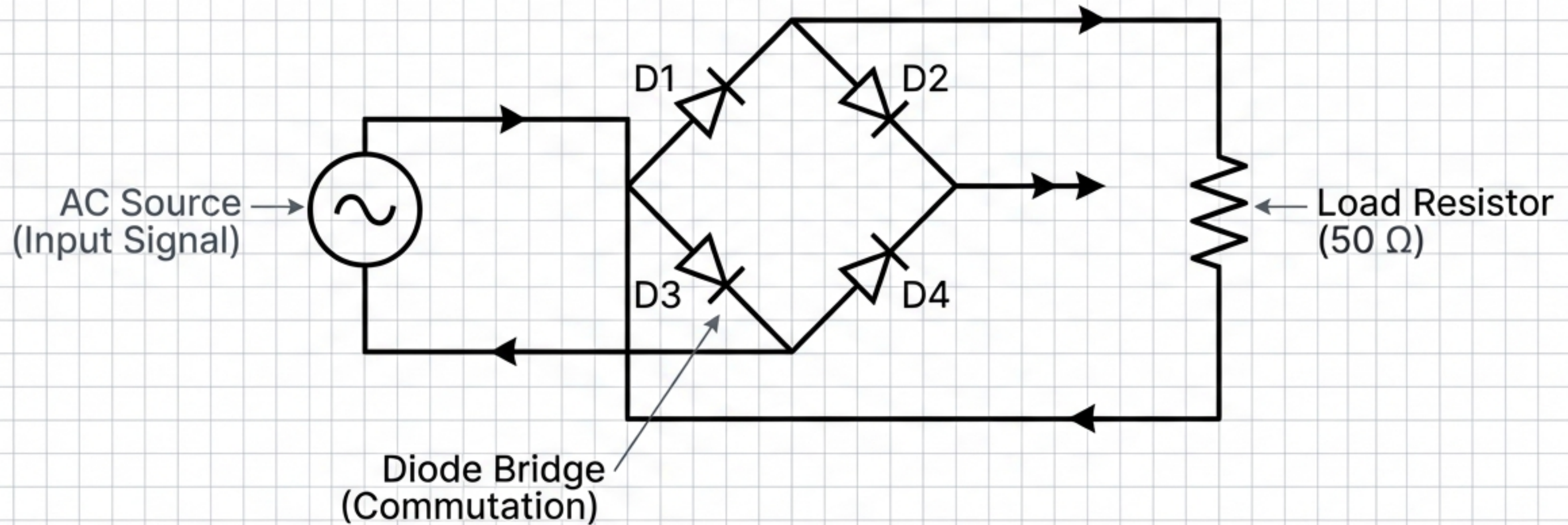

Simulation Parameters and Specifications

Accurate simulation requires precise parameter definitions to match theoretical calculations.

Parameter	Value / Setting
AC Supply Voltage	100 V (Peak Amplitude) (JetBrains Mono)
Frequency	50 Hz (JetBrains Mono)
Load Resistance	50 Ω (JetBrains Mono)
Diode Model	Ideal / Practical (0.7V drop) (JetBrains Mono)

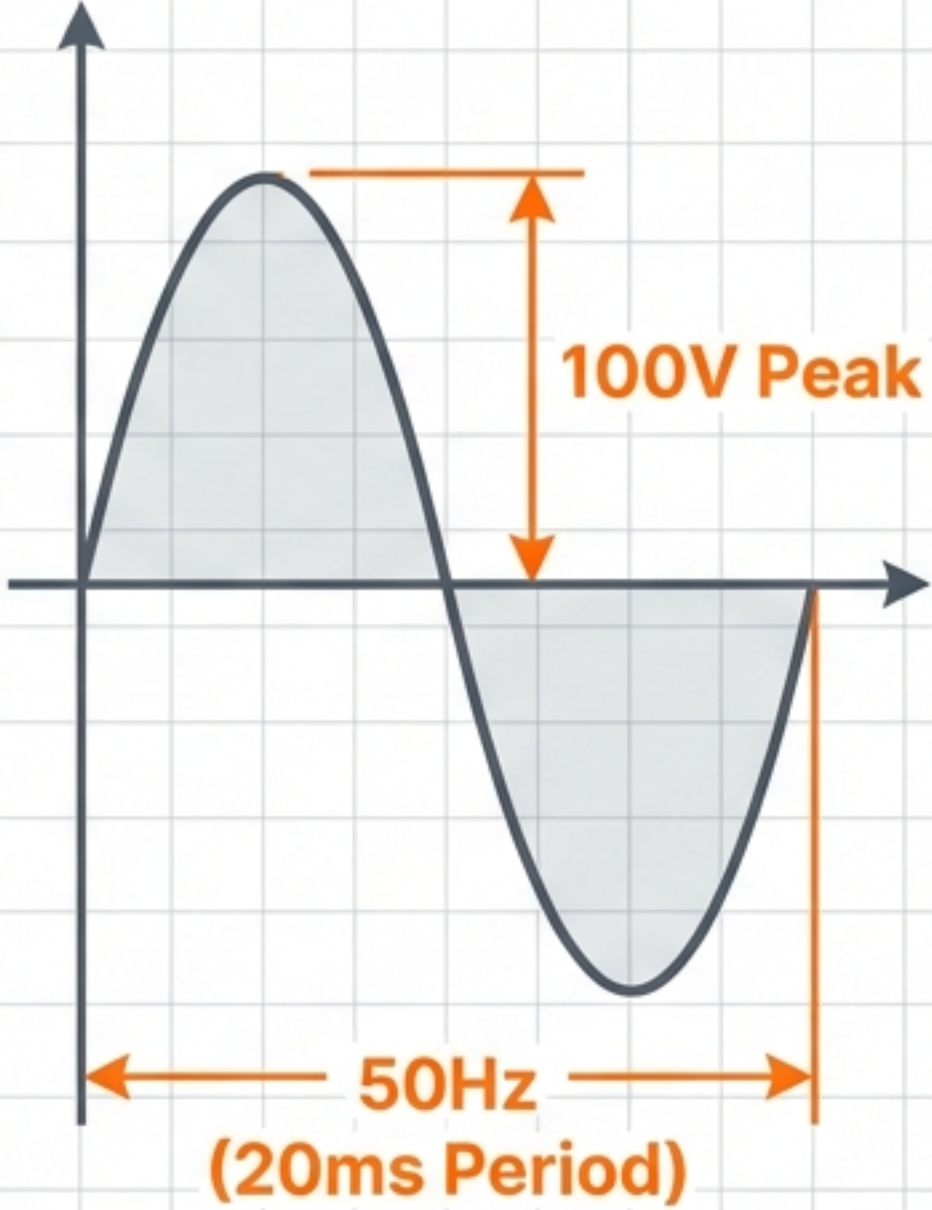

Required Simulink Library Components



AC Voltage
Source



Diode (×4)



Series RLC Branch
(Set to R)



Voltage
Measurement



Current
Measurement




Scope



Powergui
(Critical for Solver)

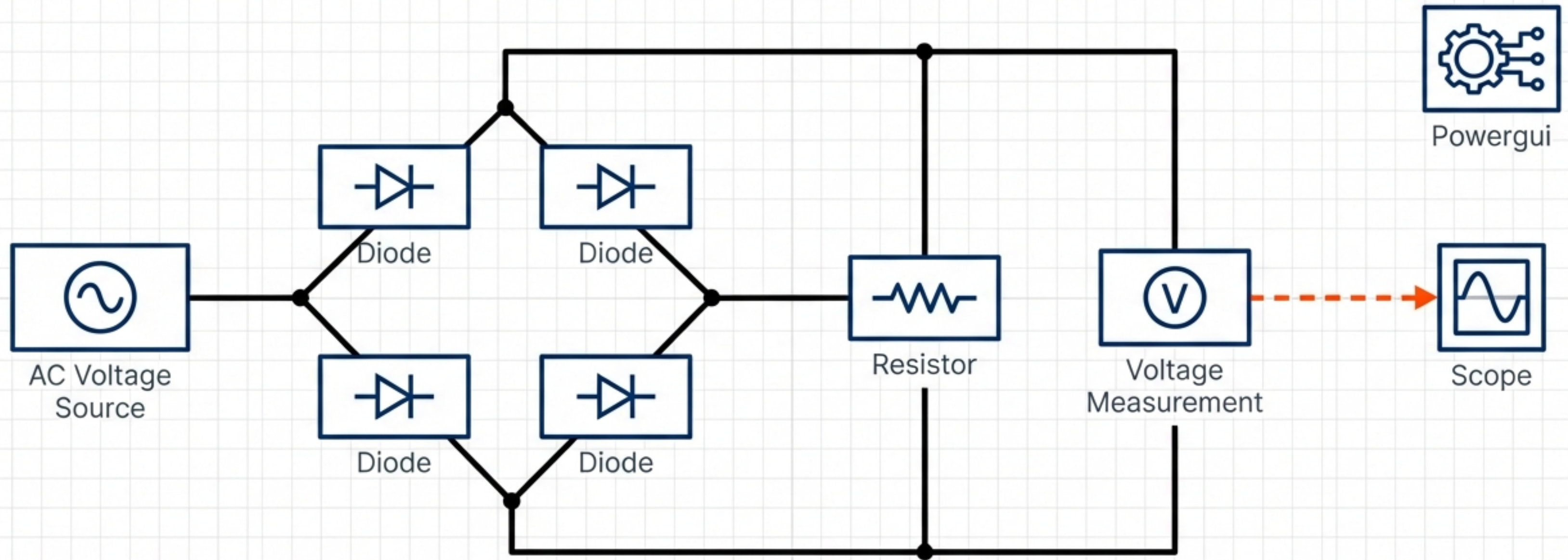
The Digital Workbench: Simulink Model Layout




The Voltage Measurement block captures the differential voltage across the load, sending real-time data to the Scope for analysis.

Verification: Waveform Analysis

Input Signal

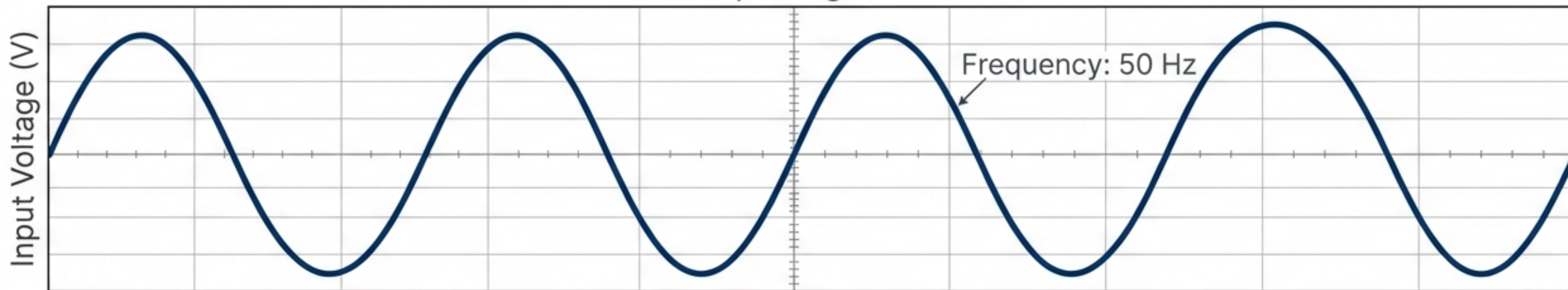


Output Signal

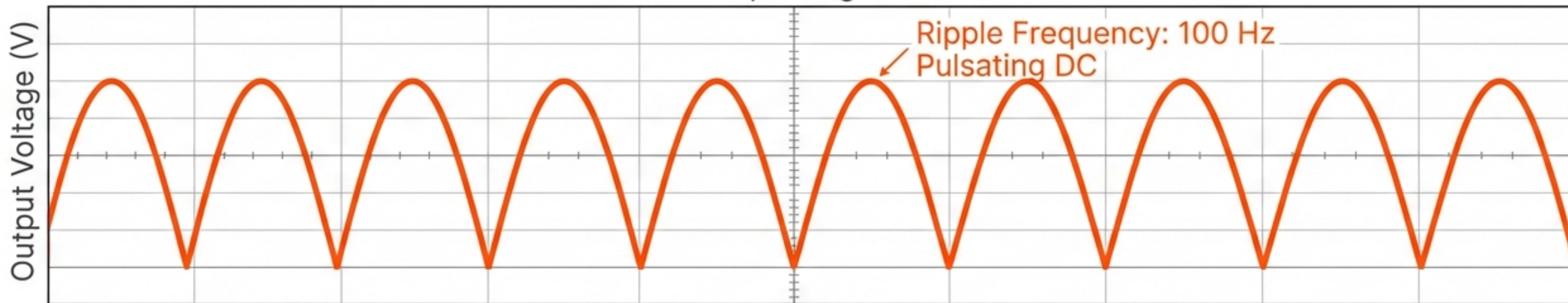

Time (s)

Observations and Results

Continuity

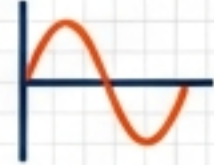


Unlike half-wave rectifiers, output voltage is present during both half-cycles of the AC input.

Magnitude




The average (DC) voltage is significantly higher than that of a half-wave configuration.

Smoothing

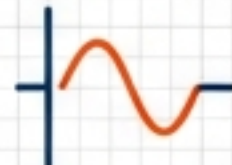

The ripple factor is reduced compared to half-wave rectification, though the output is still pulsating and not pure DC.

Frequency Shift

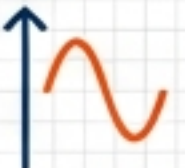

The output ripple frequency is confirmed to be double the input frequency (**100 Hz** vs **50 Hz**).

Advantages of Bridge Rectification

Efficiency




Higher rectification efficiency; power is delivered to the load during the entire AC cycle.

Quality




Lower ripple content makes the output easier to filter into smooth DC.

Design Utility Inter

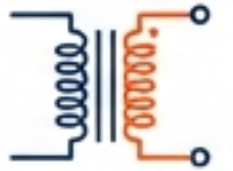


- **Better Transformer Utilization:** Secondary winding carries current in both half-cycles.
- **No Center-Tap Needed:** Works with standard two-wire transformer secondary.


Real-World Applications

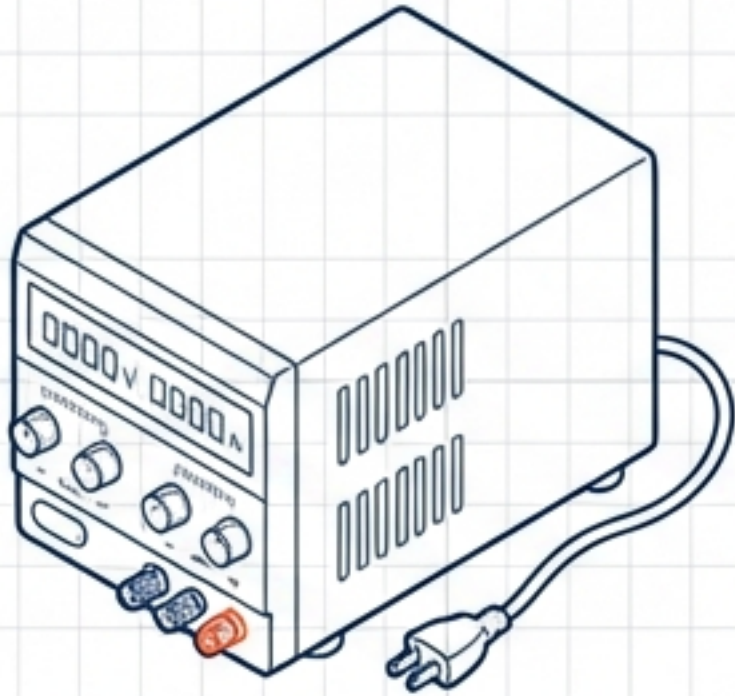


DC Power
Supplies

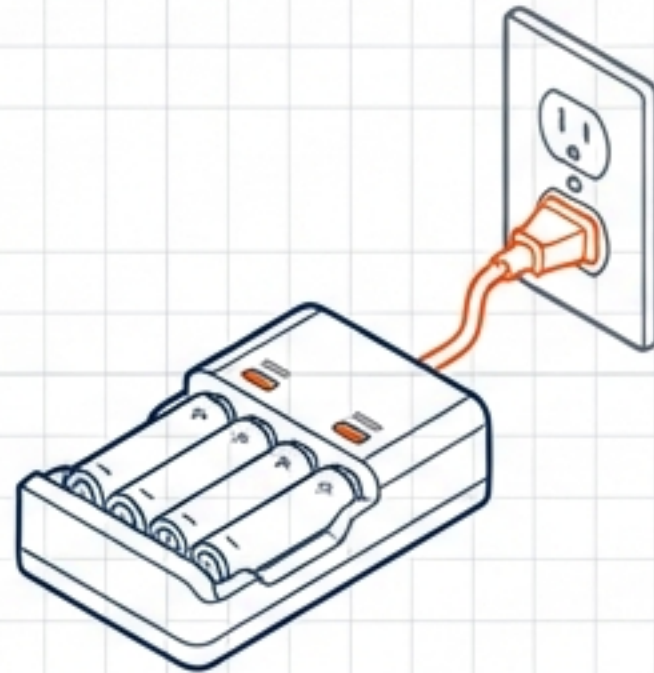

Battery
Chargers

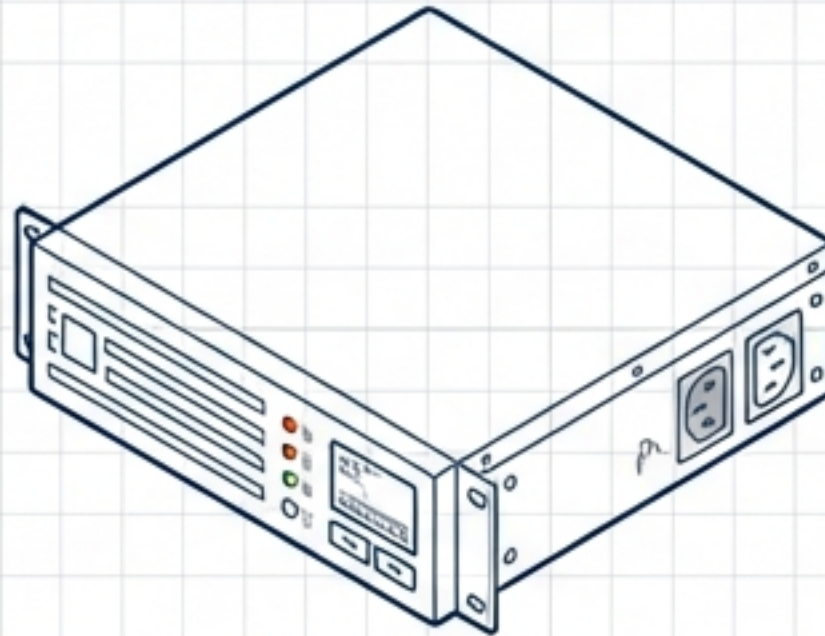

Uninterruptible
Power Supplies (UPS)

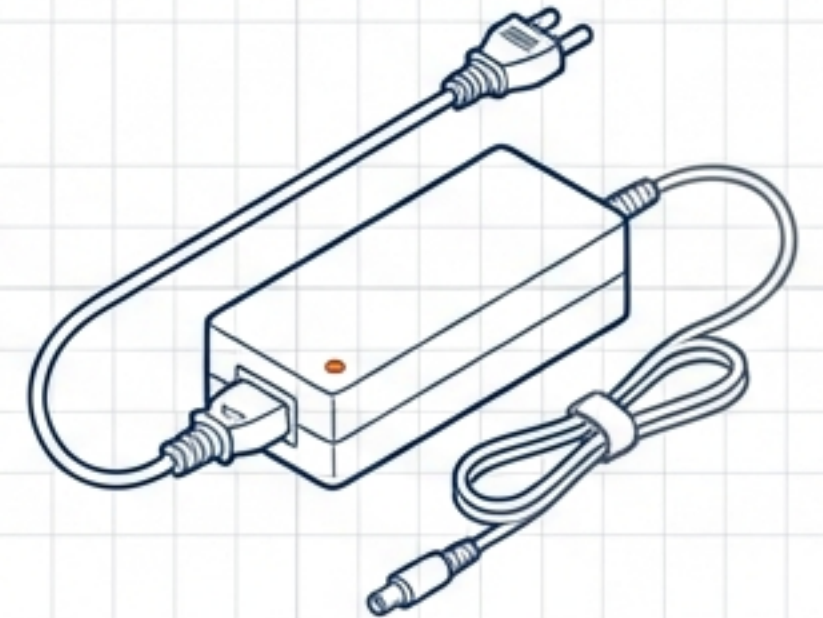

Consumer
Electronics

Conclusion

SUMMARY OF FINDINGS

- The Single Phase Full-Wave Bridge Rectifier was successfully modeled and simulated.
- MATLAB Simulink provided an accurate 'Digital Twin' visualization of the circuit behavior.
- Waveform analysis confirms the output is smoother and more efficient compared to half-wave rectification.
- The simulation verified the frequency doubling effect (Input 50Hz → Output 100Hz ripple).



References and Documentation

MathWorks Documentation

Full-Wave Rectifier (Simulink): [mathworks.com/help/sps/ug/full-wave-rectifier.html](https://www.mathworks.com/help/sps/ug/full-wave-rectifier.html)

Diode Block: [mathworks.com/help/sps/ref/diode.html](https://www.mathworks.com/help/sps/ref/diode.html)

AC Voltage Source: [mathworks.com/help/sps/ref/acvoltage.html](https://www.mathworks.com/help/sps/ref/acvoltage.html)

Powergui Block: [mathworks.com/help/sps/ref/powergui.html](https://www.mathworks.com/help/sps/ref/powergui.html)

Academic Resource

NPTEL – Power Electronics (Single-Phase Rectifiers):
nptel.ac.in/courses/108/105/108105066/